

# ELEC2208 Power Electronics and Drives

## DC-DC Converter

Yoshi Tsuchiya  
Smart Electronic Materials and Systems (SEMS)  
Research Group  
[yt2@ecs.soton.ac.uk](mailto:yt2@ecs.soton.ac.uk)

# Classification

- Phase-Controlled Thyristor Converter


**AC-AC, Voltage**

- Rectifier **AC-DC**

- Cycloconverter **AC-AC, Frequency**

- Inverter **DC-AC**

- DC-to-DC Converter **DC-DC**

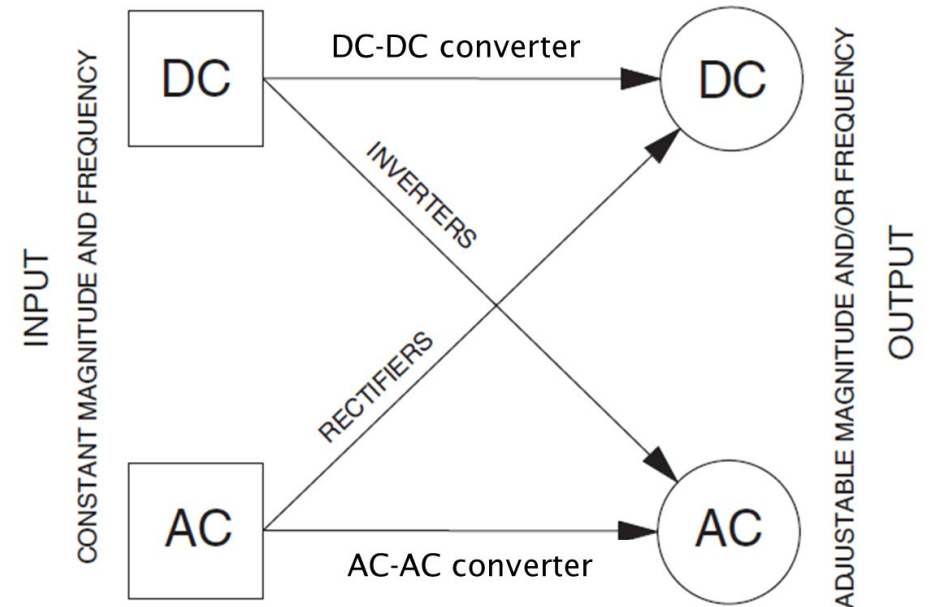

# Outline

---

Switching converter


Step-down (Buck) converter

Step-up (Boost) converter

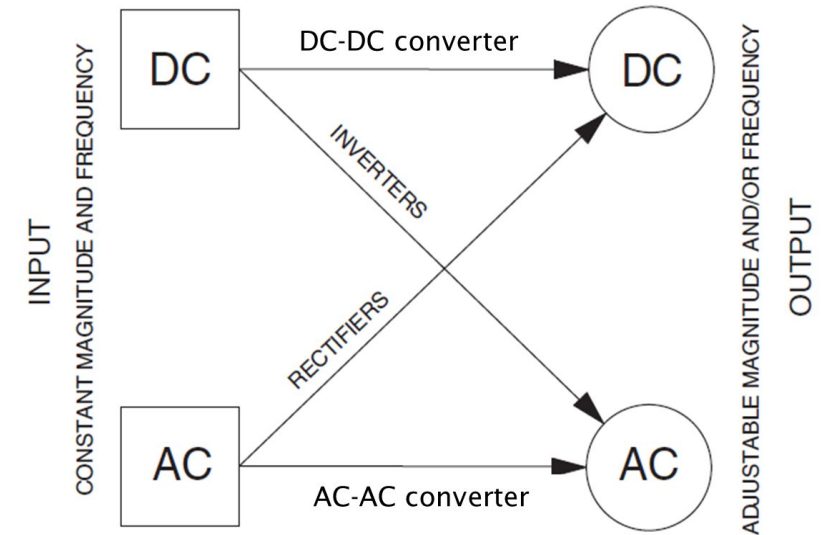
# What is DC-DC converter?

DC-DC converters are power electronic circuits that convert a dc voltage to a different DC voltage level, often providing a regulated output.


- Linear voltage regulator
- Switching converter (DC chopper)



# Linear voltage regulator

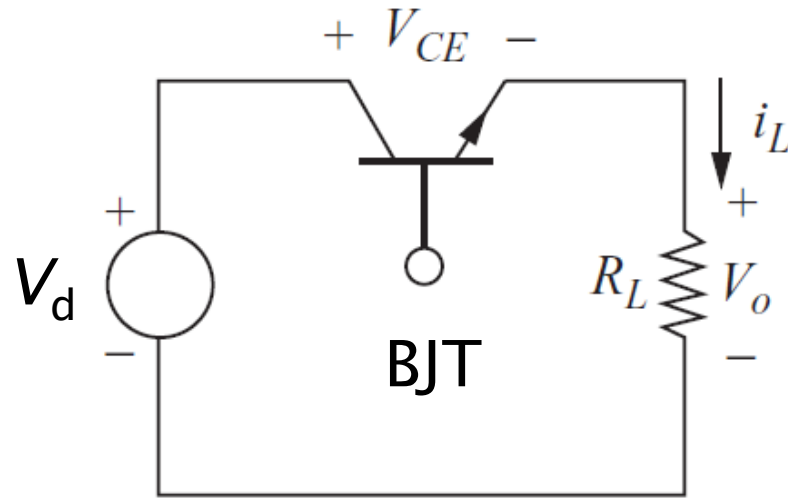

$$V_o = R_L i_L$$

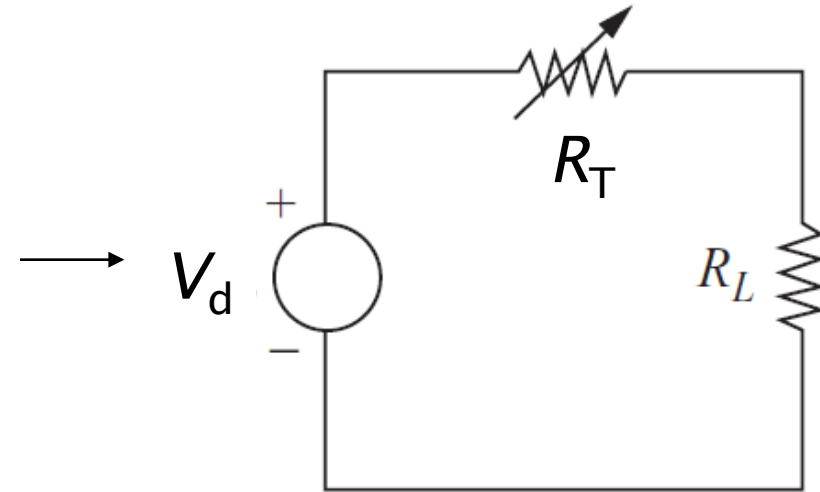


eg.  $V_d = 9 \text{ V}$ ,  $R_L = 3 \Omega$ ,  $R_T = 6 \Omega$

$$i_L = 1 \text{ A}, V_o = 3 \text{ V}$$


Voltage is converted from 9 V (Source) to 3 V (Output).

What is problem?  $\longrightarrow$  Power efficiency 33.333 %

# Switching Converter (DC Chopper)

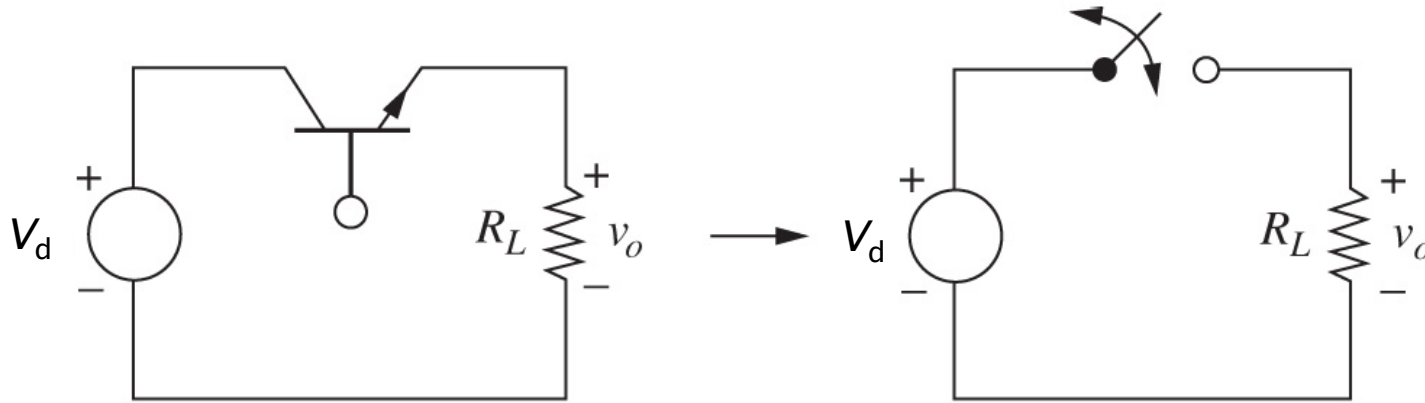


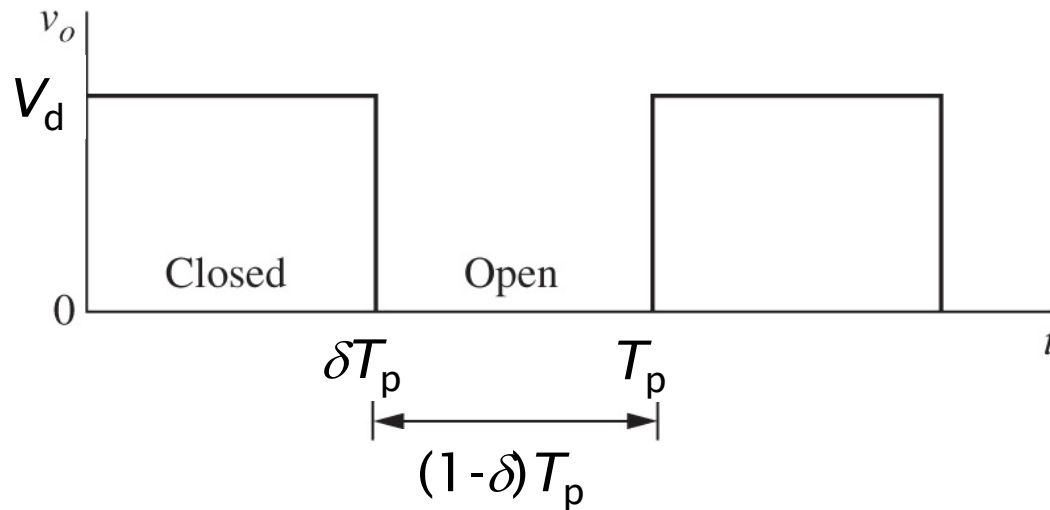
- When the switch is open, there is no current in it; when the switch is closed, there is no voltage across it.




- Duty ratio  $\delta$  is the fraction of the switching period that the switch is closed.
- The average or dc component of the output voltage is  $V_o = \delta V_d$ .
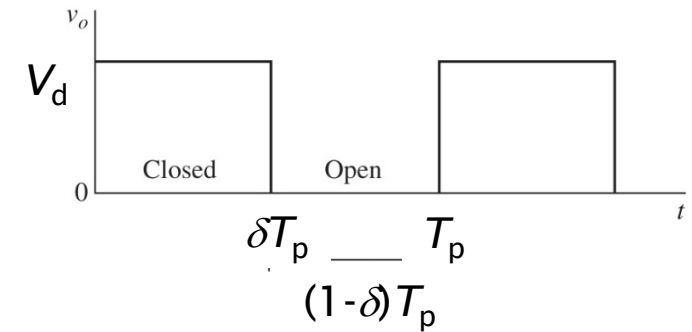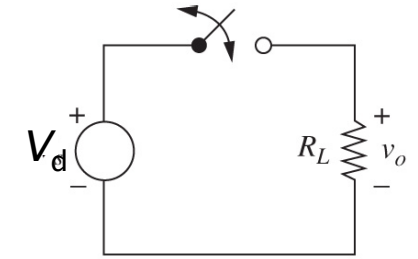
# Switching Converter (DC Chopper)

- Transistor operates as an electronic switch by being completely **on** or completely **off** (saturation or cutoff for a BJT or the triode and cutoff regions of a MOSFET).
- The power absorbed by the ideal switch is zero.
- Therefore, all power is absorbed by the load, and the **energy efficiency is 100%**.
- Losses will occur in a real switch because the voltage across it will not be zero when it is on (conduction loss).
- The switch must pass through the linear region when making a transition from one state to the other (switching loss).




# Step down (Buck) Converter

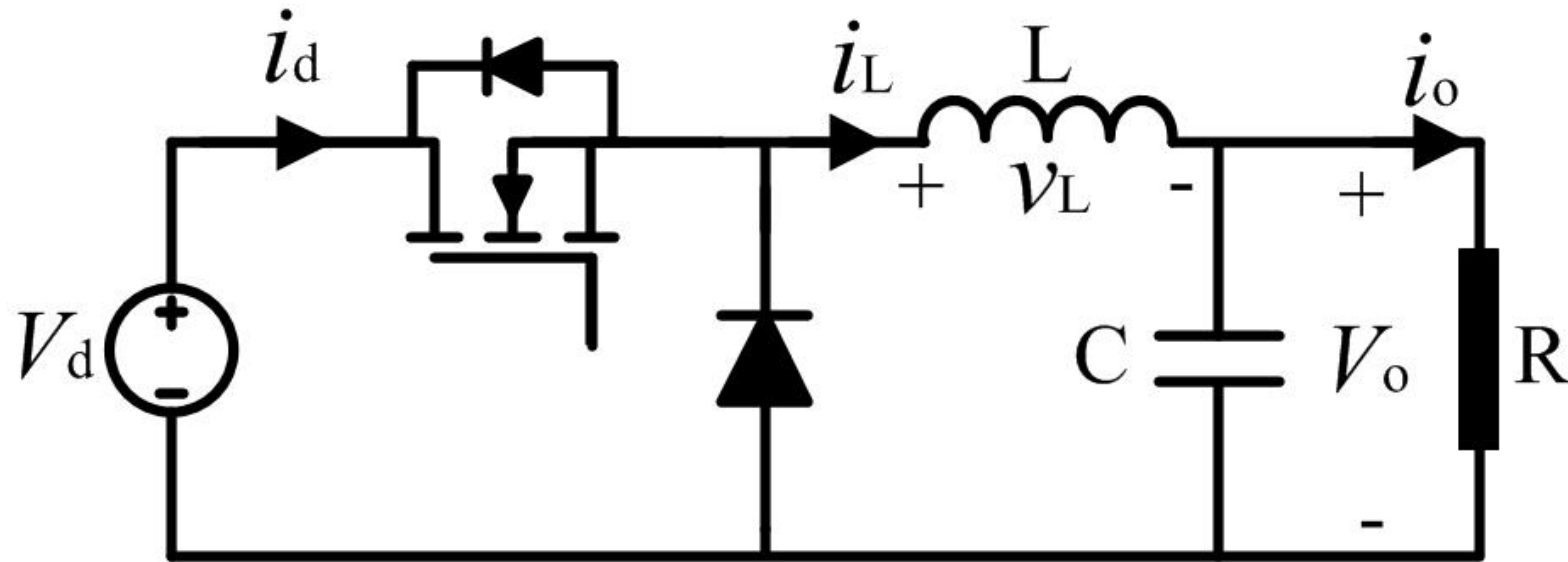


- Three states in operation
- Three modes of operation



# Three states in operation

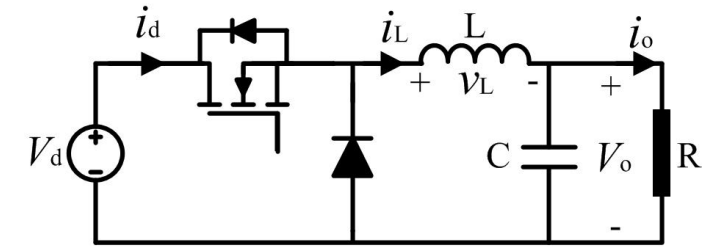


State 1

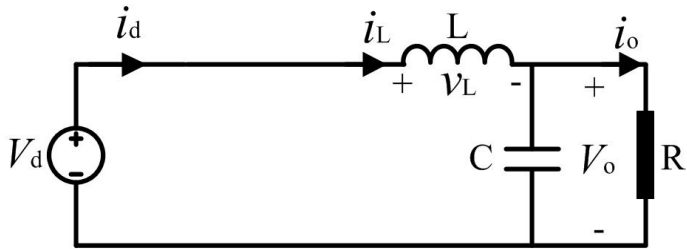

- MOSFET ON
- Diode reverse biased
- Inductor stores energy

$$v_L = V_d - V_o$$


State 2

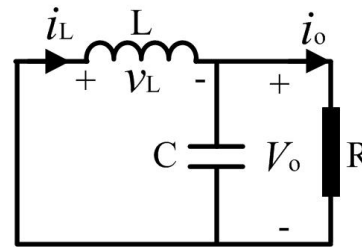

- MOSFET OFF
- Inductor current freewheels through diode

$$v_L = -V_o$$

State 3

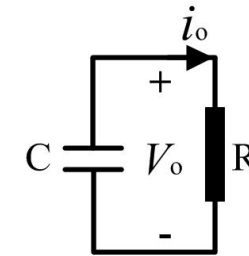

- MOSFET OFF
- Stored energy (inductor) fully discharged


$$i_L = 0$$

# Three operation modes

---

1. Continuous current operation      State 1 & 2
2. Boundary between continuous and discontinuous  
current operation      State 1 & 2
3. Discontinuous current operation      State 1, 2 & 3

# Continuous current operation

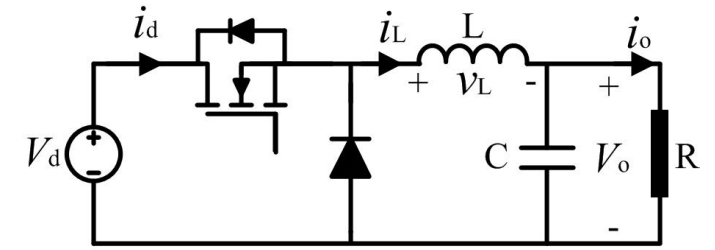

$\delta$ : Duty ratio

$$t_1 = \delta T_p$$

$$t_2 = (1 - \delta) T_p$$

$T_p$ : Period

On time

Off time

**Inductor voltage  $v_L$**

$$V_d - V_o$$

State 1 (On state)

$$-V_o$$

State 2 (Off state)



**Inductor current  $i_L$**

$I_1$ : Maximum current



$I_2$ : Minimum current

$I_L$ : Average inductor current

$$I_L = I_o$$

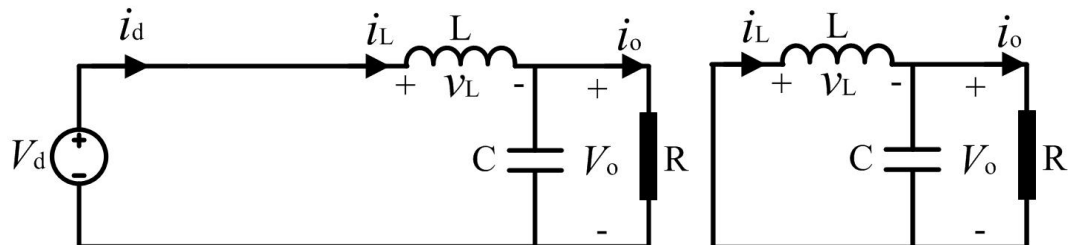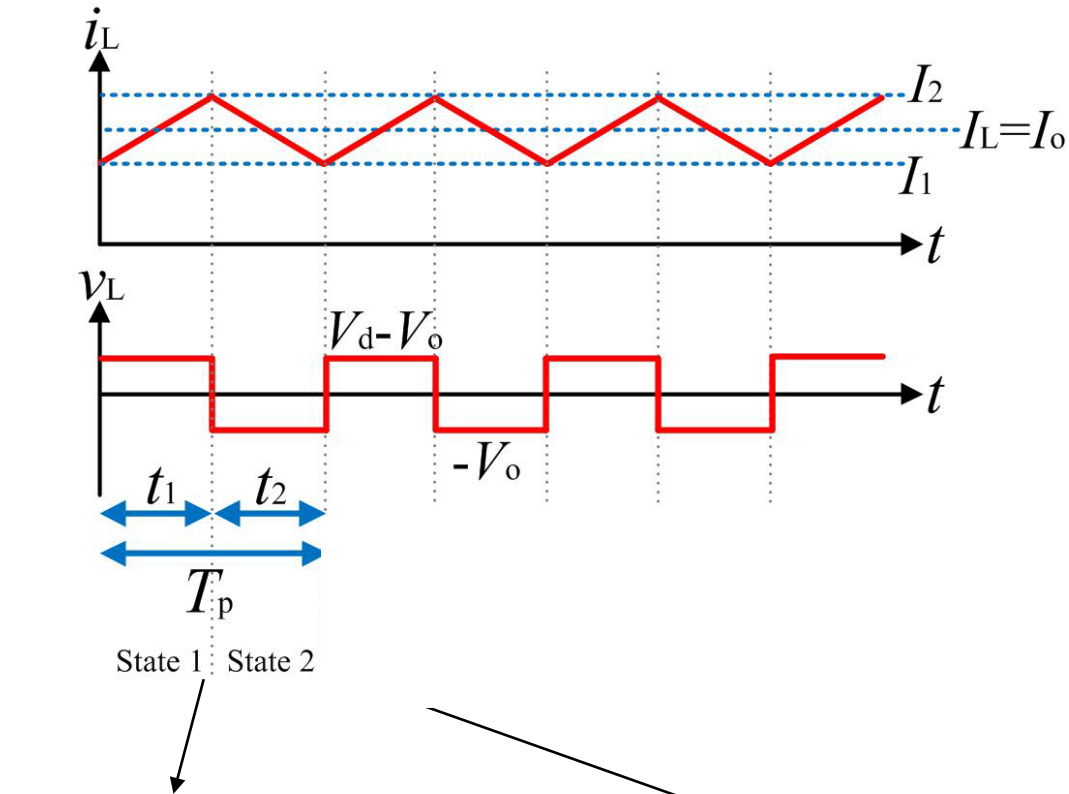

# Continuous current operation

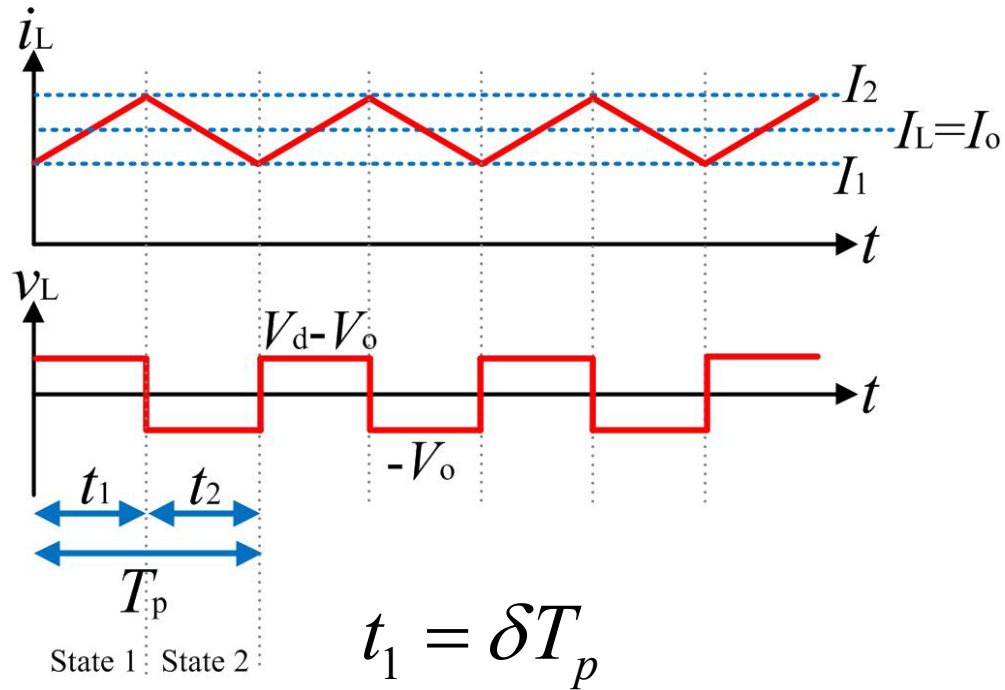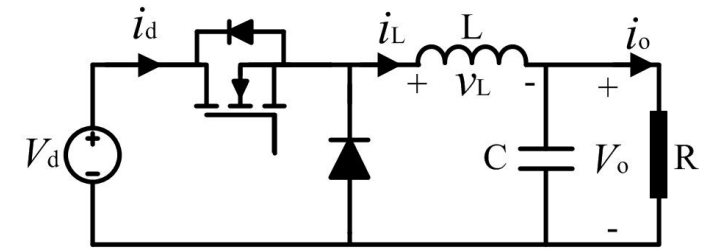

$$t_1 = \delta T_p$$

$$t_2 = (1 - \delta) T_p$$

$$I_L = I_o = \frac{I_1 + I_2}{2}$$

At periodic steady-state, the average inductor voltage is zero.

$$V_L = \frac{1}{T_p} \int_0^{T_p} v_L dt = 0$$


$$\frac{1}{T_p} [(V_d - V_o)t_1 + (-V_o)t_2] = 0$$

$$\frac{1}{T_p} [(V_d - V_o)\delta T_p + (-V_o)(1 - \delta)T_p] = 0$$

$$V_o = \delta V_d$$

# Continuous current operation

## Example question

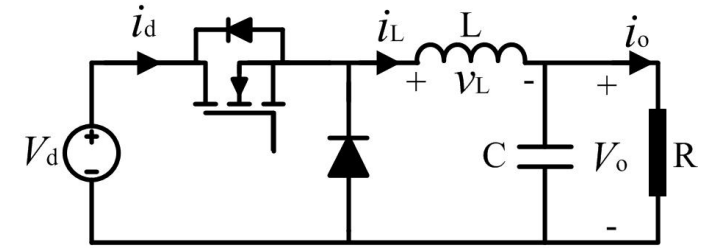

The buck dc-dc converter has the following parameters:

$$V_d = 50 \text{ V}, \quad \delta = 0.4, \quad L = 400 \text{ } \mu\text{H}$$
$$C = 100 \text{ } \mu\text{F}, \quad f = 20 \text{ kHz}, \quad R = 20 \text{ } \Omega$$

Assuming ideal components, calculate

- (a) the output voltage  $V_o$
- (b) the maximum and minimum inductor current.

# Answer

(a) The output voltage  $V_o$

$$V_o = \delta V_d = 50 \times 0.4 = 20 \text{ V}$$

(b) The maximum and minimum inductor current

$$I_o = V_o / R = 20 / 20 = 1 \text{ A}$$

$$v_L = L \frac{di_L}{dt}$$



$$\Delta i = (V_d - V_o)t_1 / L = (V_d - V_o)\delta T_p / L$$

$$= (V_d - V_o)\delta / fL$$



$$= (30 \times 0.4) / (20 \times 10^3 \times 400 \times 10^{-6}) = 1.5 \text{ A}$$

$$\Delta i / 2 = 0.75 \text{ A}$$
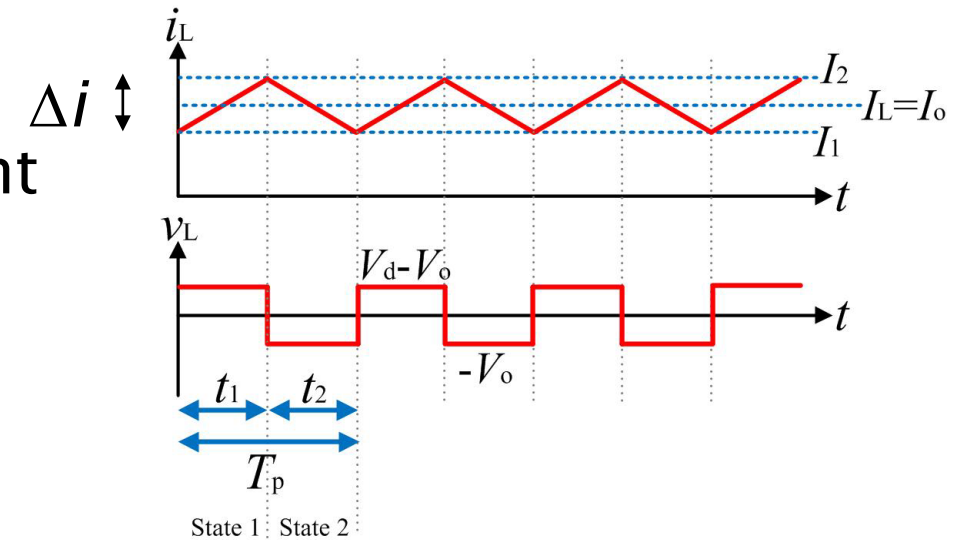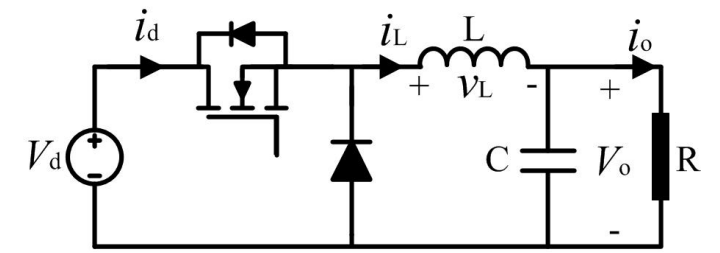
$$I_2 = I_o + \Delta i / 2 = 1.75 \text{ A} \quad I_1 = I_o - \Delta i / 2 = 0.25 \text{ A}$$



# Boundary condition

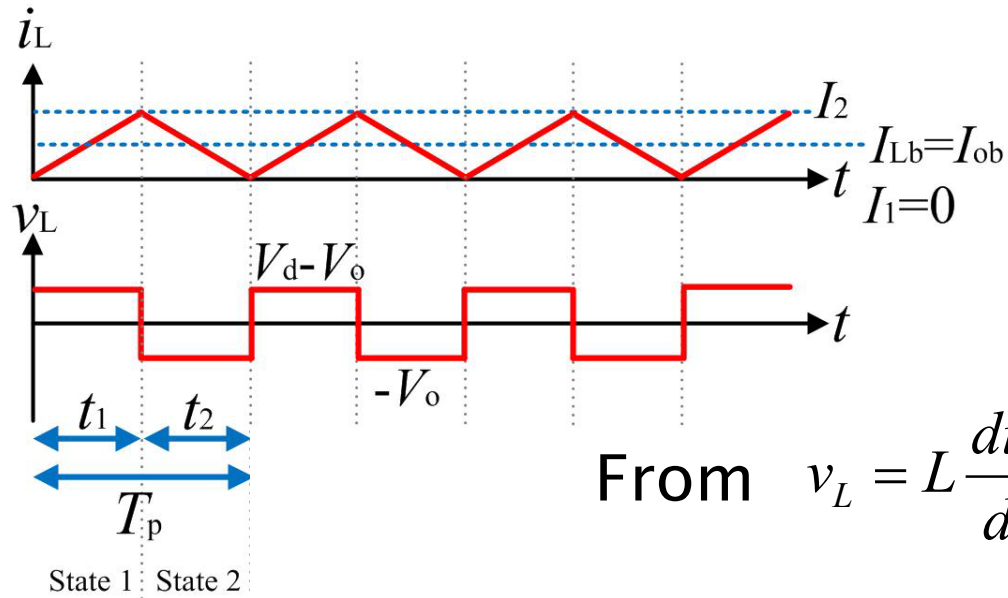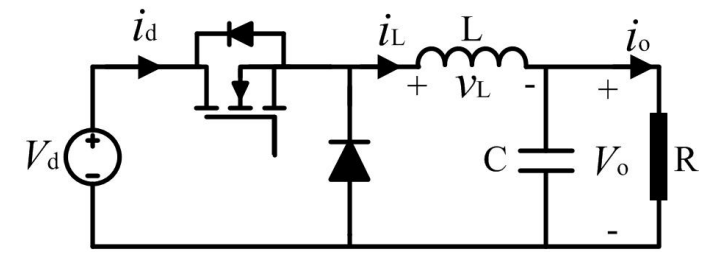

The minimum inductor current  $I_1 = 0$

The average inductor current at boundary  $I_{Lb} = \frac{I_2}{2}$

From  $v_L = L \frac{di_L}{dt}$  at State 1 (On state),  $V_d - V_o = L \frac{I_2}{\delta T_p}$

The maximum current  $I_2 = \frac{(V_d - V_o) \delta T_p}{L}$

$$I_{Lb} = \frac{(V_d - V_o) \delta T_p}{2L} = \frac{(V_d - \delta V_d) \delta T_p}{2L} = \frac{(1 - \delta) \delta T_p V_d}{2L}$$



$$t_1 = \delta T_p$$

$$t_2 = (1 - \delta) T_p$$

$$V_o = \delta V_d$$

$$I_{ob} = I_{Lb} = \frac{(1 - \delta) \delta T_p V_d}{2L}$$

# Discontinuous current operation

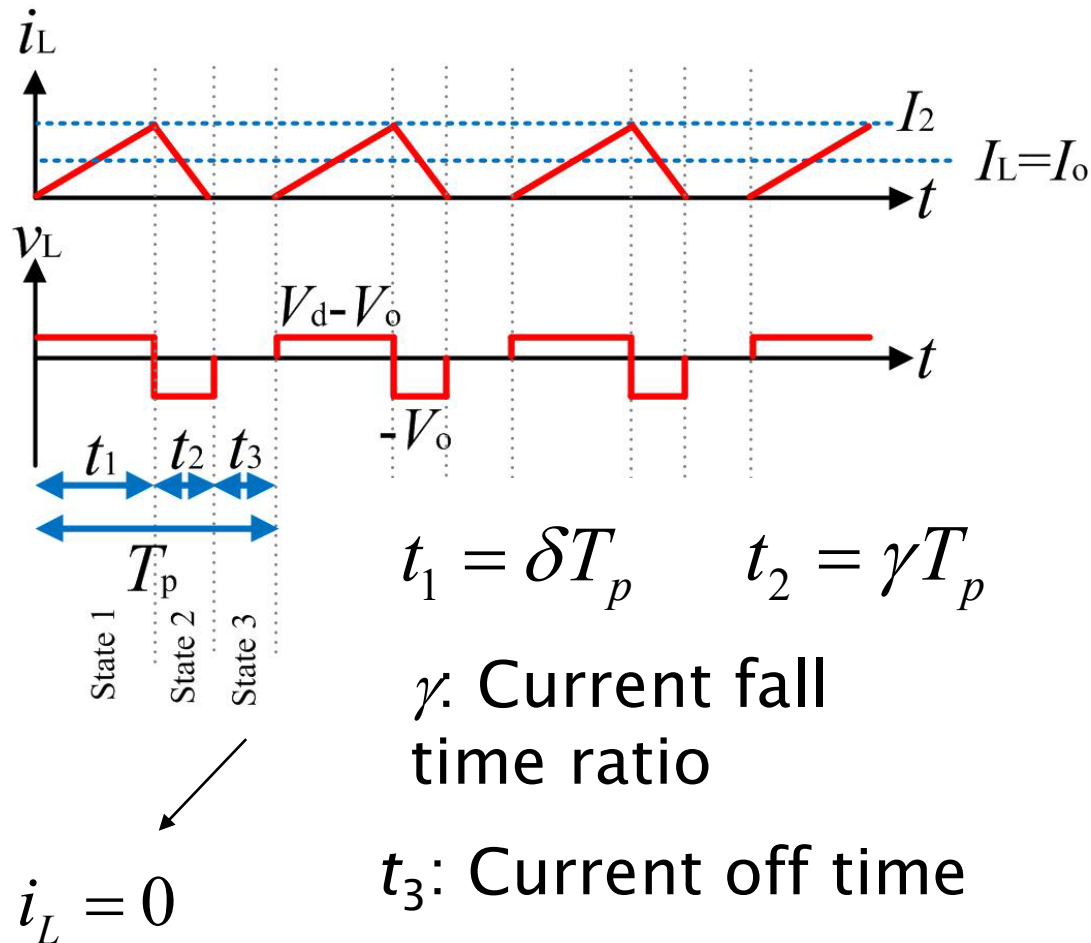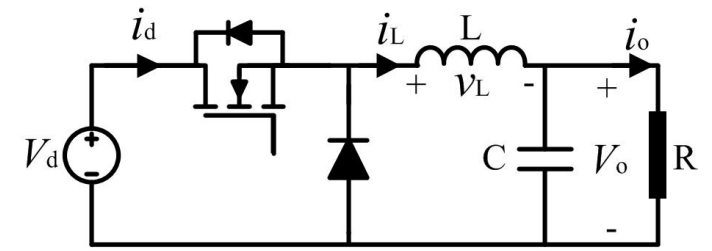

$$V_L = \frac{1}{T_p} \int_0^{T_p} v_L dt = 0$$



$$\frac{1}{T_p} [(V_d - V_o)t_1 + (-V_o)t_2] = 0$$

$$\frac{1}{T_p} [(V_d - V_o)\delta T_p + (-V_o)\gamma T_p] = 0$$

$$V_o = \frac{\delta}{\delta + \gamma} V_d$$



# Discontinuous current operation

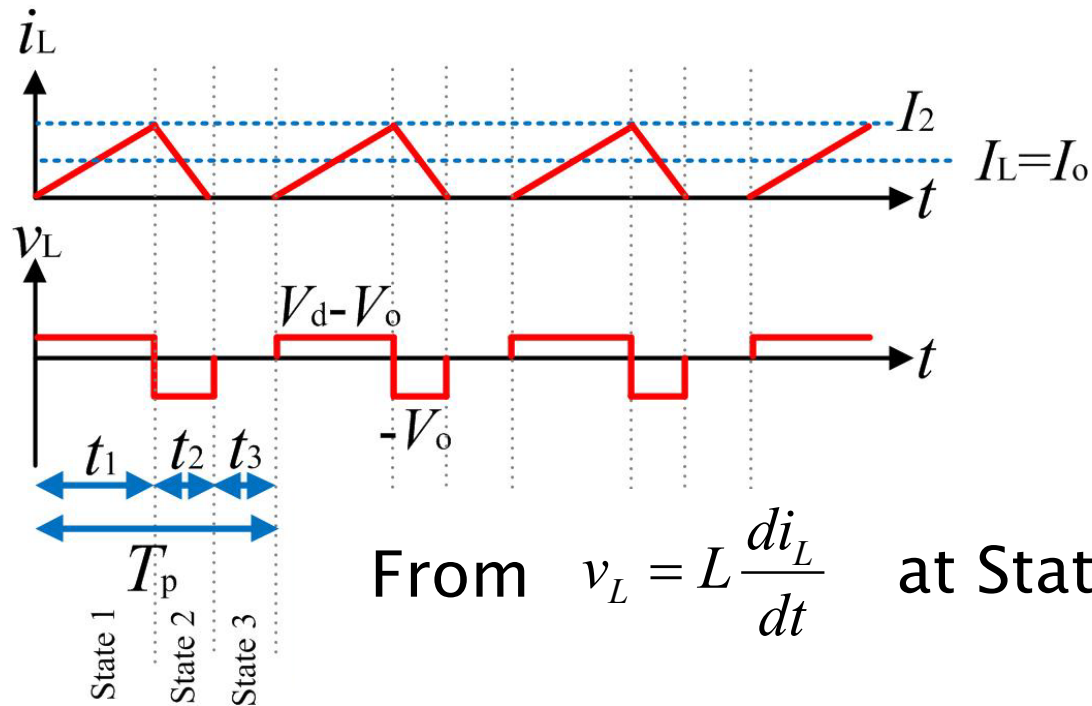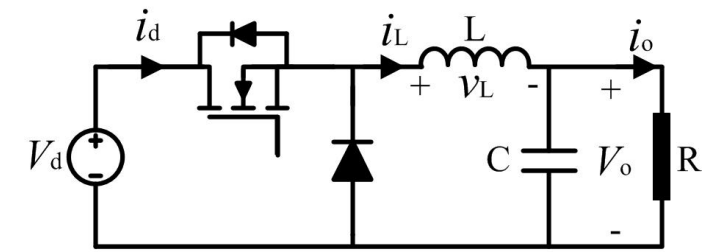

From  $v_L = L \frac{di_L}{dt}$  at State 1 (On state),

$$V_d - V_o = L \frac{I_2}{\delta T_p} \quad I_2 = \frac{(V_d - V_o) \delta T_p}{L}$$

From  $v_L = L \frac{di_L}{dt}$  at State 2 (Off state),  $-V_o = -L \frac{I_2}{\gamma T_p}$   $I_2 = \frac{\gamma T_p V_o}{L}$

$$t_1 = \delta T_p$$



By equalising  $I_2$ ,  $\frac{(V_d - V_o) \delta T_p}{L} = \frac{\gamma T_p V_o}{L}$

$$t_2 = \gamma T_p$$

Current fall time ratio  $\gamma = \delta \frac{(V_d - V_o)}{V_o}$

$$V_o = \frac{\delta}{\delta + \gamma} V_d$$

# Discontinuous current operation

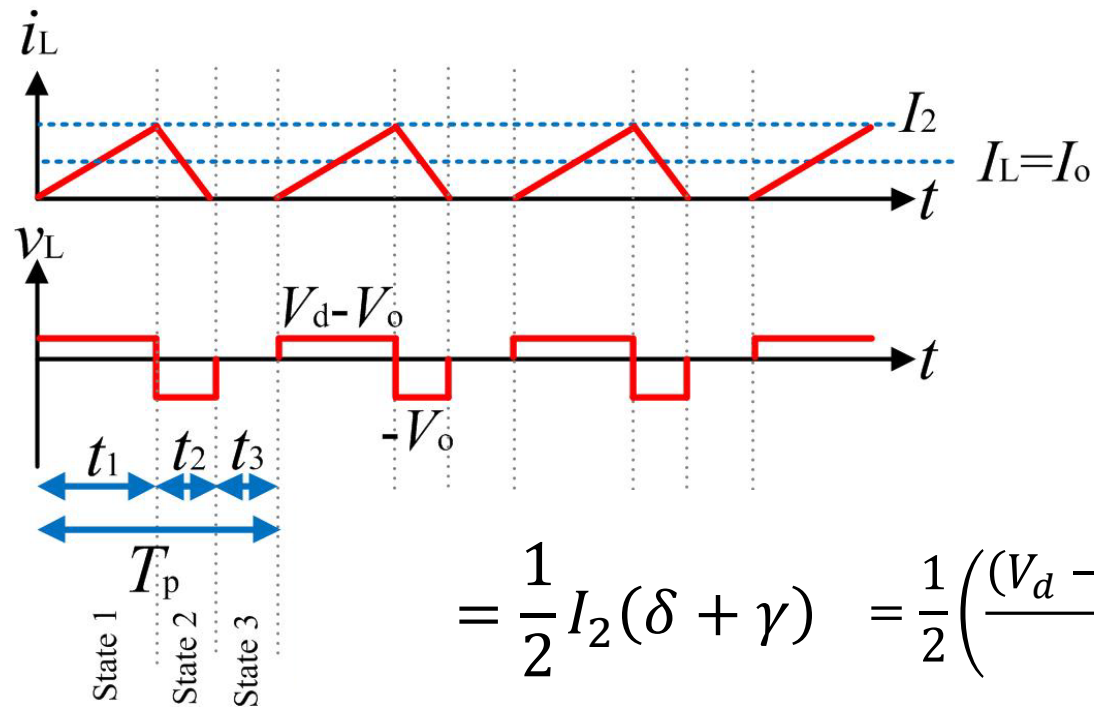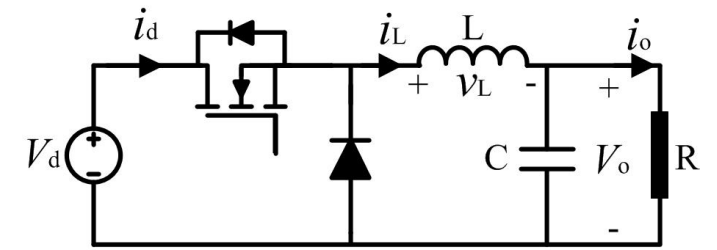

Average inductor current

$$I_L = \frac{1}{T_p} \int_0^{T_p} i_L dt = \frac{1}{T_p} \left[ \frac{1}{2} \delta T_p I_2 + \frac{1}{2} \gamma T_p I_2 \right]$$

$$= \frac{1}{2} I_2 (\delta + \gamma) = \frac{1}{2} \left( \frac{(V_d - V_o) \delta T_p}{L} \right) \left( \delta + \delta \frac{(V_d - V_o)}{V_o} \right) = \frac{\delta^2 T_p V_d (V_d - V_o)}{2 L V_o}$$

Output current

$$I_o = I_L = \frac{\delta^2 T_p V_d (V_d - V_o)}{2 L V_o}$$

$$t_1 = \delta T_p$$


$$t_2 = \gamma T_p$$

$$V_o = \frac{\delta}{\delta + \gamma} V_d$$

# Step-down (Buck) converter


Continuous current operation	Boundary Condition	Discontinuous current operation
$V_o = \delta V_d$	$V_o = \delta V_d$	$V_o = \frac{\delta}{\delta + \gamma} V_d$
$I_L = I_o = \frac{I_1 + I_2}{2}$	$I_{Lb} = \frac{(1 - \delta) \delta T_p V_d}{2L}$ $I_{Lb} = I_{Lo}$	$I_L = \frac{\delta^2 T_p V_d (V_d - V_o)}{2L V_o}$ $I_L = I_o$

# Step-up (Boost) converter

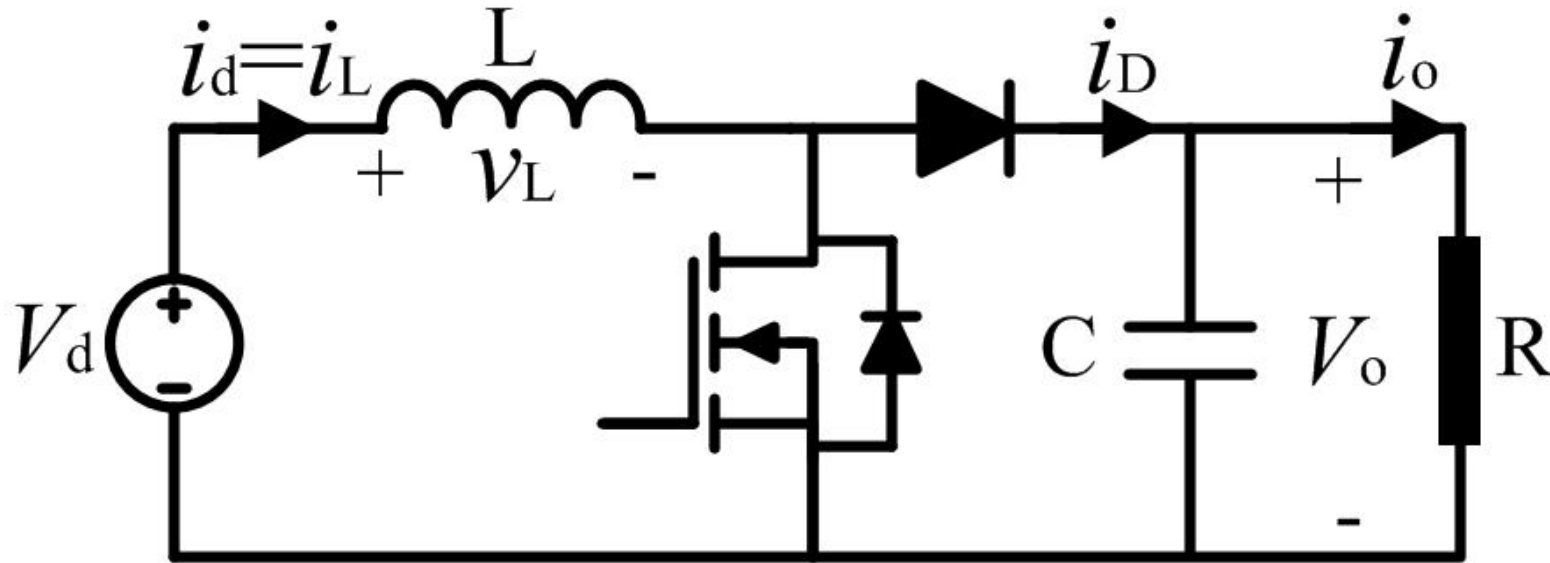


- Three states in operation
- Three modes of operation

# Three states in operation

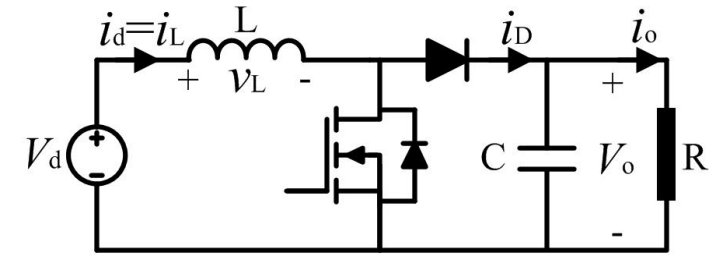


State 1

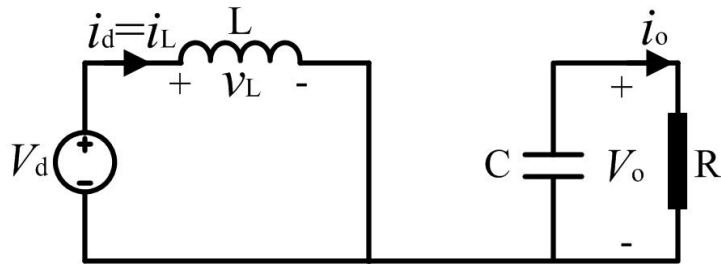


- MOSFET ON
- Diode reverse biased
- Inductor stores energy

State 2

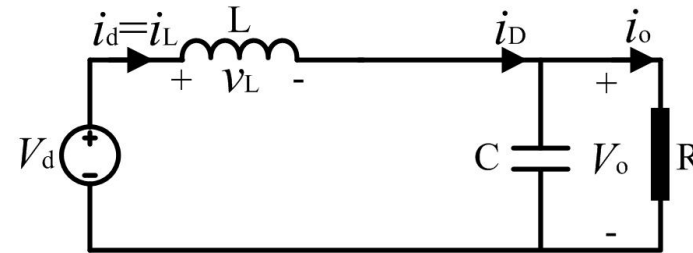

- MOSFET OFF
- Inductor discharges energy through diode

State 3

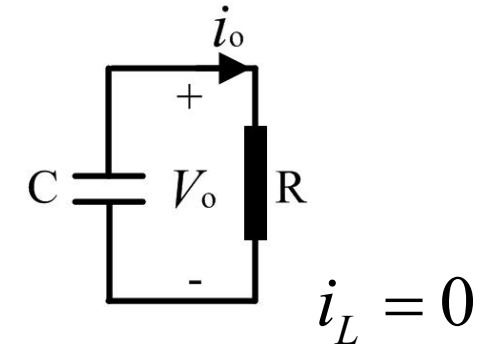



- MOSFET OFF
- Stored energy (inductor) fully discharged
- Diode reverse biased

# Three operation modes

---

- |  |                |
|--|----------------|
| 1. Continuous current operation                                    | State 1 & 2    |
| 2. Boundary between continuous and discontinuous current operation | State 1 & 2    |
| 3. Discontinuous current operation                                 | State 1, 2 & 3 |

# Continuous current condition

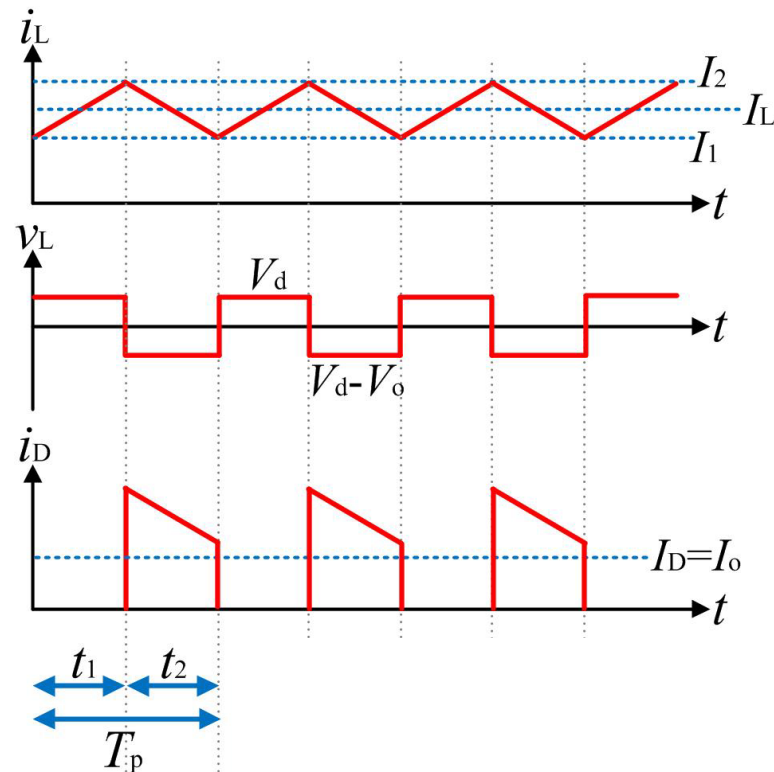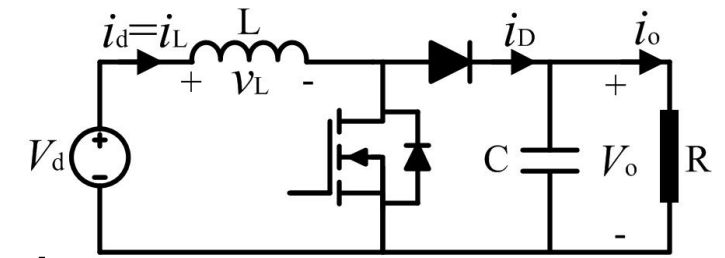

$\delta$ : Duty ratio

$T_p$ : Period

$t_1 = \delta T_p$  On time

$t_2 = (1 - \delta) T_p$  Off time

**Inductor voltage  $v_L$**

$V_d$

State 1 (On state)

$V_d - V_o$

State 2 (Off state)


**Inductor current  $i_L$**   $I_L$ : Average inductor current

$I_1$ : Maximum current  $I_2$ : Minimum current



**Diode current  $i_d$**

$I_D$ : Average diode current

$I_o = I_D$

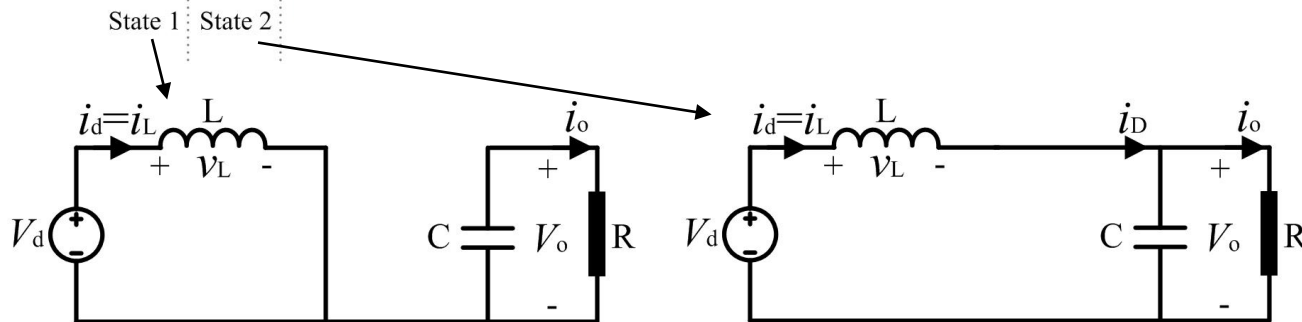

# Continuous current condition

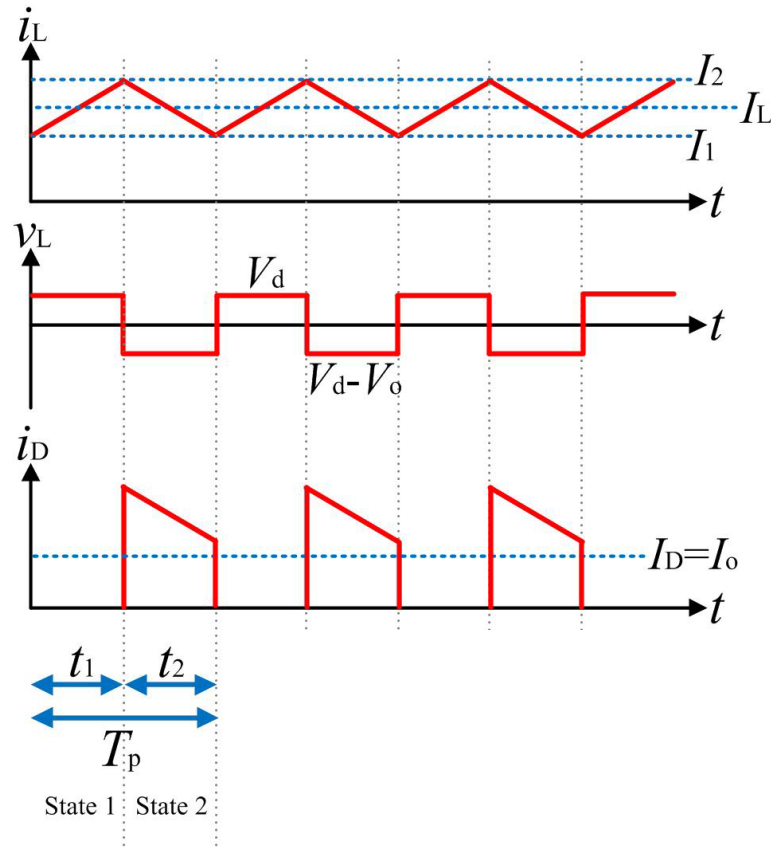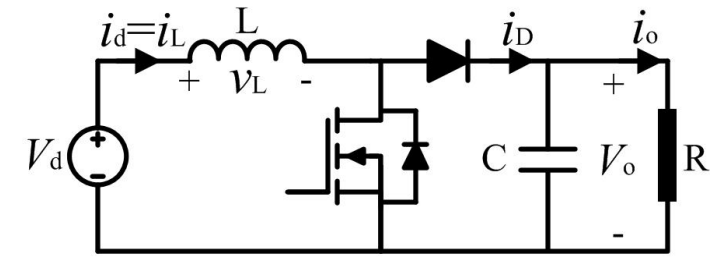

At periodic steady-state, the average inductor voltage is zero.

$$V_L = \frac{1}{T_p} \int_0^{T_p} v_L dt = 0$$

$$\frac{1}{T_p} [V_d t_1 + (V_d - V_o) t_2] = 0$$

$$\frac{1}{T_p} [V_d \delta T_p + (V_d - V_o)(1 - \delta) T_p] = 0$$

$$t_1 = \delta T_p$$



$$t_2 = (1 - \delta) T_p$$

$$V_o = \frac{V_d}{1 - \delta}$$

$$I_L = \frac{I_1 + I_2}{2}$$



# Boundary condition

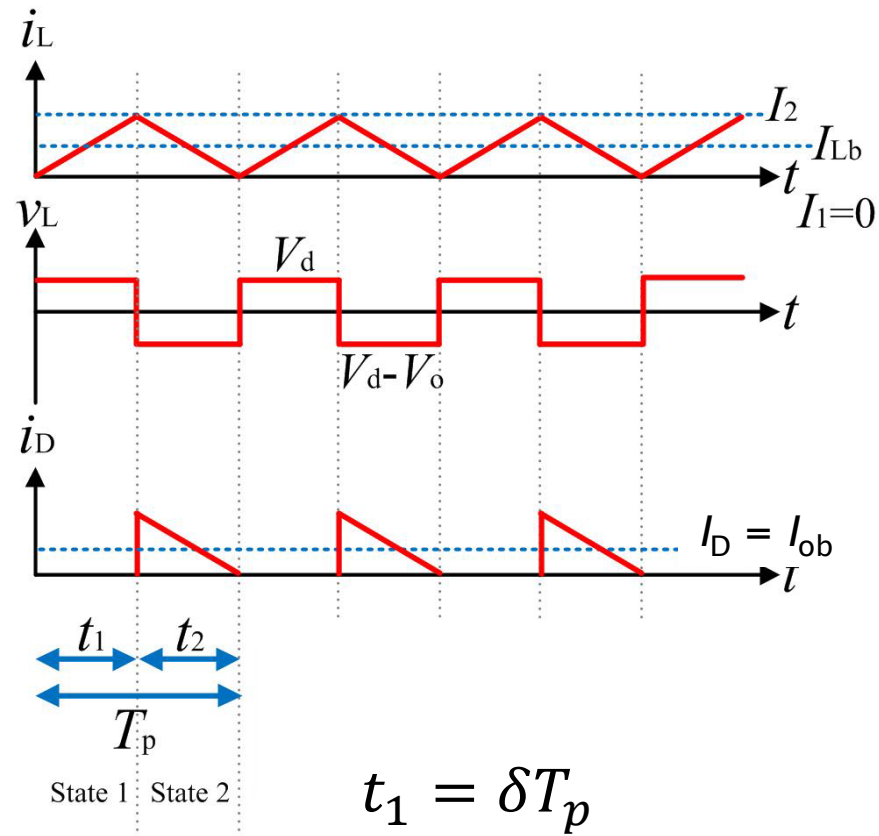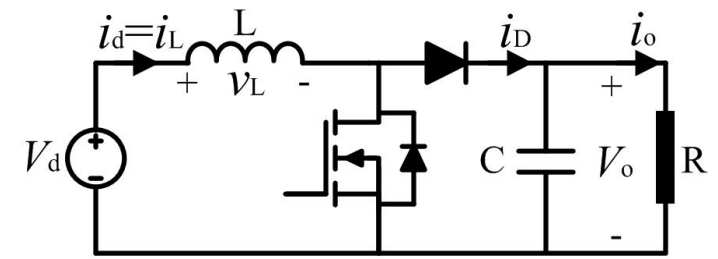

$$t_1 = \delta T_p$$

$$t_2 = (1 - \delta) T_p$$

$$V_d = (1 - \delta) V_o$$

From  $v_L = L \frac{di_L}{dt}$  at State 1 (On state),

$$V_d = L \frac{I_2}{t_1} \quad I_2 = \frac{V_d \delta T_p}{L}$$

$$I_{Lb} = \frac{I_1 + I_2}{2} = \frac{I_2}{2} = \frac{V_d \delta T_p}{2L} = \frac{(1 - \delta) V_o \delta T_p}{2L}$$


Assume efficiency = 100%

$$P_{in} = P_{out} \quad V_d I_d = V_o I_{ob}, \quad I_d = I_{Lb}$$

$$I_{ob} = \frac{V_d I_{Lb}}{V_o} = (1 - \delta) I_{Lb} = \frac{(1 - \delta)^2 V_o \delta T_p}{2L}$$

Output current at the boundary condition

# Boundary condition

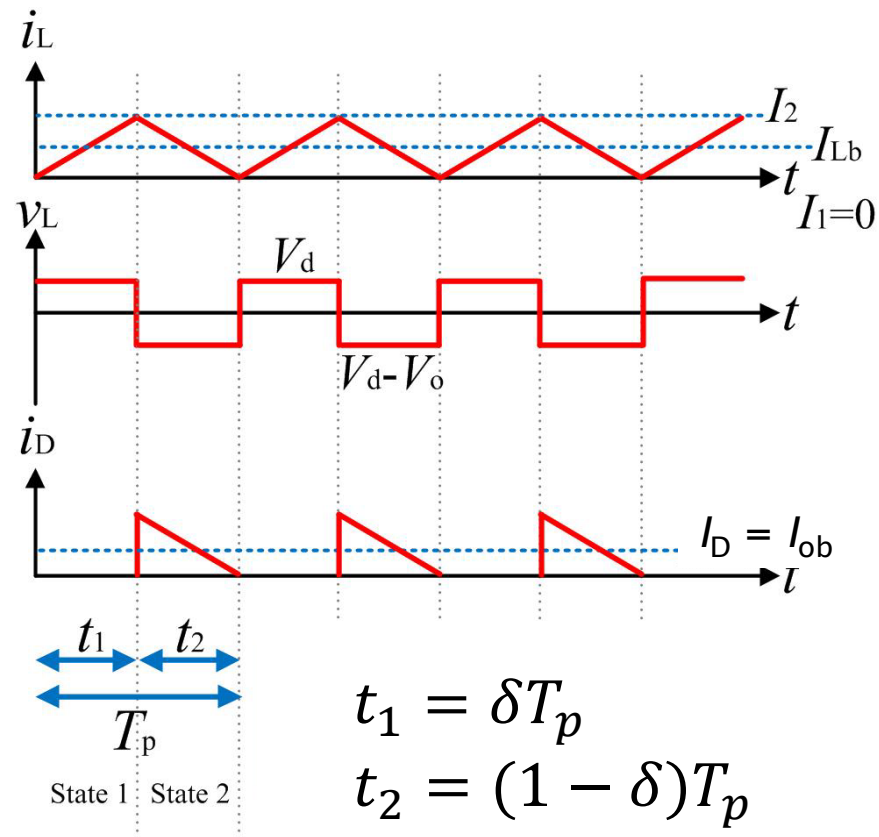


$$t_1 = \delta T_p$$

$$t_2 = (1 - \delta) T_p$$

$$V_d = (1 - \delta) V_o$$

$$I_2 = \frac{V_d \delta T_p}{L},$$

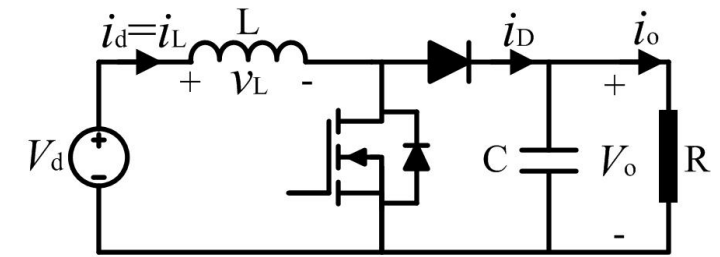

## Alternative derivation for $I_{ob}$



At periodic steady-state, the average capacitor current is zero. Hence, average diode current equal to average load current.

$$I_{ob} = I_D = \frac{1}{T_p} \int_0^{T_p} i_D dt = \frac{1}{T_p} \left[ \frac{1}{2} (1 - \delta) T_p I_2 \right]$$

$$= \frac{I_2 (1 - \delta)}{2}$$

$$= \frac{(1 - \delta)^2 V_o \delta T_p}{2L}$$

# Discontinuous current condition

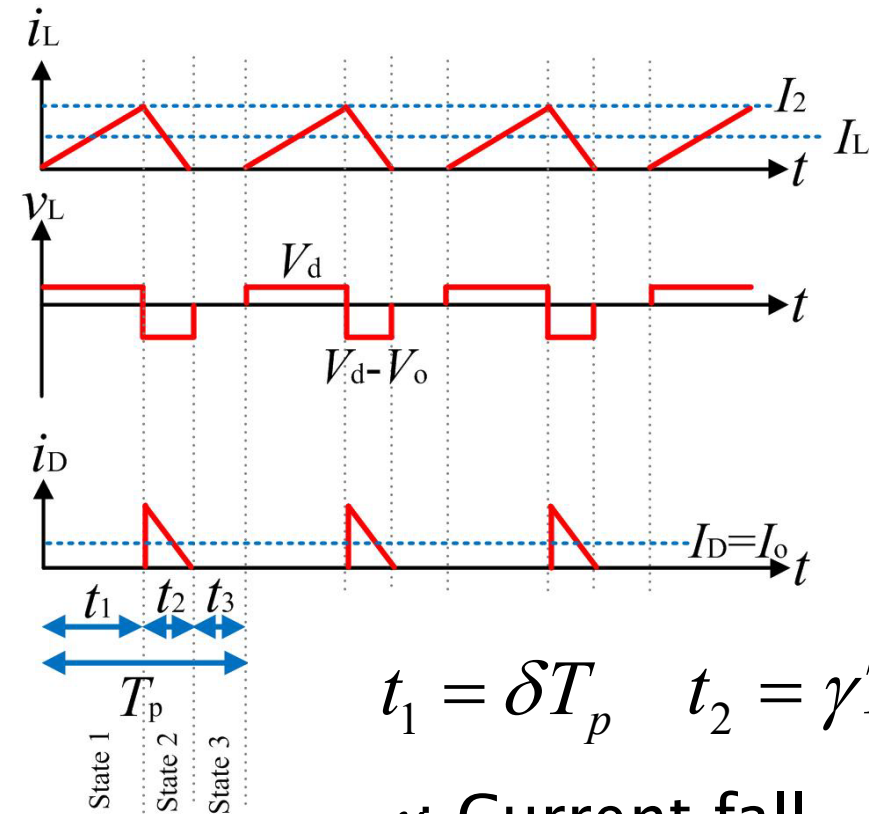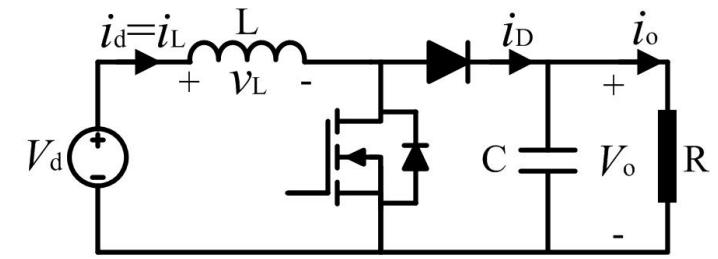

$$t_1 = \delta T_p \quad t_2 = \gamma T_p$$

$\gamma$ : Current fall  
time ratio

$t_3$ : Current off time

$$i_L = 0$$



$$V_L = \frac{1}{T_p} \int_0^{T_p} v_L dt = 0$$

$$\frac{1}{T_p} [V_d \delta T_p + (V_d - V_o) \gamma T_p] = 0$$

$$V_d \delta + V_d \gamma - V_o \gamma = 0$$

$$\frac{V_o}{V_d} = \frac{\delta + \gamma}{\gamma}$$

# Discontinuous current condition

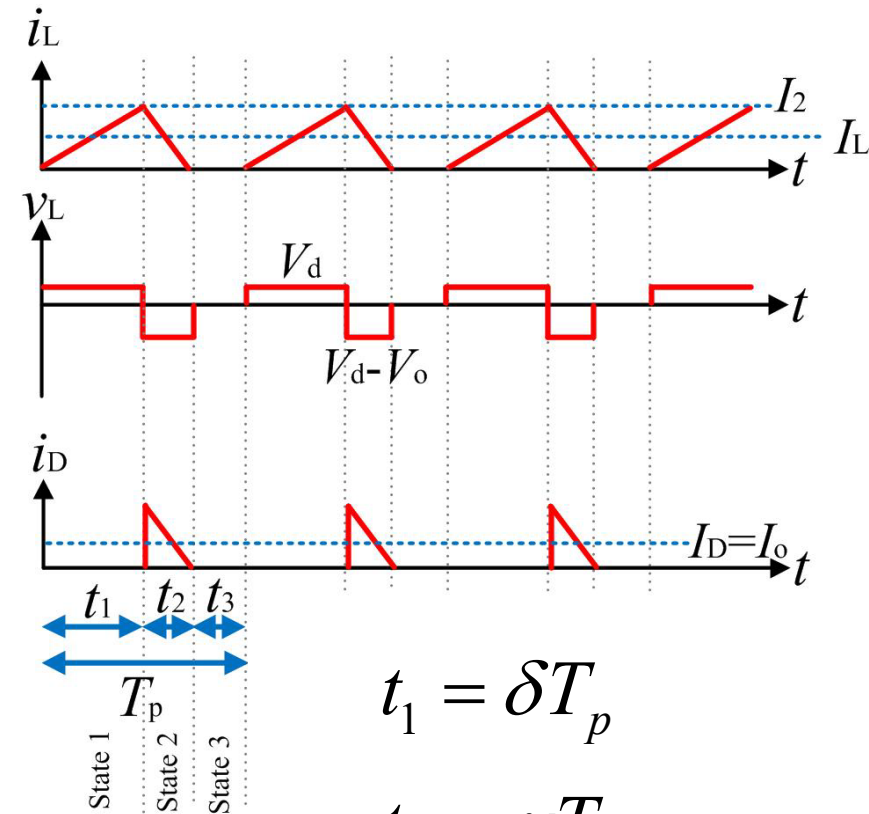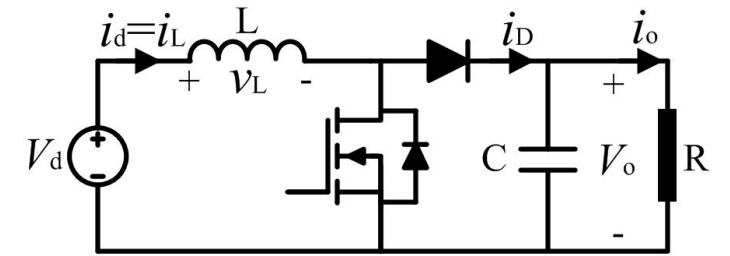

$i_L = 0$

$$t_1 = \delta T_p$$

$$t_2 = \gamma T_p$$

$$\frac{V_o}{V_d} = \frac{\delta + \gamma}{\gamma}$$

From  $v_L = L \frac{di_L}{dt}$  at State 1 (On state),

$$V_d = L \frac{I_2}{\delta T_p} \quad I_2 = \frac{\delta T_p V_d}{L}$$

From  $v_L = L \frac{di_L}{dt}$  at State 2 (Off state),


$$V_d - V_o = -L \frac{I_2}{\gamma T_p} \quad I_2 = \frac{-\gamma T_p (V_d - V_o)}{L}$$

By equalising  $I_2$ ,

$$\frac{\delta T_p V_d}{L} = \frac{-\gamma T_p (V_d - V_o)}{L}$$

Current fall time ratio  $\gamma = \frac{\delta V_d}{V_o - V_d}$

# Discontinuous current condition

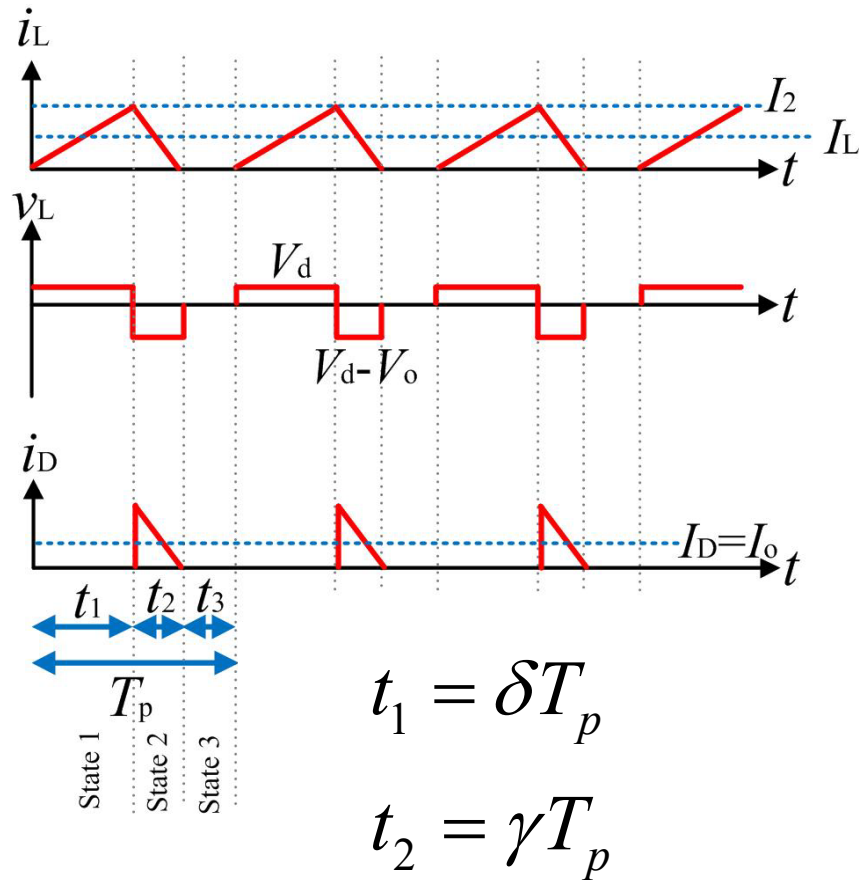

$$I_2 = \frac{\delta T_p V_d}{L} \quad \gamma = \frac{\delta V_d}{V_o - V_d}$$

Average inductor current

$$I_L = \frac{1}{T_p} \int_0^{T_p} i_L dt = \frac{1}{T_p} \left[ \frac{1}{2} \delta T_p I_2 + \frac{1}{2} \gamma T_p I_2 \right] = \frac{1}{2} (\delta + \gamma) I_2$$


$$= \frac{1}{2} (\delta + \gamma) \frac{\delta T_p V_d}{L} = \frac{1}{2} \left( \delta + \frac{\delta V_d}{V_o - V_d} \right) \frac{\delta T_p V_d}{L}$$

$$= \frac{\delta^2 T_p V_d V_o}{2L(V_o - V_d)}$$

Duty ratio

$$\delta = \sqrt{\frac{2L(V_o - V_d)I_L}{T_p V_d V_o}}$$

# Discontinuous current condition

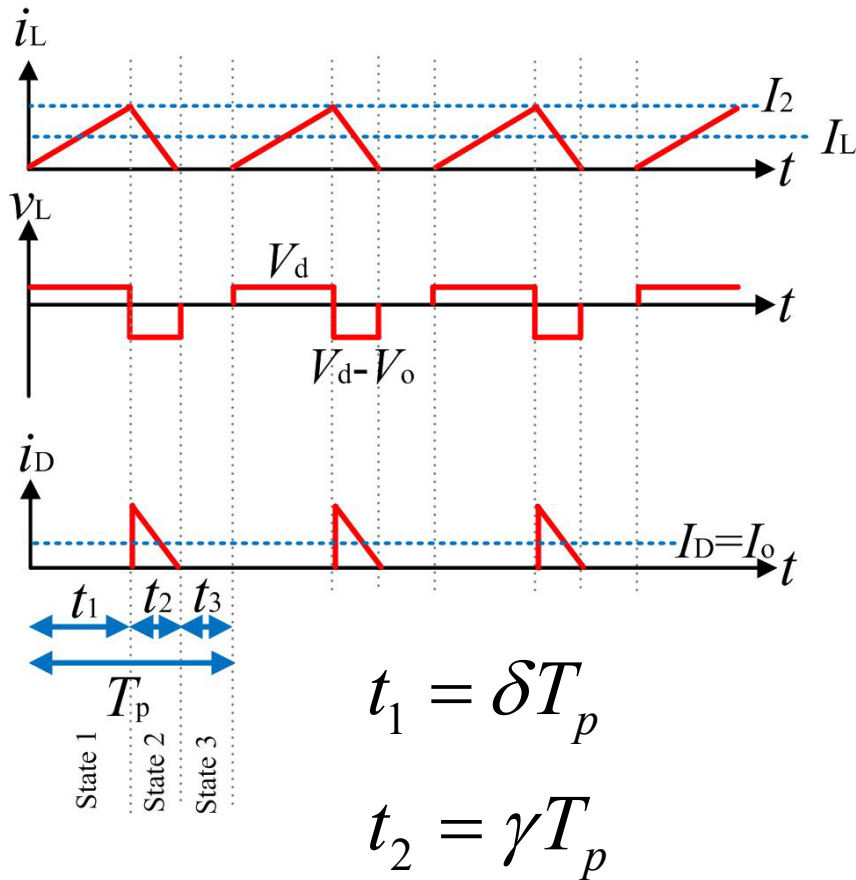

$$I_2 = \frac{\delta T_p V_d}{L} \quad \gamma = \frac{\delta V_d}{V_o - V_d}$$

At steady-state, average capacitor current is zero. Hence, average diode current equal to average load current.

$$I_o = I_D = \frac{1}{T_p} \int_0^{T_p} i_D dt = \frac{1}{T_p} \left[ \frac{1}{2} \gamma T_p I_2 \right] = \frac{1}{2} \gamma I_2,$$

$$= \frac{1}{2} I_2 \frac{\delta V_d}{V_o - V_d} = \frac{1}{2} \left( \frac{\delta V_d}{V_o - V_d} \right) \left( \frac{\delta T_p V_d}{L} \right)$$

$$= \frac{\delta^2 T_p V_d^2}{2L(V_o - V_d)}$$

Output current

# Summary – Step-up (Boost) converter

Continuous current operation	Boundary Condition	Discontinuous current operation
$V_o = \frac{V_d}{1 - \delta}$	$V_o = \frac{V_d}{1 - \delta}$	$\frac{V_o}{V_d} = \frac{\delta + \gamma}{\gamma}$
$I_L = \frac{I_1 + I_2}{2}$	$I_{Lb} = \frac{(1 - \delta)V_o \delta T_p}{2L}$ $I_{ob} = \frac{(1 - \delta)^2 V_o \delta T_p}{2L}$	$I_L = \frac{\delta^2 T_p V_d V_o}{2L(V_o - V_d)}$ $I_o = \frac{\delta^2 T_p V_d^2}{2L(V_o - V_d)}$



# Summary – DC-DC Converter

---

- DC-DC converters are power electronic circuits that convert a dc voltage to a different dc voltage level, often providing a regulated output.
- Step-down (Buck) converter and Step-up (Boost) converter have been analysed.