
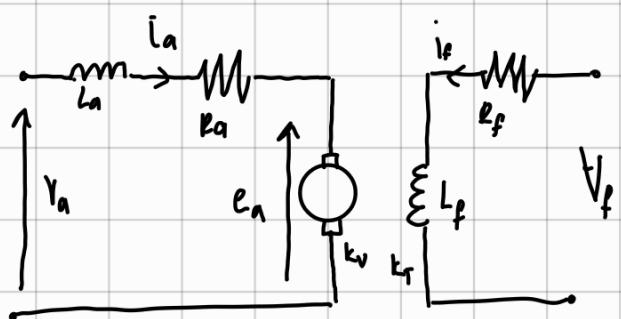


DC

## Four Quadrant

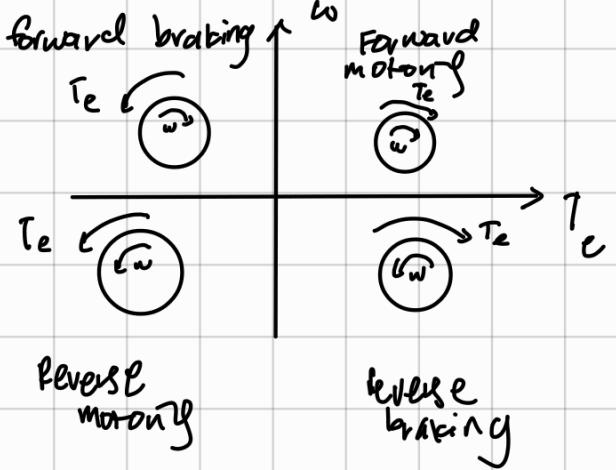

$$V_f = R_f i_f + L_f \frac{di_f}{dt} \quad V_a = R_a i_a + L_a \frac{di_a}{dt} + e_a$$

$$e_a = k_v \omega i_a$$

$$T_e = k_T i_f i_a \rightarrow \text{electromagnetic torque}$$


$$= J \frac{d\omega}{dt} + B\omega + T_L \rightarrow \text{DC motor under electrical steady state}$$

$$= B\omega + T_L$$

$$V_p = \frac{2V_{pk}}{IT} \cos \alpha_f \rightarrow \text{single phase converter}$$
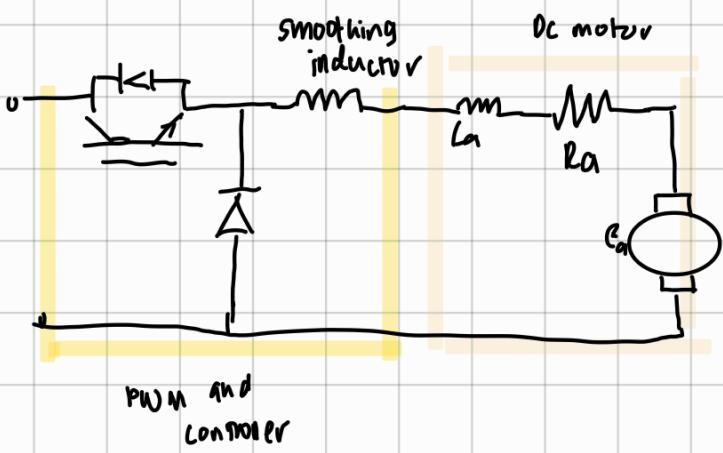
## Chopper control of DC machines

- refer to power electronic converter with PWM-operated (MOSFET) IGBT



$$V_{dc} = L \frac{di}{dt} + R_i + E$$

$$i_1(t) = I_1 e^{-\frac{R}{L}t} - \frac{(I_1 - V_{dc})}{R} \left[ 1 - e^{-\frac{R}{L}t} \right]$$

$$i_2(t) = I_2 e^{-\frac{R}{L}kT} - \frac{(I_2 - V_{dc})}{R} \left[ 1 - e^{-\frac{R}{L}kT} \right]$$


$$T_2 \neq T_3 : V_{dc}$$

$$-V_{dc} = L \frac{di}{dt} + R_i + E$$


$$P_{developed} = T_e \omega \quad \omega = \frac{V_a - R_a i_a}{k_v V_f / R_f}$$

$$\text{Speed regulation} = \frac{\omega_{no-load} - \omega_{full-load}}{\omega_{full-load}} \times 100\%$$

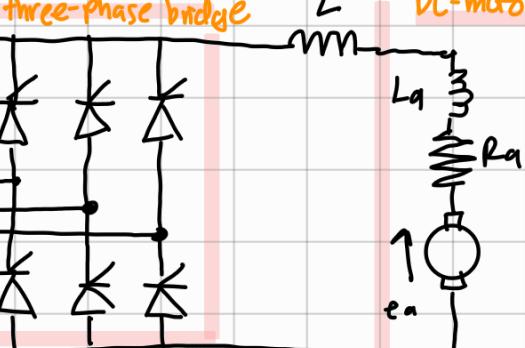DC motor drive based on 3-phase fully controllable bridge



Single-phase bridge

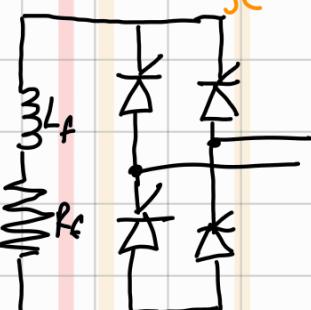

$$V_{an} = V_{pc} \sin(\omega t)$$

$$V_{bn} = V_{pc} \sin(\omega t - 2\pi/3)$$


$$V_{cn} = V_{pc} \sin(\omega t + 2\pi/3)$$

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_{pc} \sin(\omega t + \pi/6)$$

$$V_{bc} = \sqrt{3} V_{pc} \sin(\omega t - \pi/2)$$

$$V_{ca} = \sqrt{3} V_{pc} \sin(\omega t + \pi/2)$$

# Regenerative Braking

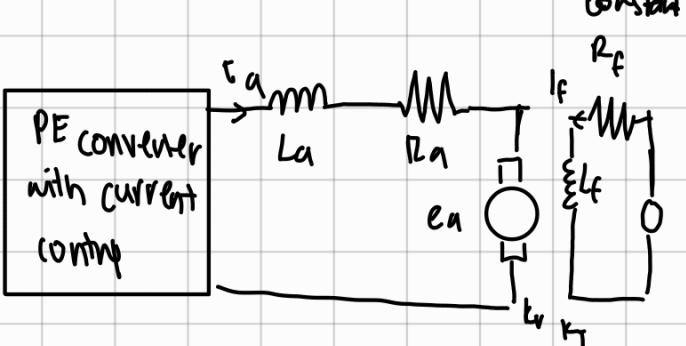

$$v_m = K_c \omega_m + i_a R_a + L_a \frac{di_a}{dt}$$

$$\begin{aligned} T &= K_T i_a \quad \text{speed rotation} \\ &= J \frac{d\omega}{dt} + B \omega_m \end{aligned}$$

Copper loss at the armature

$$P_d = i_a^2 R_a$$

The braking current is controlled by the DC drive to remain constant ( $I_R$  negative)

$$V_m(t) = K_c \omega_m(t) + I_R R_a + 0$$

windage fraction = 0, no load connected with constant braking armature current

Torque constant during braking period  
deceleration constant  $\alpha$

$$\omega_m(t) = \left[ 1 - \frac{t}{t_2} \right] \omega_{int}$$


$$\text{initial } t=0 \quad \omega_{int} = \omega_m(0)$$

Calculated regenerated energy

$$t=0 \rightarrow t=t_0$$

$$\begin{aligned} E_{regen} &= t_0 \left[ \frac{K_c \omega_{int} I_R}{2} + \frac{I_R^2 R_a}{2} \right] \\ &= -J \omega_{int} \left[ 1 + \frac{I_R R_a}{K_c \omega_{int}} \right] \left[ \frac{K_c \omega_{int} I_R}{2} + \frac{I_R^2 R_a}{2} \right] \\ &= -\frac{J \omega_{int}}{K_c} \left[ \frac{K_c \omega_{int}}{2} + \frac{I_R^2 R_a}{2 K_c \omega_{int}} + \frac{I_R R_a}{2} \right] \end{aligned}$$

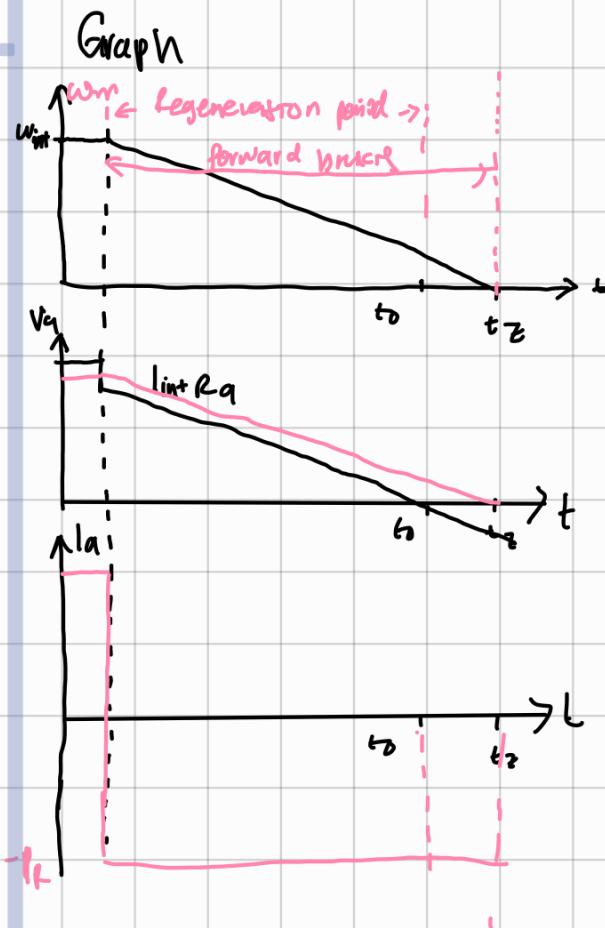Based on assumptions,  
• constant braking current  
• no load torque and  
no friction.



Prior to deceleration from  $\omega_{int}$ ,

$$V_m(t) = K_c \left[ 1 - \frac{t}{t_2} \right] \omega_{int} + I_R R_a$$

Immediately following the application of the negative braking current the terminal voltage drop to ( $K_c \omega_{int} + I_R R_a$ ,  $I_R$  negative)

$K_c \omega_{int}$  = initial back EMF

$V_m \downarrow$ ,  $\omega_m \downarrow$  due to EMF  $\downarrow$  until zero

$$t_0 = t_2 \left[ 1 + \frac{I_R R_a}{K_c \omega_{int}} \right]$$

$$\begin{aligned} E_{regen} &= \int_0^{t_0} V_m(t) I_R dt \\ &= \int_0^{t_0} \left[ \frac{-K_c \omega_{int} t + K_c \omega_{int} + I_R R_a}{t_2} \right] I_R dt \\ &= t_0 \left[ \frac{K_c \omega_{int} I_R}{2} + \frac{I_R^2 R_a}{2} \right] \end{aligned}$$

$$\text{Braking Torque, } T_{braking} = K_T I_R = J \alpha \quad \alpha = \frac{K_T I_R}{J}$$

$$\text{Deceleration: } \alpha = \frac{\omega_{int}}{t_2}$$

$$\begin{aligned} K_T I_R &= -\frac{\omega_{int}}{t_2} \\ t_2 &= -\frac{\omega_{int}}{K_T I_R} \end{aligned}$$

Relationship between  $t_0$  and  $t_2$

$$t_0 = -J \omega_{int} \left[ 1 + \frac{I_R R_a}{K_c \omega_{int}} \right]$$

# AC induction motor drives

2 categories: wound-rotor type & squirrel cage type


Synchronous speed

$$\omega_s = \frac{\omega}{p}$$

$$= \frac{\pi f}{p}$$

$$p = \text{pole pairs} = p/2$$

$$f = \text{supply frequency}$$

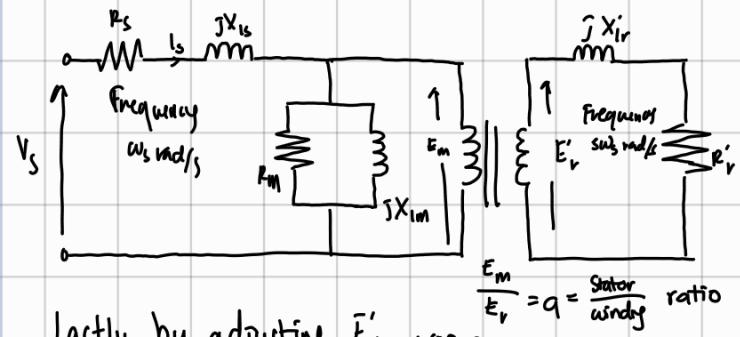

$$\text{sip of the motor, } s = \frac{\omega_s - \omega_m}{\omega_s}$$

$$\text{motor speed, } \omega_m = \omega_s (1-s)$$

$$\text{stator phase voltage } v_s = \sqrt{v_{pk}} \sin \omega_s t$$

produces steady-state magnetic flux linkage  $\phi(t)$  in the rotor at a given  $\omega_m$ :


$$\phi(t) = \phi_{pk} \cos(\omega_m t + \delta - \omega_s t)$$

Induced back EMF at one phase of the rotor windings with equivalent N<sub>r</sub> turns ( $\omega_s$  &  $\omega_m$  constant)

$$\begin{aligned} e_r(t) &= \frac{d(CN_r \phi(t))}{dt} = N_r \frac{d}{dt} (\phi_{pk} (\cos(\omega_m t + \delta - \omega_s t))) \\ &= -N_r \phi_{pk} (\omega_m - \omega_s) \sin((\omega_m - \omega_s)t + \delta) \\ &= -N_r \phi_{pk} (\omega_s - \omega_m) \sin[(\omega_s - \omega_m)t - \delta] \\ &= -N_r \phi_{pk} (\omega_s - \omega_s + \omega_m) \sin[(\omega_s - \omega_s + \omega_m)t + \delta] \\ &= -SN_r \phi_{pk} \omega_s \sin[(S\omega_m)t + \delta] \quad \begin{matrix} \delta = \text{relative position} \\ \text{of the rotor} \\ N_r = \text{num. of turns} \\ \text{on each rotor phase} \end{matrix} \\ &= -SE_{pk} \sin(S\omega_m t + \delta) \quad \begin{matrix} E_{pk} = N_r \phi_{pk} \omega_s \\ = \text{peak value of} \\ \text{the rotor induced} \\ \text{back EMF} \end{matrix} \\ &= S\sqrt{2} E_r \sin(S\omega_m t - \delta) \quad \begin{matrix} E_r = \text{RMS value of} \\ \text{the rotor induced} \\ \text{back EMF} \end{matrix} \end{aligned}$$

Lastly, by adjusting  $E_r'$ , using  $q$ .

Equivalent circuit.

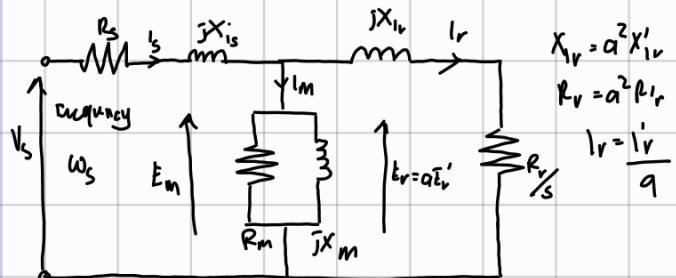

$V_s$  is rated phase to neutral rms voltage of the stator.

All of the reactance are at rated frequency.

(power transferred from stator to rotor)

$$\text{Air gap power, } P_g = 3I_r^2 \frac{R_r}{s}$$

$$\text{Stator copper loss, } P_{scloss} = 3I_s^2 R_s$$

$$\text{Rotor copper loss, } P_{rlloss} = 3I_r^2 R_r$$

$$\text{Core loss, } P_{core-loss} = \frac{3E_m^2}{R_m} \approx \frac{3V_s^2}{R_m}$$


Total input active power

$$P_{in} = 3I_s^2 I_s \cos \theta_m$$

$\theta_m$  = phase angle

$$= P_{core-loss} + P_{scloss} + P_g$$

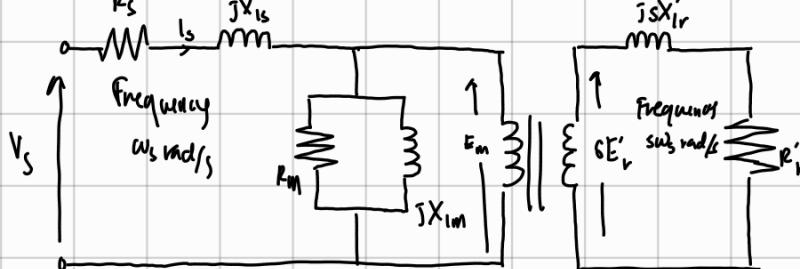Circuit of transformer model of an induction motor



Rotor current in rms phasor:

$$I_r' = \frac{SE_r'}{R_r' + jS X_{ir}'} = \frac{E_r'}{\frac{R_r'}{s} + jX_{ir}'}$$

$$P_{mech} = P_g - P_{scloss}$$

$$= 3I_r^2 \frac{R_r}{s} - 3I_r^2 R_r$$

$$= 3I_r^2 R_r \frac{(1-s)}{s}$$

$$= P_g (1-s)$$

$$P_{out} = P_{mech} - P_{notool}$$


efficiency

$$\eta = \frac{P_{mech}}{P_{in}} = \frac{P_{mech}}{P_{core-loss} + P_{scloss} + P_g}$$

$$P_g \gg P_{core-loss}, P_g \gg P_{scloss}$$


$$\eta \approx \frac{P_{mech}}{P_{in}} = \frac{P_g (1-s)}{P_g}$$

$$= 1-s$$

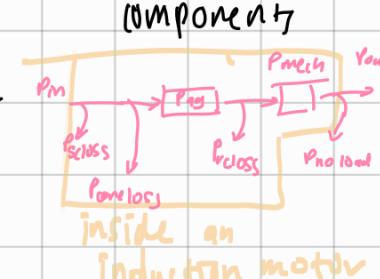



$$\begin{aligned}
 V_{TH} &= \frac{jX_m}{R_s + jX_{ls} + jX_m} V_s \\
 &= \frac{X_m}{\sqrt{R_s^2 + (X_m + X_{ls})^2}} V_s \quad X_m \gg X_{ls} \\
 &\quad (X_m + X_{ls}) \gg R_s \\
 &\approx \frac{X_m^2 R_s}{(X_m + X_{ls})^2} + j \frac{R_s^2 X_m + X_m X_{ls} (X_m + X_{ls})}{(X_m + X_{ls})^2} \\
 &= \frac{X_m^2 R_s}{(X_m + X_{ls})^2} + j \left( R_s \frac{R_s X_m}{(X_m + X_{ls})^2} + \frac{X_m X_{ls}}{X_m} \right) \\
 &= \frac{X_m^2 R_s}{(X_m + X_{ls})^2} + j X_{ls} \\
 &= R_{TH} \left[ \frac{X_m}{X_m + X_{ls}} \right]^2 + j X_{ls} \\
 &= R_{TH} + j X_{TH} \quad (\text{zero})
 \end{aligned}$$

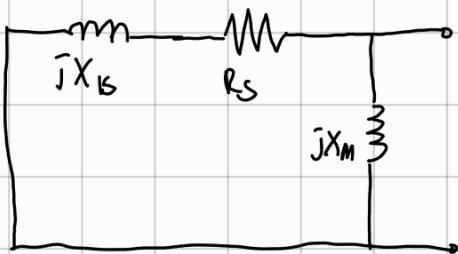

ASSUME  
 $X_m \gg X_{ls}$   
 $X_m + X_{ls} \gg R_s$

$$Z_{TH} = \frac{jX_m(R_s + jX_{ls})}{(R_s + j(X_m + X_{ls}))}$$


$$\begin{aligned}
 &= \frac{jX_m R_s - X_m X_{ls}}{R_s + j(X_m + X_{ls})} \frac{(R_s - j(X_m + X_{ls}))}{(R_s - j(X_m + X_{ls}))} \\
 &= \frac{jX_m R_s^2 + X_m R_s (X_m + X_{ls}) - R_s X_m X_{ls} + jX_m X_{ls} (X_m + X_{ls})}{R_s^2 + (X_m + X_{ls})^2}
 \end{aligned}$$

$$= \frac{j(X_m R_s^2 + X_m X_{ls} (X_m + X_{ls})) + X_m R_s (X_m + X_{ls}) - R_s X_m X_{ls}}{R_s^2 + (X_m + X_{ls})^2}$$

$$= \frac{j(X_m (R_s^2 + X_{ls} (X_m + X_{ls}))) + X_m R_s (X_m + X_{ls})}{R_s^2 + (X_m + X_{ls})^2}$$

$$= \frac{jX_m (R_s^2 + X_{ls} (X_m + X_{ls})) + X_m^2 R_s}{R_s^2 + (X_m + X_{ls})^2}$$
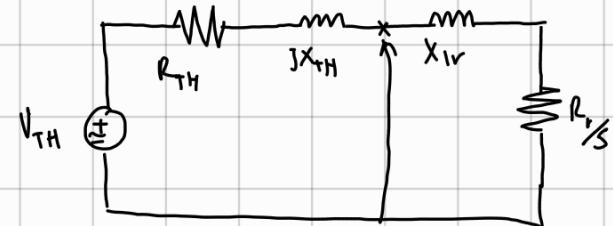
$$= \frac{X_m^2 R_s}{R_s^2 + (X_m + X_{ls})} + \frac{jX_m (R_s^2 + X_{ls} (X_m + X_{ls}))}{R_s^2 + (X_m + X_{ls})^2}$$



$$E = \frac{R_{ls}/s + jX_{lr}}{R_{TH} + \frac{R_{ls}}{s} + j(X_{TH} + X_{lr})} V_s$$

$$\begin{aligned}
 I_r &= \frac{V_{TH}}{R_{TH} + \frac{R_r}{s} + j(X_{TH} + X_{lr})} \\
 &= \frac{V_{TH}}{\sqrt{(\frac{R_r}{s} + j(X_{TH} + X_{lr}))^2 + (X_{TH} + X_{lr})^2}}
 \end{aligned}$$

Torque electromagnetic

$$\begin{aligned}
 T_e &= \frac{P_{Mech}}{\omega_m} = \frac{P_{ag}(1-s)}{(1-s)\omega_3} = \frac{P_{ag}}{\omega_3} \\
 &= \frac{3I_r^2 R_r}{s \omega_3} = \frac{3E^2 (\frac{R_r}{s})}{\omega_3 [(R_{ls})^2 + X_{lr}^2]}
 \end{aligned}$$

Or in Thermin

$$= \frac{3V_{TH}^2 (\frac{R_r}{s})}{\omega_3 [(R_{TH} + \frac{R_r}{s})^2 + (X_{TH} + X_{lr})^2]}$$

$$P_{\text{mech}} = P_{\text{ag}}(1-s)$$

$$= \frac{3V_{TH}^2 R_s(1-s)}{s[(R_{TH} + \frac{R_s}{s})^2 + (X_{TH} + X_{IR})^2]}$$

$$I_s = \frac{V_s - E}{R_s + jX_{IS}}$$

$$E = \left[ \frac{R_s/s + jX_{IR}}{R_{TH} + j(X_{TH} + X_{IR})} \right] V_{TH}$$

$$V_{TH} = \frac{jX_m V_s}{R_s + j(X_m + X_{IS})}$$

If stator frequency is changed from  $\omega_s$  to  $\beta\omega_s$   
where  $0 < \beta \leq 1$ .

$$T_e @ \beta\omega_s = \frac{3V_{TH}^2 (\frac{R_s}{s})}{\beta\omega_s [(R_{TH} + \frac{R_s}{s})^2 + (\beta X_{TH} + \beta X_{IR})^2]}$$

$$E_m = V_s - (R_s + jX_{IS}) I_s$$

$$= jX_m I_m$$

$$T_{\max} @ \beta\omega_s = \frac{3V_{TH}^2}{2\beta\omega_s [R_{TH} + \sqrt{R_{TH}^2 + (\beta X_{TH} + \beta X_{IR})^2}]}$$


$$V_s = jX_m I_m + (R_s + jX_{IS}) I_s$$
?

Assume  $R_{TH} \approx$  negligible

$$T_{\max} @ \beta\omega_s = \frac{3V_{TH}^2}{2\beta\omega_s (\beta X_{TH} + \beta X_{IR})}$$


$$= \frac{3}{2\omega_s (X_{TH} + X_{IR})} \left[ \frac{V_{TH}}{\beta} \right]^2$$

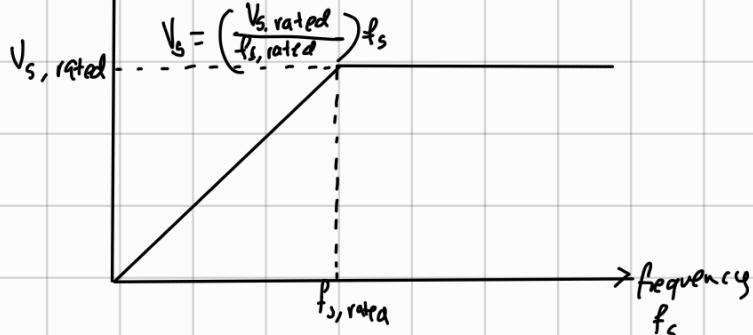Ideal  $V_s$  profile  
Phase voltage  
1 v rms  $V_s$





Yoshi

## Cycloconverter

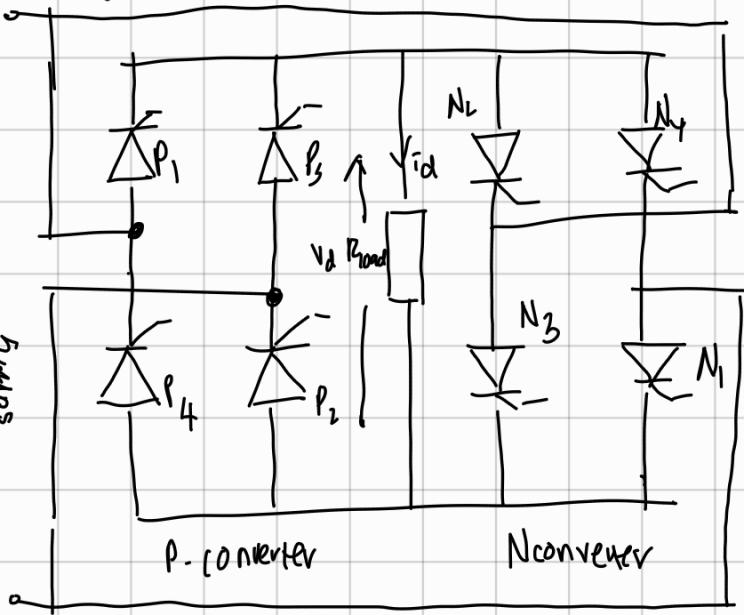


P-converter operates in rectification mode and produces positive voltage for first half cycle


## Step-down (Buck) converter

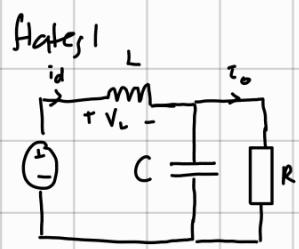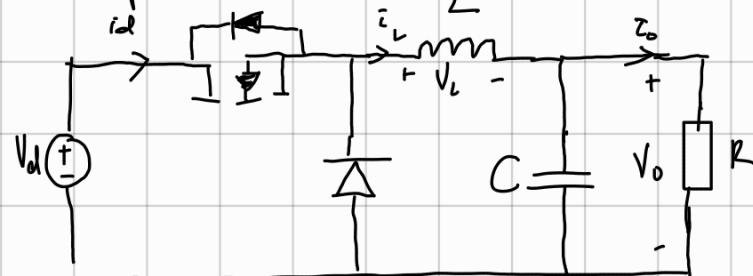

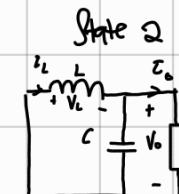MOSFET ON  
Diode reverse biased  
Inductor stores energy  
 $i_L = V_d - V_o$



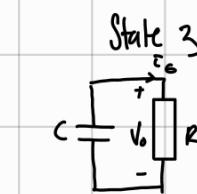
MOSFET OFF  
Inductor current freewheels through diode  
 $i_L = -V_o$




MOSFET OFF  
Stored energy (inductor) fully discharged  
 $i_L = 0$

## DC-DC converter


### linear voltage regulator

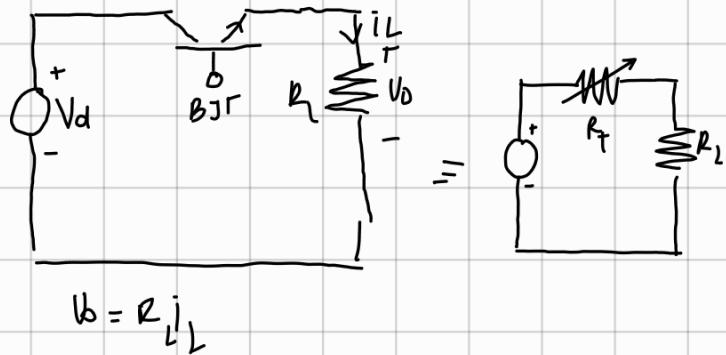

### Switching Converter (DC chopper)

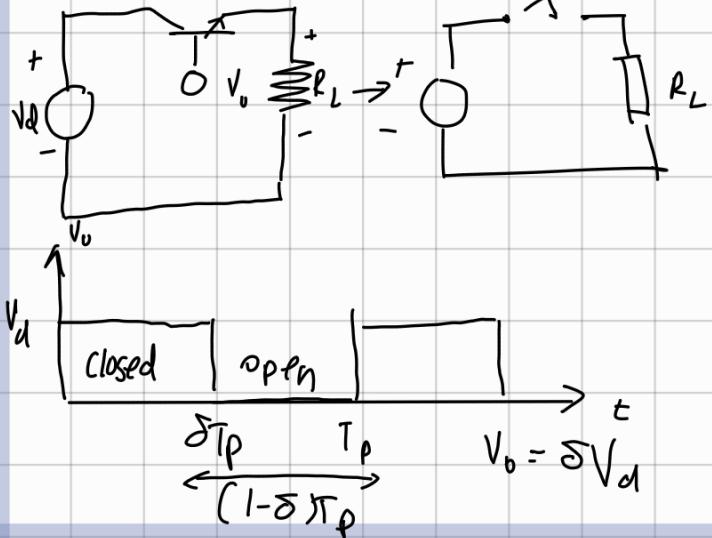

### b) Boundary condition

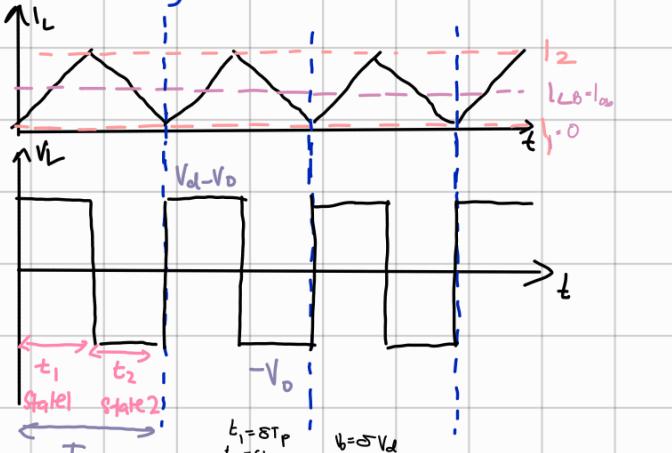


The min. inductor current  $i_L = 0$   
The average inductor current at boundary  $\frac{i_{L1} + i_{L2}}{2}$   
From  $i_L = L \frac{di_L}{dt}$  at State 1 (constant)  $i_{L1} = \frac{i_0}{\sigma T_p}$   
 $i_0 = \delta V_d$

$$i_{L0} = \frac{(V_d - V_o)\delta T_p}{2L} = \frac{(V_d - \delta V_d)\delta T_p}{2L} = \frac{(1 - \delta)\delta V_d T_p}{2L} = i_{L0}$$

- a)  $i_L \leq 2$
- b)  $i_L \geq 2$
- c)  $i_L < 2$

- Continuous current operation
- Boundary between continuous and discontinuous current operation
- Discontinuous current operation
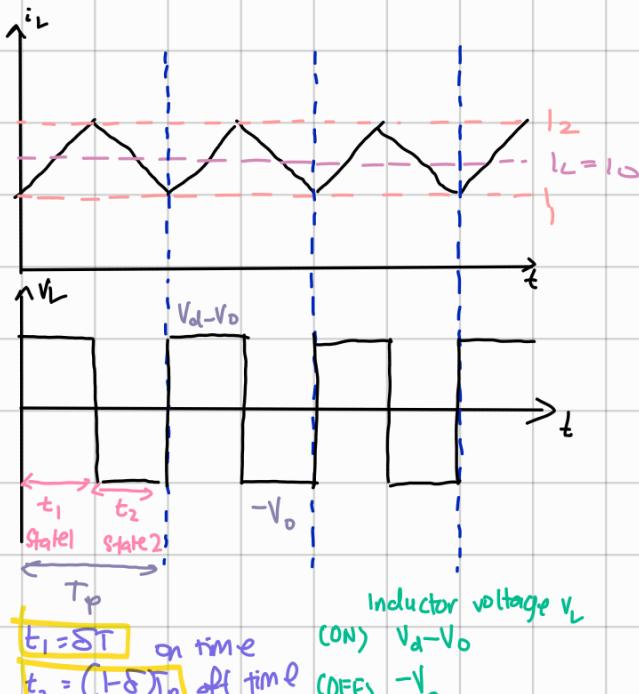
# a) Continuous Current Operation (State 1 & 2)



Inductor current  $i_L$

$$I_1 = \text{Max current}$$

$$I_2 = \text{Min current}$$

$$I_L = \text{Average inductor current}$$

At periodic steady-state, the average inductor voltage is 0.

$$V_L = \frac{1}{T_p} \int_0^{T_p} v_L dt = 0$$

$$\frac{1}{T_p} [(V_d - V_o)t_1 + (-V_o)t_2] = 0$$

$$\frac{1}{T_p} [(V_d - V_o)\delta T_p + (-V_o)(1-\delta)T_p] = 0$$

$$V_o = \delta V_d$$

Summary

Continuous current operation

$$V_o = \delta V_d$$

Boundary condition

$$V_o = \delta V_d$$

Discontinuous current operation

$$V_o = \frac{\delta}{\delta + \gamma} V_d$$

$$I_L = I_o = \frac{I_1 + I_2}{2}$$


$$I_{Lb} = \frac{(1-\delta)\delta T_p V_d}{2L}$$

$$I_{Lb} = I_o$$

$$I_L = \frac{\delta^2 T_p V_d (V_d - V_o)}{2L V_o}$$

$$I_L = I_o$$

# c) Discontinuous current operation

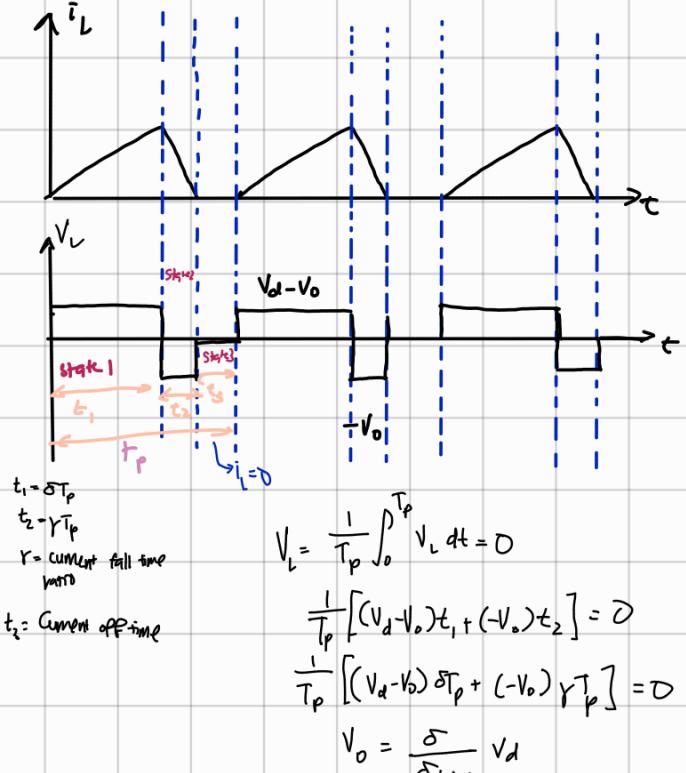

From  $v_L = L \frac{di_L}{dt}$  State 1 (ON state)

$$V_d - V_o = L \frac{i_2}{\delta T_p} \quad I_2 = \frac{(V_d - V_o)\delta T_p}{L}$$

$$\text{State 2 (Off state)} \quad -V_o = -L \frac{i_2}{\gamma T_p} \quad I_2 = \frac{\gamma T_p V_o}{L}$$

By equality  $I_2$

$$\frac{(V_d - V_o)\delta T_p}{L} = \gamma \frac{T_p V_o}{L}$$

Current fall time ratio

$$\gamma = \frac{\delta(V_d - V_o)}{V_o}$$

Average inductor current

$$I_L = \frac{1}{T_p} \int_0^{T_p} i_L dt$$


$$= \frac{1}{T_p} \left[ \frac{1}{2} \delta T_p I_2 + \frac{1}{2} \gamma T_p I_2 \right]$$

$$= \frac{I_2}{2} [\delta + \gamma] = \frac{1}{2} \left( \frac{(V_d - V_o)\delta T_p}{L} \right) \left( \delta + \gamma \frac{V_o}{V_d} \right)$$


$$= \frac{\delta^2 T_p V_d (V_d - V_o)}{2L V_o} = I_o$$

Output current


# Step-up (Boost) converter

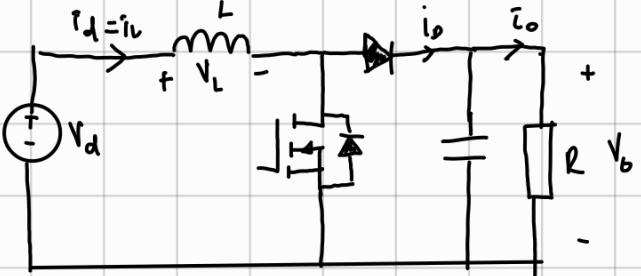


State 1

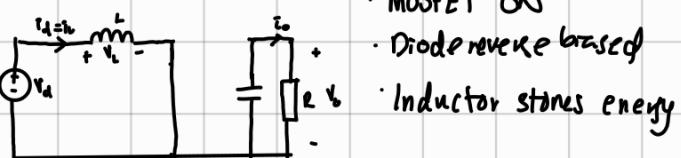

State 2

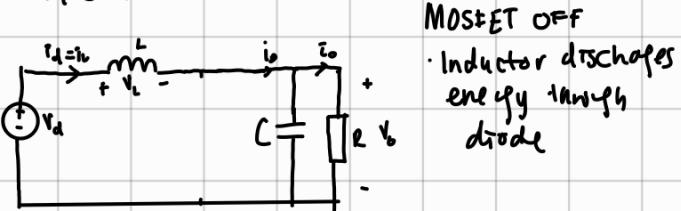


State 3

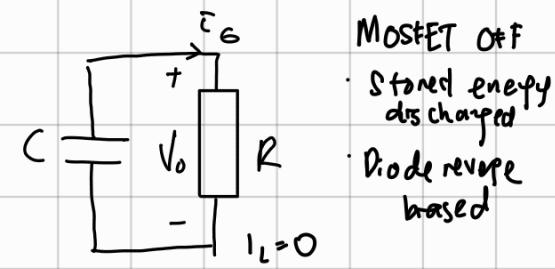

State

- $i_L \geq 0$  continuous current operation
- $i_L < 0$  boundary between continuous and discontinuous current operation
- $i_L = 0$  Discontinuous current operation

## a) Continuous current condition

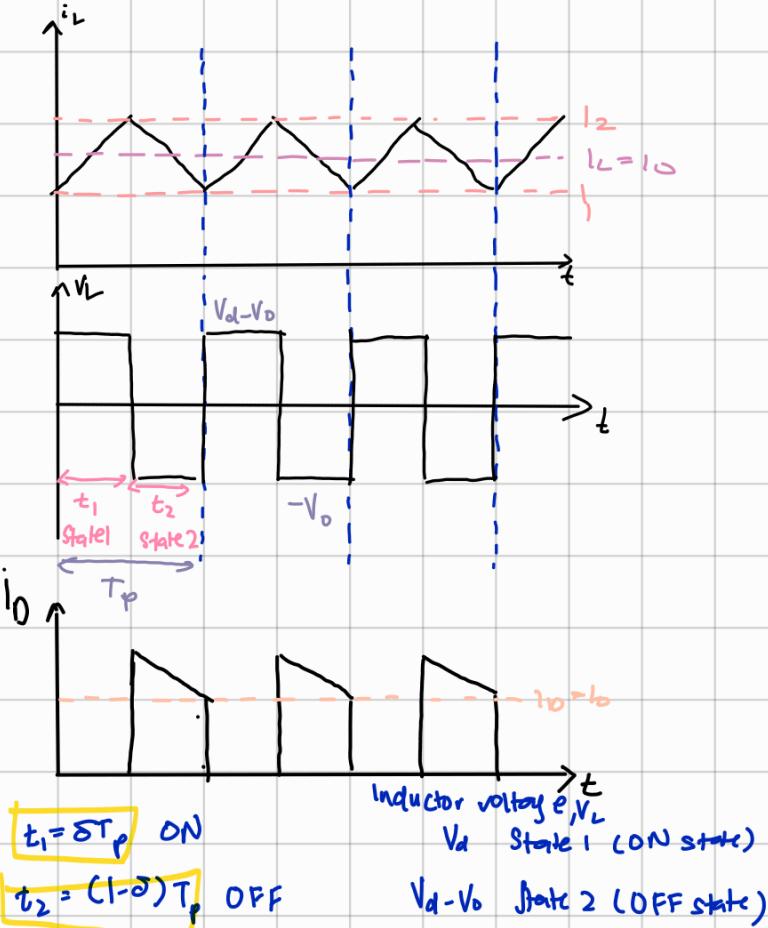

Inductor current  $i_L$        $I_L$ : Average inductor current

$I_1$  = Max. current       $I_2$  = Min. current

Diode current,  $i_D$

$$I_D = \text{Average diode current} \\ I_D = I_0$$

At periodic steady-state, the average inductor voltage = 0

$$V_L = \frac{1}{T_p} \int_{t_0}^{T_p} i_L dt = 0$$


$$\frac{1}{T_p} [V_d t_1 + (V_d - V_o) t_2] = 0$$

$$\frac{1}{T_p} [V_d \delta T_p + (V_d - V_o)(1 - \delta) T_p] = 0$$


$$V_o = \frac{V_d}{1 - \delta}$$

$$I_L = \frac{I_1 + I_2}{2}$$

## b) Boundary conditions

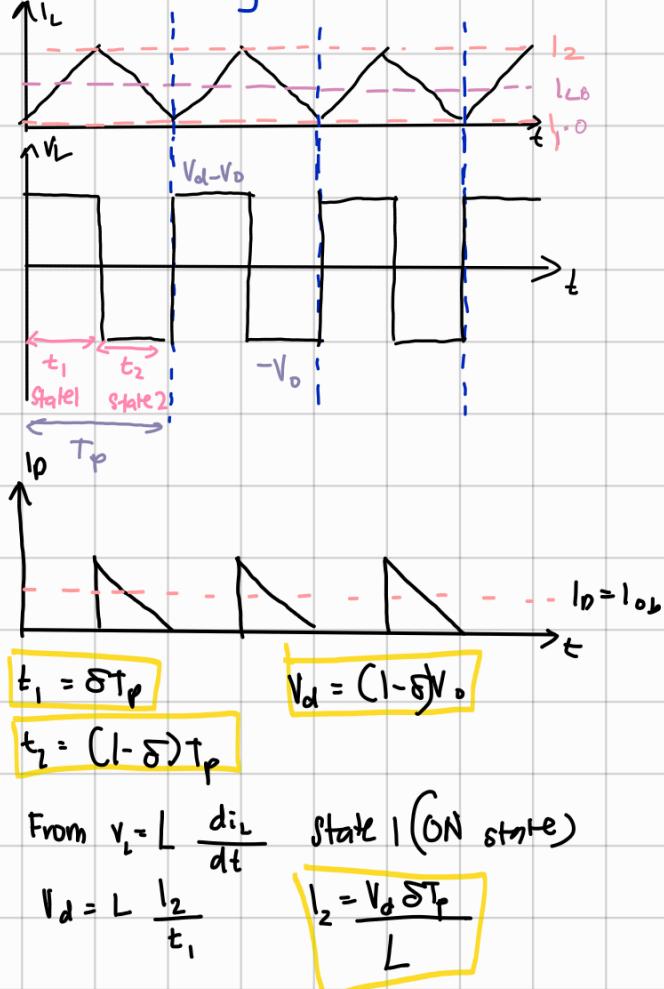

## c) Discontinuous condition

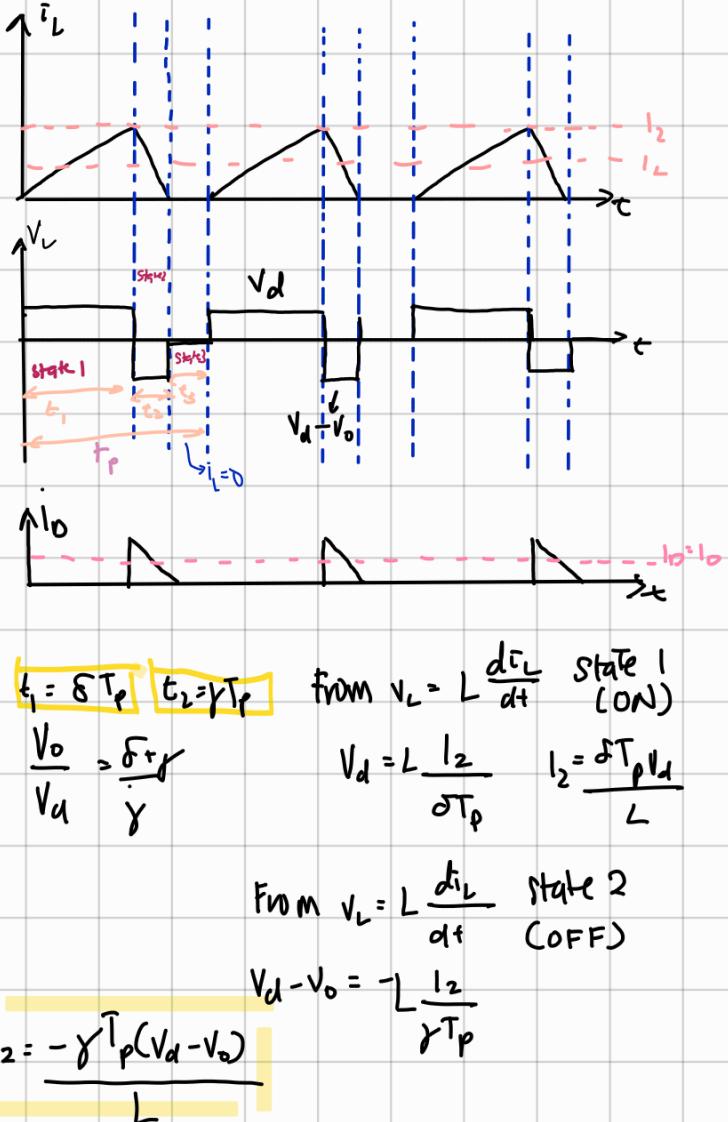

current fall time

$$\gamma = \frac{\delta V_d}{V_o - V_d}$$

Average inductor current

$$I_L = \frac{1}{T_p} \int_0^{T_p} i_L dt = \frac{1}{T_p} \left[ \frac{1}{2} \delta T_p I_2 + \frac{1}{2} \gamma T_p I_2 \right] = \frac{1}{2} (\delta + \gamma) I_2$$

$$= \frac{1}{2} (\delta + \gamma) \frac{\delta T_p V_d}{L} = \frac{1}{2} \left( \delta + \frac{\delta V_d}{V_o - V_d} \right) \frac{\delta T_p V_d}{L} = \frac{\delta^2 T_p V_d V_o}{2L(V_o - V_d)}$$

$$\text{Duty ratio } \delta = \frac{2\delta(V_o - V_d) I_L}{T_p V_d V_o} = I_L$$

Alternative derivation for  $I_{Lb}$

At period  $T_p$  steady-state, the average capacitor current = 0

Hence, average  $I_D = I_L$

$$I_{D\bar{b}} = I_D = \frac{1}{T_p} \int_0^{T_p} i_D dt = \frac{1}{T_p} \left[ \frac{1}{2} (1-\delta) T_p I_2 \right]$$

$$= \frac{I_2 (1-\delta)}{2}$$

$$I_{Lb} = \frac{(1-\delta)^2 V_o \delta T_p}{2L}$$

At steady state, average  $I_C = 0$ . Hence, average diode current =  $I_D = I_D$

$$I_D = I_D = \frac{1}{T_p} \int_0^{T_p} i_D dt = \frac{1}{T_p} \left[ \frac{1}{2} \gamma T_p I_2 \right] = \frac{1}{2} \gamma I_2$$

$$= \frac{1}{2} I_2 \frac{\delta V_d}{V_o - V_d} = \frac{1}{2} \left( \frac{\delta V_d}{V_o - V_d} \right) \left( \frac{\delta T_p V_d}{L} \right)$$

$$= \frac{\delta^2 T_p V_d^2}{2L(V_o - V_d)}$$

# Step-up Boost

Continuous

$$V_o = \frac{V_d}{1-\gamma}$$

Boundary

$$V_o = \frac{V_d}{1-\delta}$$

Discontinuous  
Current operation

$$\frac{V_o}{V_d} = \frac{\delta + \gamma}{\gamma}$$

$$I_L = \frac{I_1 + I_2}{2}$$

$$I_{Lb} = \frac{(1-\delta)V_o \delta T_p}{2L}$$

$$I_L = \frac{\delta^2 T_p V_d V_o}{2L(V_o - V_d)}$$

$$I_{ob} = \frac{(1-\delta)^2 V_o \delta T_p}{2L}$$

$$I_o = \frac{\delta^2 T_p V_d^2}{2L(V_o - V_d)}$$

# Step-down Buck

Continuous  
current  
operation

$$V_o = \delta V_d$$

Boundary  
condition

$$V_o = \delta V_d$$

Discontinuous  
current operation

$$V_o = \frac{\delta}{\delta + \gamma} V_d$$

$$I_L = I_o = \frac{I_1 + I_2}{2}$$

$$I_{Lb} = \frac{(1-\delta)\delta T_p V_d}{2L}$$

$$I_L = \frac{\delta^2 T_p V_d (V_d - V_o)}{2L V_o}$$

$$I_{Lb} = I_o$$

$$I_L = I_o$$

