

# ELEC2208 Power Electronics and Drives


## Tutorial 1 - Thyristors

Yoshi Tsuchiya  
Smart Electronic Materials and Systems (SEMS) Group  
[yt2@ecs.soton.ac.uk](mailto:yt2@ecs.soton.ac.uk)  
59/4219
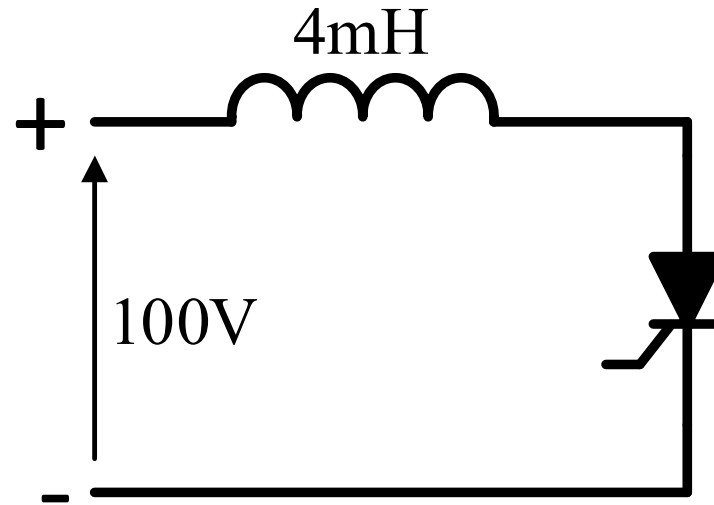
# Question 1

---


If the latching current of the thyristor in the circuit shown is 4 mA, determine the minimum width of the gating pulse required to turn on the thyristor.




# Revision
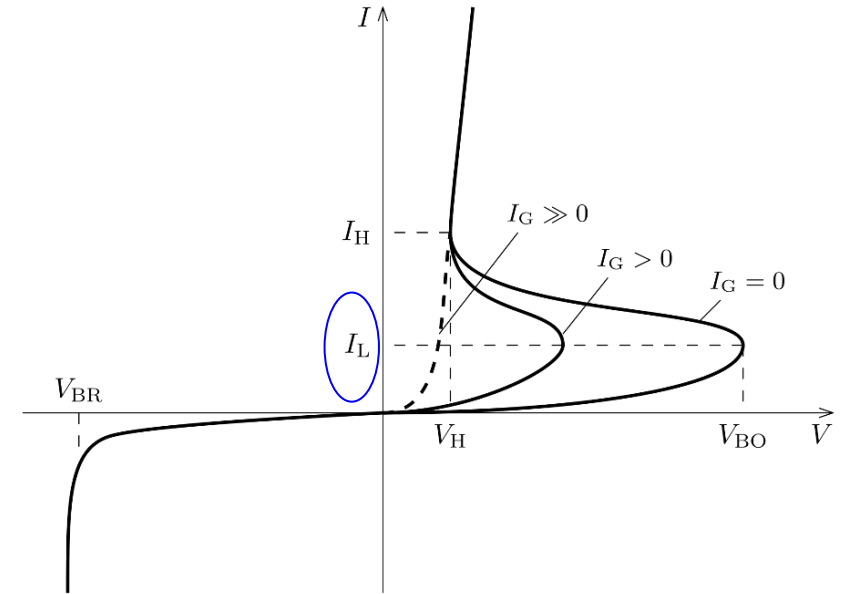
## Latching Current ( $I_L$ )

Minimum principal current required to maintain the thyristor in the on state immediately after the switching from the off state, and the triggering gate signal has been removed.




→ Related to Switch ON

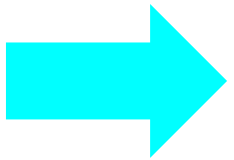


The duration of the gate pulse should be longer than the period for the thyristor current to get to the latching current.
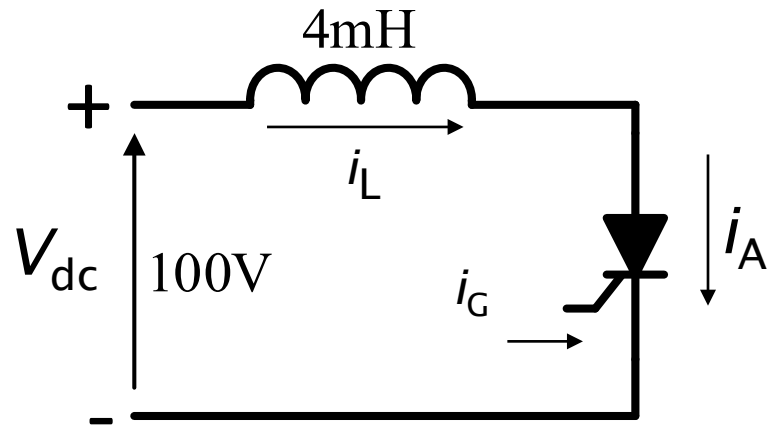
# Answer 1


If the **latching current** of the thyristor in the circuit shown is **4 mA**, determine the minimum width of the gating pulse required to turn on the thyristor.




$$v_L = L \frac{di_L}{dt}$$

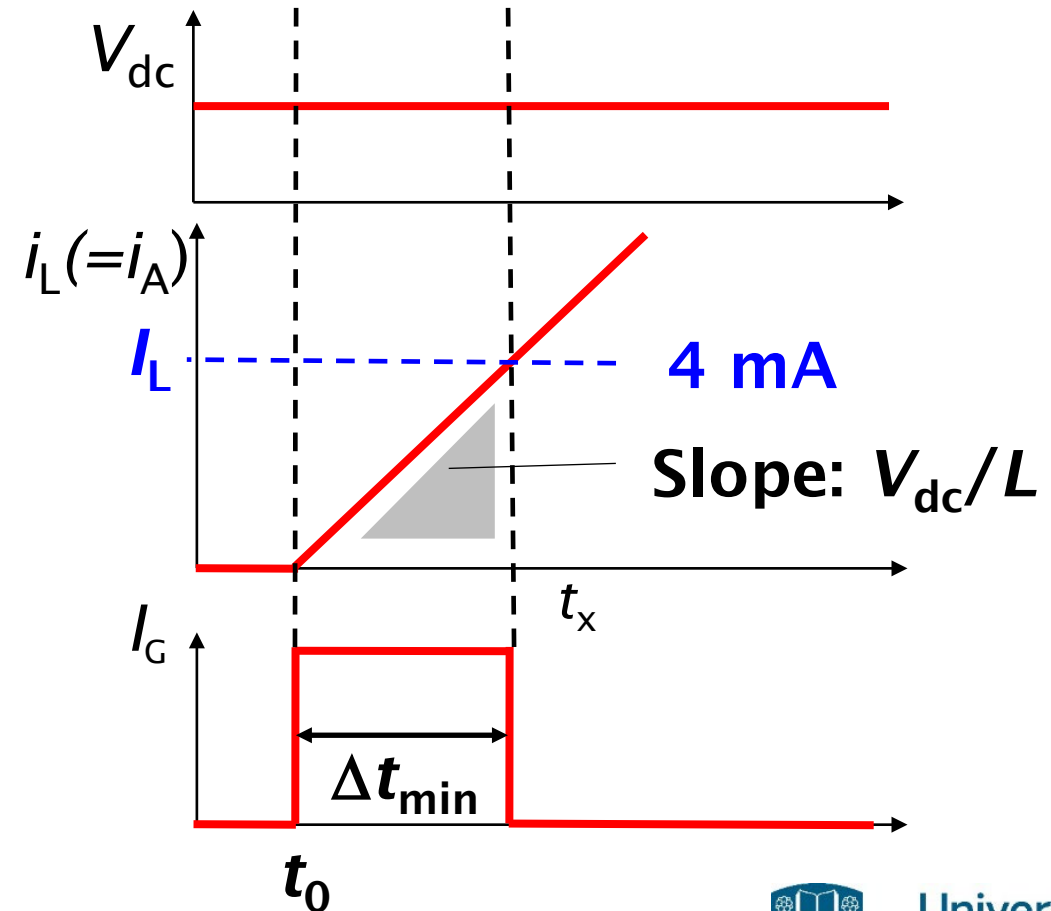

# Answer 1

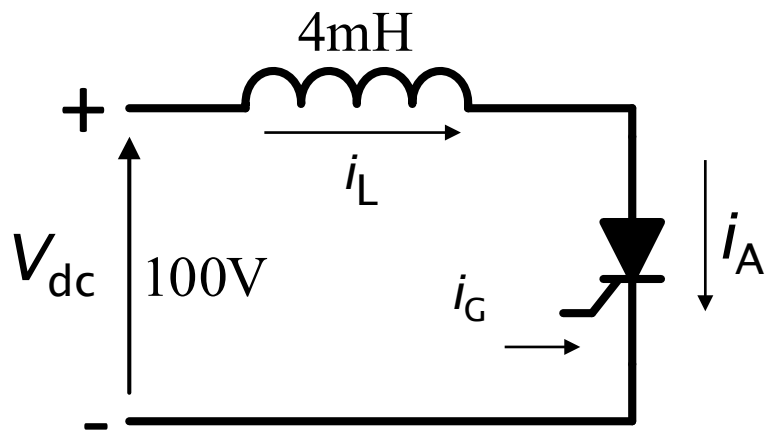

$$I_L / \Delta t_{\min} = V_{dc} / L$$

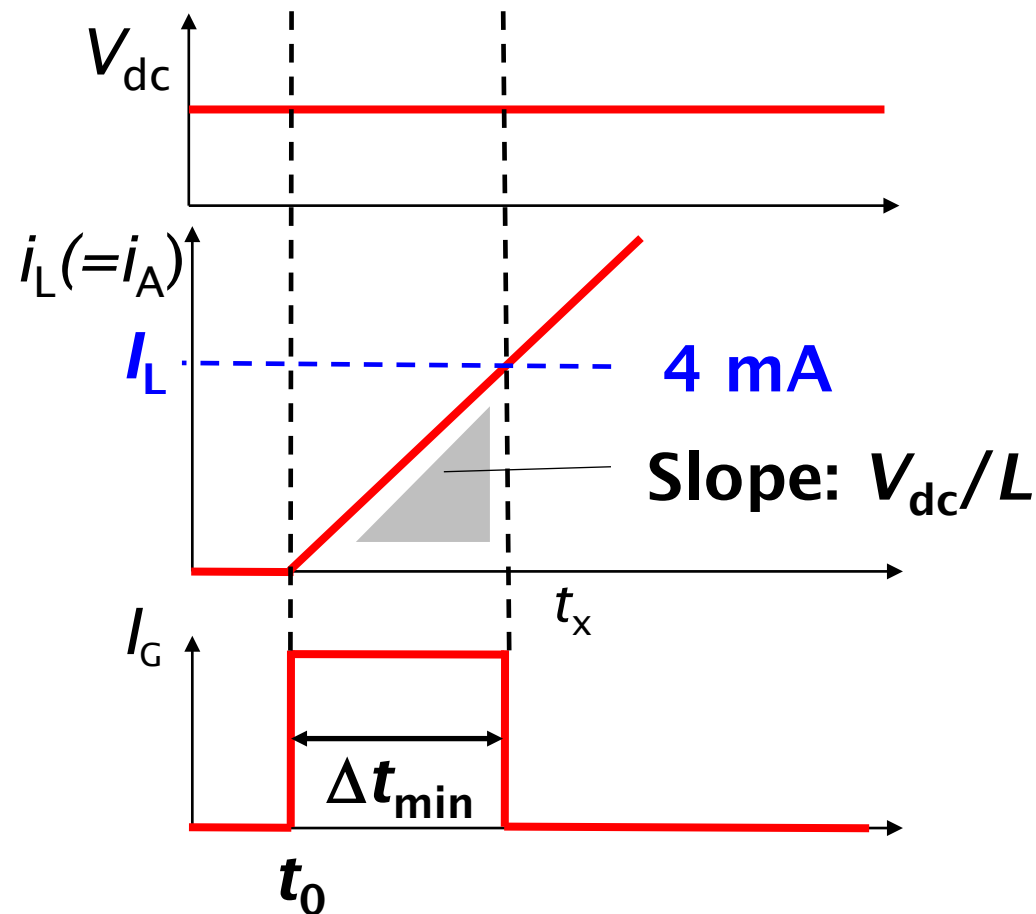

$$\begin{aligned} \Delta t_{\min} &= L I_L / v_{dc} = (4 \text{ (mH)} \times 4 \text{ (mA)}) / 100 \text{ (V)} \\ &= 16.000 \times 10^{-8} \text{ (s)} = \mathbf{160 \text{ (ns)}} \end{aligned}$$


## Question 2

---

The gate-cathode characteristic for a thyristor is given by a straight line with a gradient of 16 volts per ampere passing through the origin; the gate pulse is limited to 0.5 A. If the gate source voltage is 15 V, calculate the external resistance to be connected in series with the thyristor gate.

# Revision

## Thyristor triggering

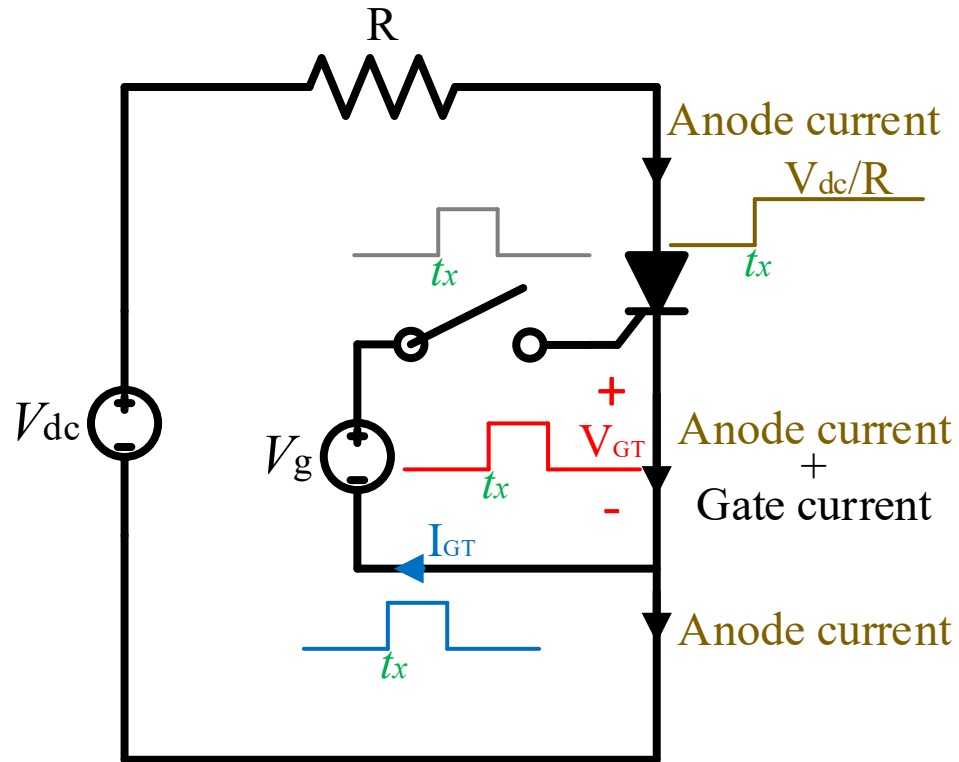



- Only a simple **voltage pulse** is needed to turn on a thyristor.
- Often the triggering circuit with low power/voltage level should be isolated from thyristor gate (power circuit) for protection.



Consider triggering circuit only.
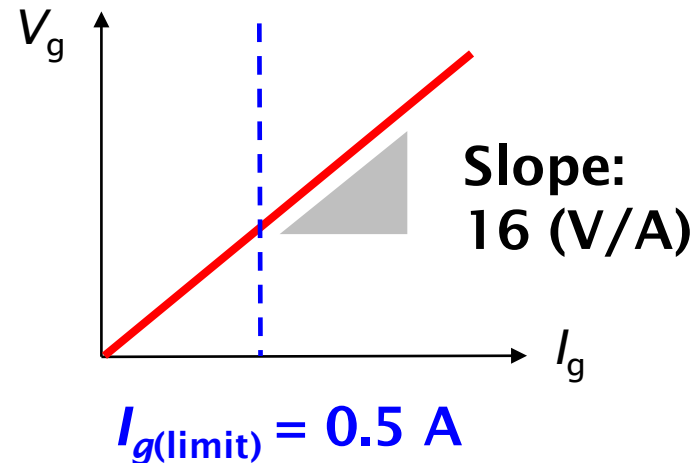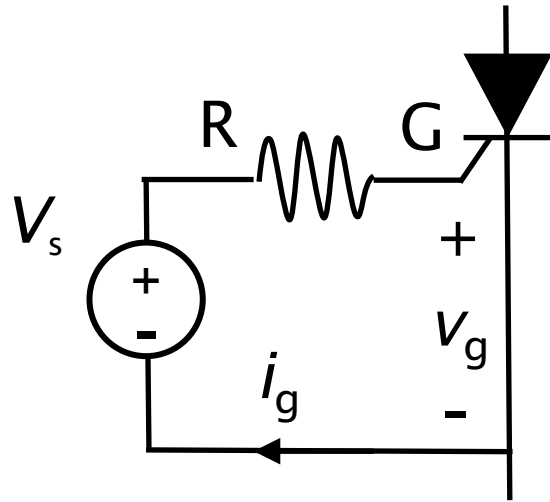
# Answer 2



The gate-cathode characteristic for a thyristor is given by a straight line with a gradient of 16 volts per ampere passing through the origin; the gate pulse is limited to 0.5 A. If the gate source voltage is 15 V, calculate the external resistance to be connected in series with the thyristor gate.



**R can drop the voltage to limit the gate current.**



# Answer 2

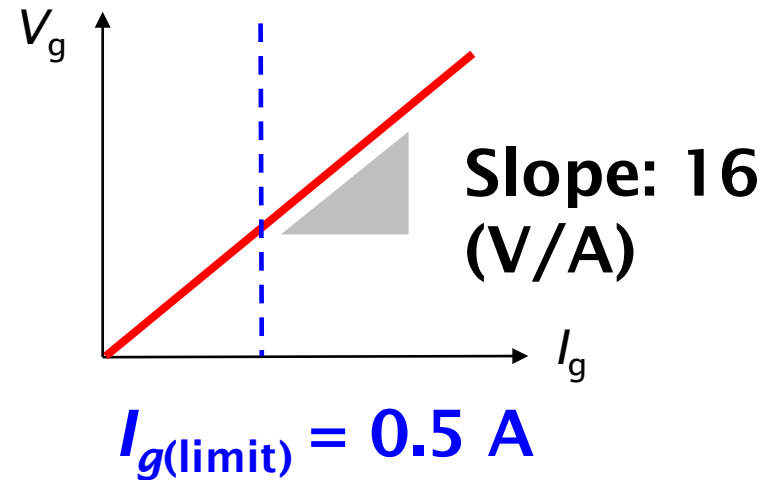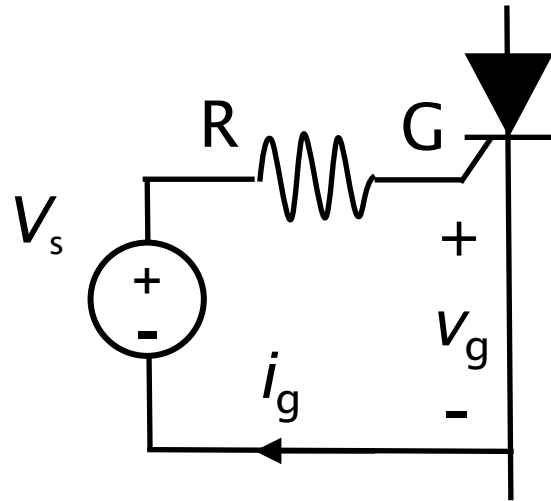

$$V_g = 16i_g$$

$$V_s = Ri_g + V_g = (R + 16)i_g$$

$$i_g = V_s / (R + 16) = 15 / (R + 16) = 0.5$$

$$R = 14 \text{ } (\Omega)$$

$$R + 16 = 15 / 0.5 = 30$$


# Question 3

---

The thyristor in question 2 is supplied with gate pulse of  $4\text{ }\mu\text{s}$  in length. If the gate power dissipation is limited to  $0.3\text{ W}$ , determine the maximum gate pulse repetition rate.

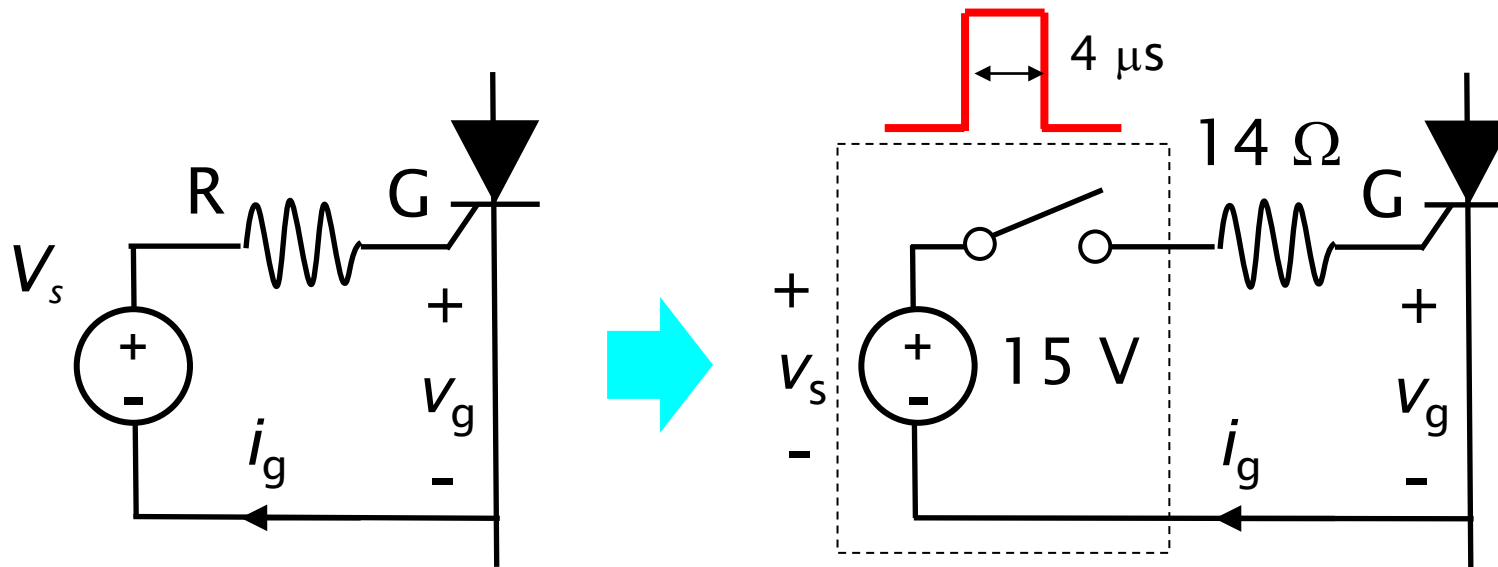
## Question 3

The thyristor in question 2 is supplied with gate pulse of  $4\ \mu\text{s}$  in length. If the gate power dissipation is limited to  $0.3\ \text{W}$ , determine the maximum gate pulse repetition rate.




# Revision

Maximum pulse repetition rate

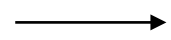


Maximum switching frequency  $f_s$

Gate power dissipation  $P_g$

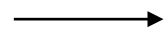

Average power dissipated in a period


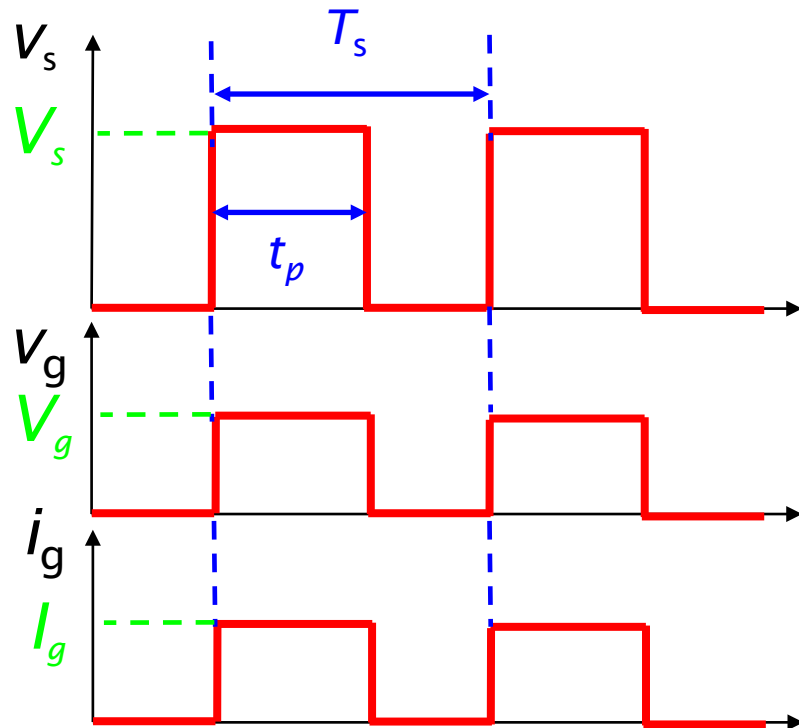


$$f_s = \frac{1}{T_s}$$


$$P_g = \frac{1}{T_s} \int_0^{T_s} v_g(t) i_g(t) dt$$
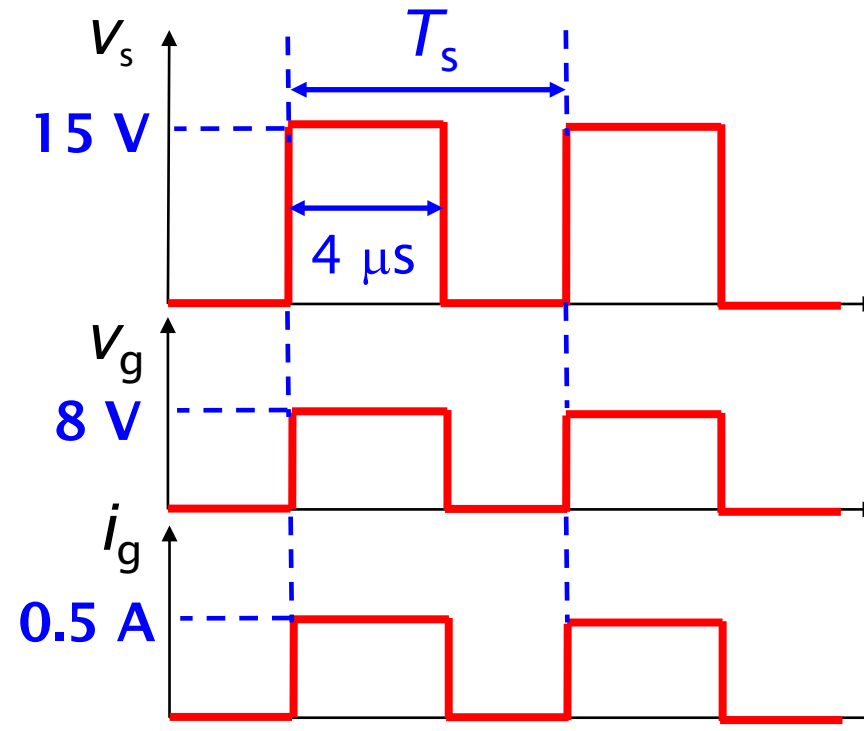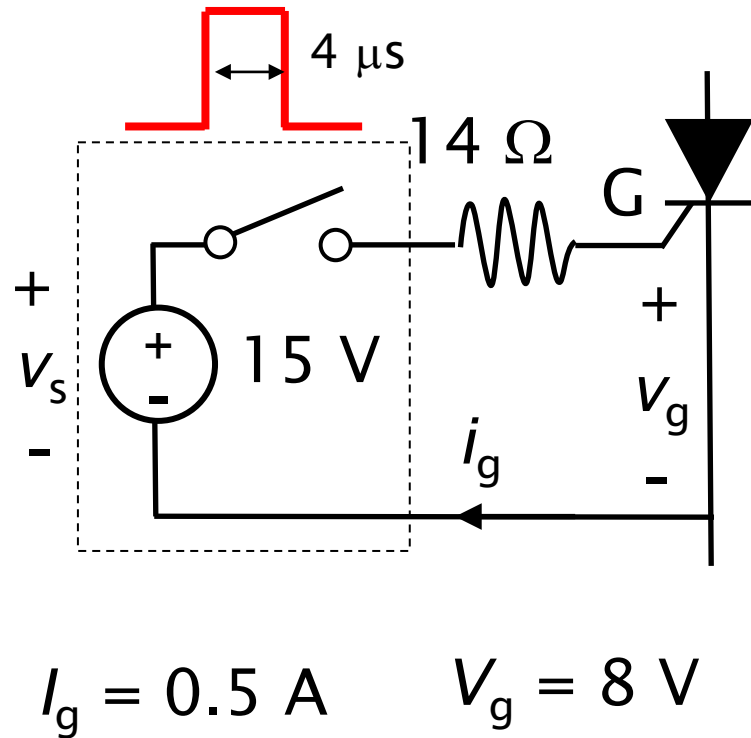
# Answer 3

The thyristor in question 2 is supplied with gate pulse of  $4\ \mu\text{s}$  in length. If the gate power dissipation is limited to  $0.3\ \text{W}$ , determine the maximum gate pulse repetition rate.



# Answer 3

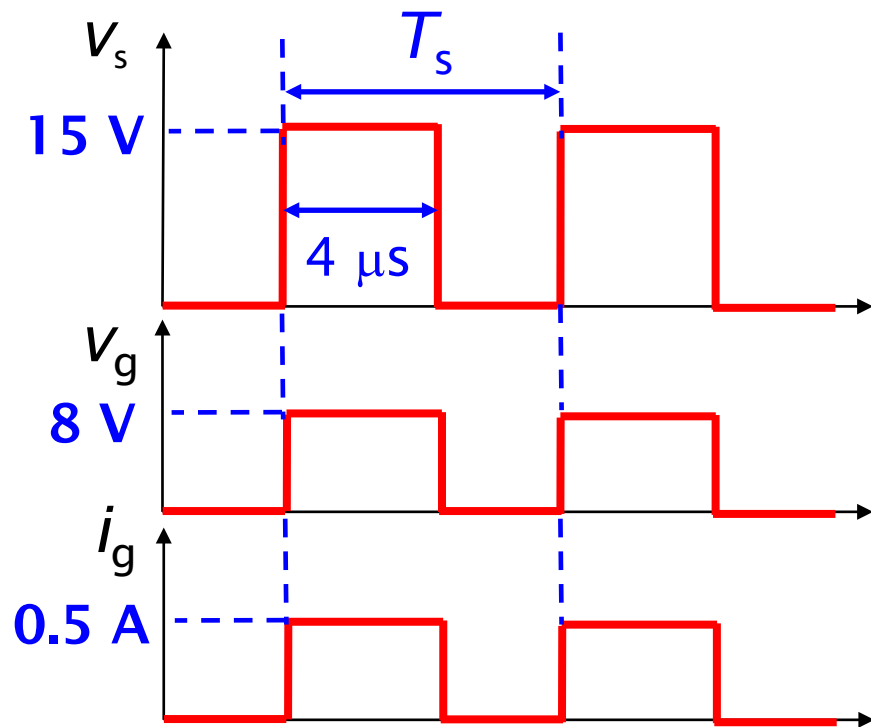

$$\begin{aligned} P_g &= \frac{1}{T_s} \int_0^{T_s} v_g(t) i_g(t) dt \\ &= \frac{1}{T_s} \left( \int_0^{4 \mu\text{s}} v_g(t) i_g(t) dt \right) + \frac{1}{T_s} \underbrace{\left( \int_{4 \mu\text{s}}^{T_s} v_g(t) i_g(t) dt \right)}_0 \\ &= \frac{1}{T_s} \left( \int_0^{4 \mu\text{s}} (8 \times 0.5) dt \right) \\ &= \frac{1}{T_s} [4t]_0^{4 \mu\text{s}} = \frac{16 \mu}{T_s} \leq 0.3 \end{aligned}$$

$$f_s = \frac{1}{T_s} \leq \frac{0.3}{16 \times 10^{-6}} = 18750 = \mathbf{18.750 \text{ kHz}}$$