

ELEC2208 Power Electronics and Drives

Rectifier (1)

- Single Phase Rectifier -

Yoshi Tsuchiya

Smart Electronic Materials and Systems (SEMS) Group

yt2@ecs.soton.ac.uk

59/4219

Classification

- Phase-Controlled Thyristor Converter


AC-AC, Voltage

- Rectifier **AC-DC**

- Cycloconverter **AC-AC, Frequency**


- Inverter **DC-AC**

- DC-to-DC Converter **DC-DC**

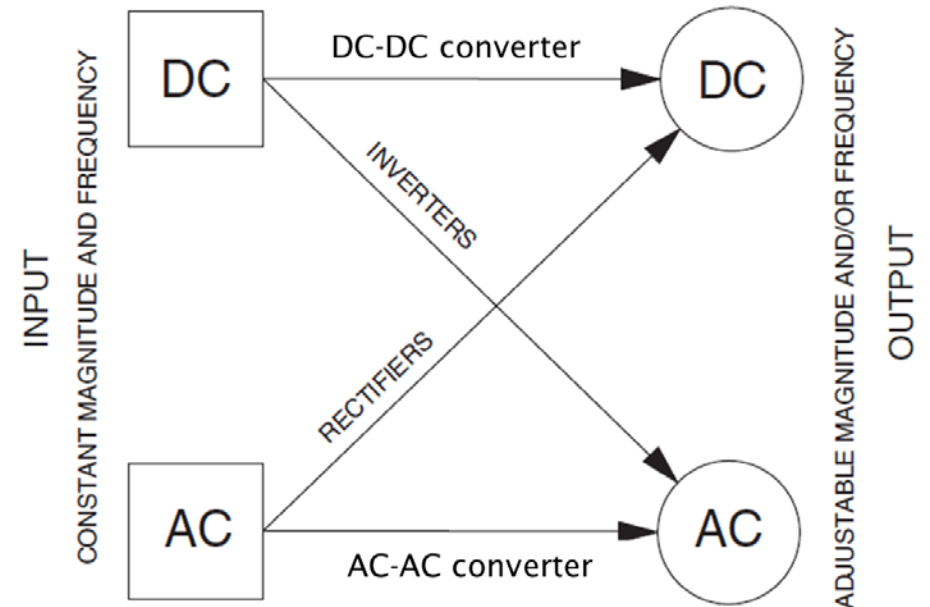


Rectifier - Classification

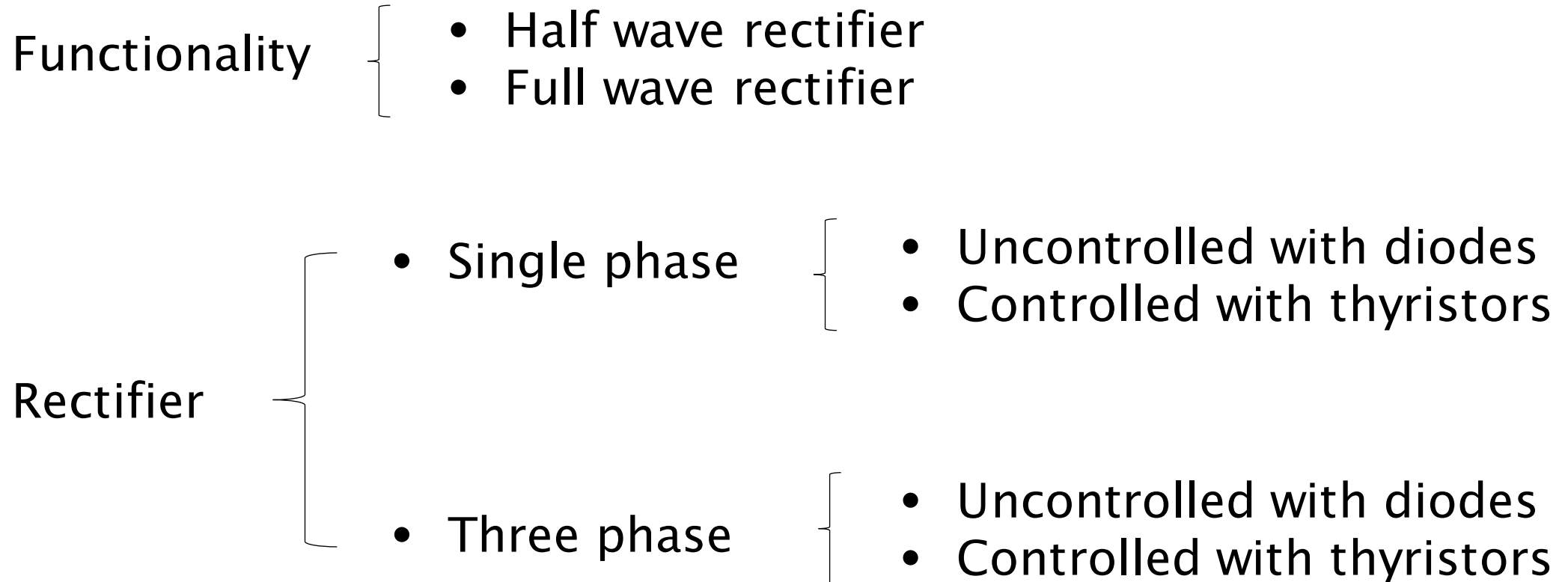
Rectifier converts AC voltage to DC voltage



Half wave rectifier

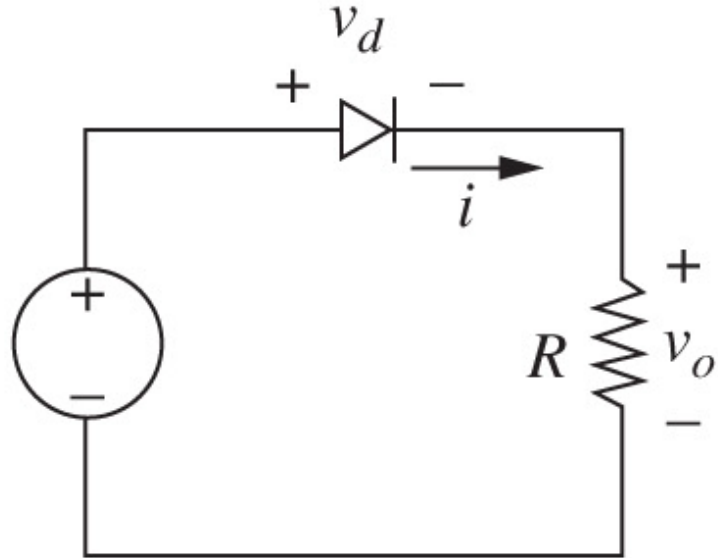

$$v_s = V_m \sin(\omega t)$$

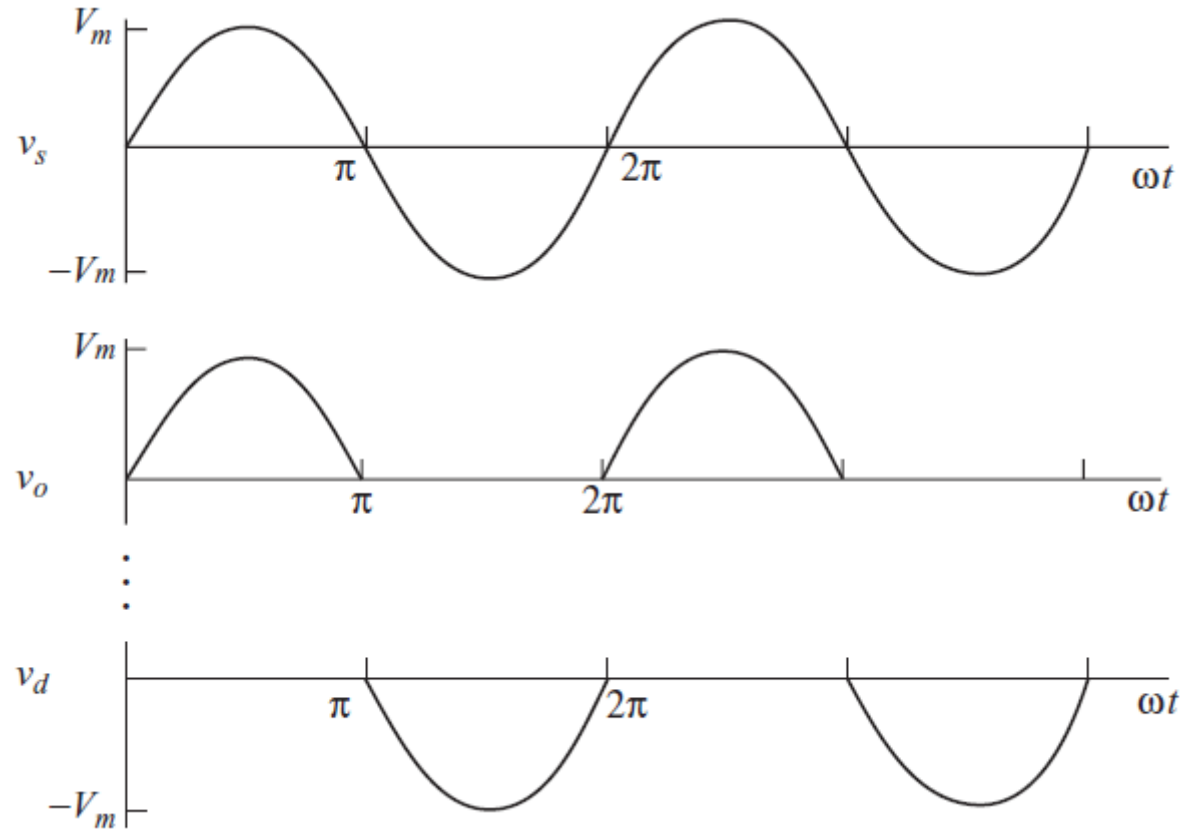



Practically limited to used for low power.

Full wave rectifier


Full wave rectifier is preferred due to following advantages:

- The average current in the ac source is zero.
- The output of the full-wave rectifier has inherently less ripple than the half-wave rectifier.

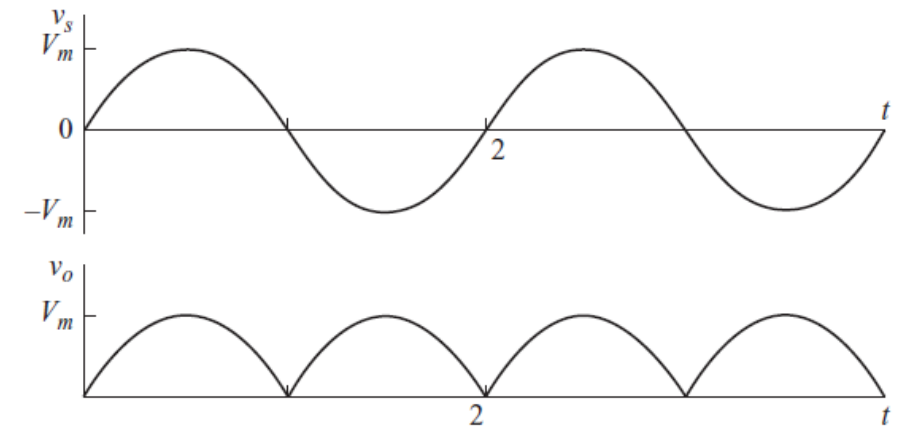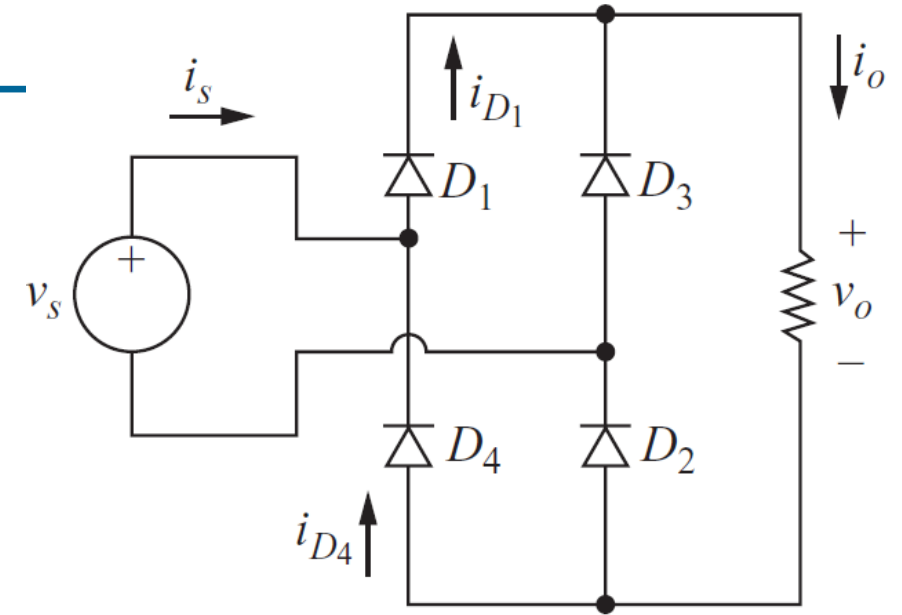Single phase rectifier and three phase rectifier are to be analysed.




Single phase full wave rectifier

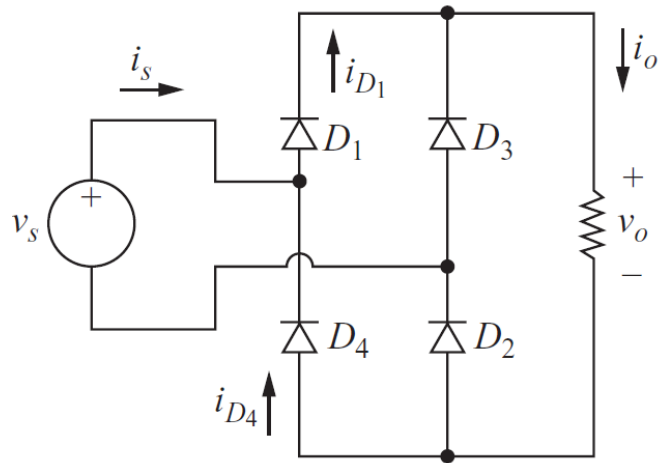

**Full wave rectifier
with 4 diodes
(uncontrolled),
Resistive load**

Operation

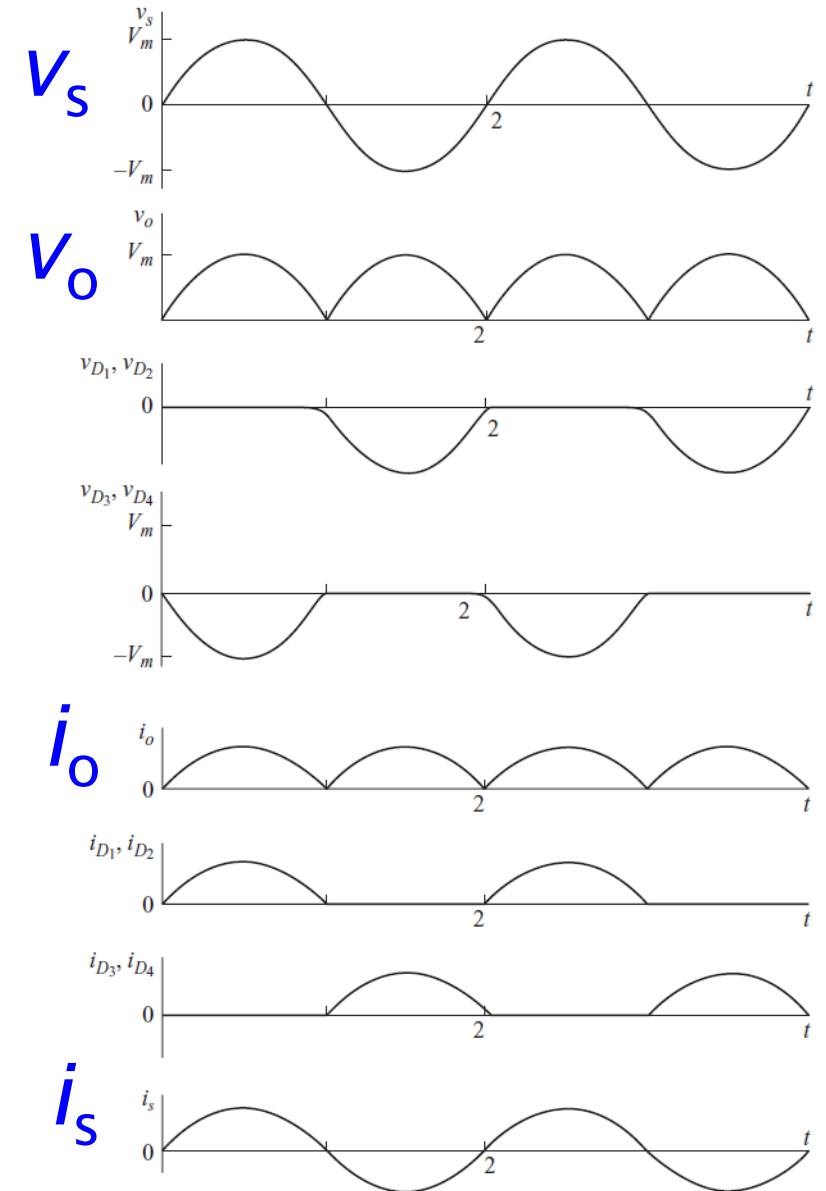- Output voltage is $+v_s$ when D1 and D2 are on.
- Output voltage is $-v_s$ when D3 and D4 are on.
- The load current can be positive or zero but can never be negative.
- D1 & D3 and D2 & D4 cannot conduct simultaneously.



Single phase full wave rectifier

Output voltage v_o

$$v_o(t) = \begin{cases} V_m \sin(\omega t) & \text{for } 0 \leq \omega t \leq \pi \\ -V_m \sin(\omega t) & \text{for } \pi \leq \omega t \leq 2\pi \end{cases}$$

DC component of output voltage and current

$$V_o = \frac{1}{\pi} \int_0^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{V_m}{\pi} [-\cos \theta]_0^{\pi} = \frac{2V_m}{\pi}$$


$$I_o = \frac{V_o}{R} = \frac{2V_m}{\pi R}$$

(Resistive load)


Power absorbed by the load

$$P = I_{rms}^2 R \quad I_{rms} = \frac{I_m}{\sqrt{2}} \quad (\text{same as RMS of source})$$

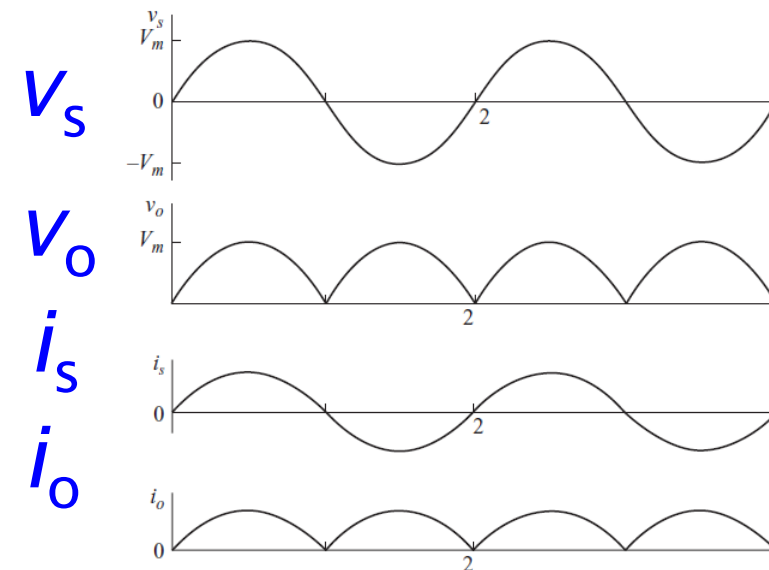
The fundamental frequency of the output voltage is $2f_{\text{source}}$.



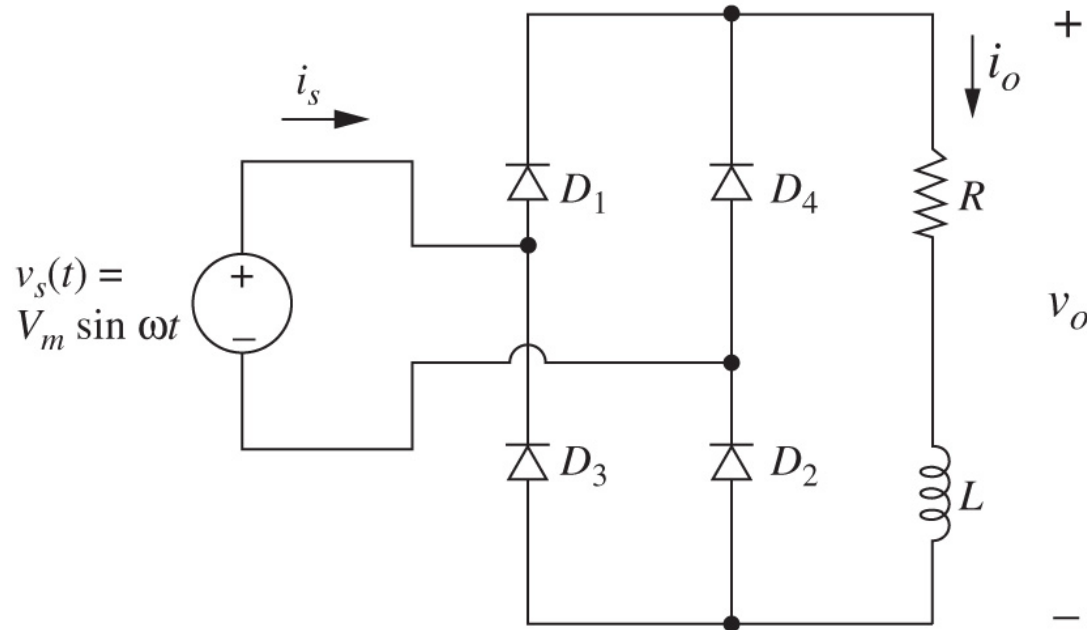Single phase full wave rectifier – *RL* load



Voltages and currents

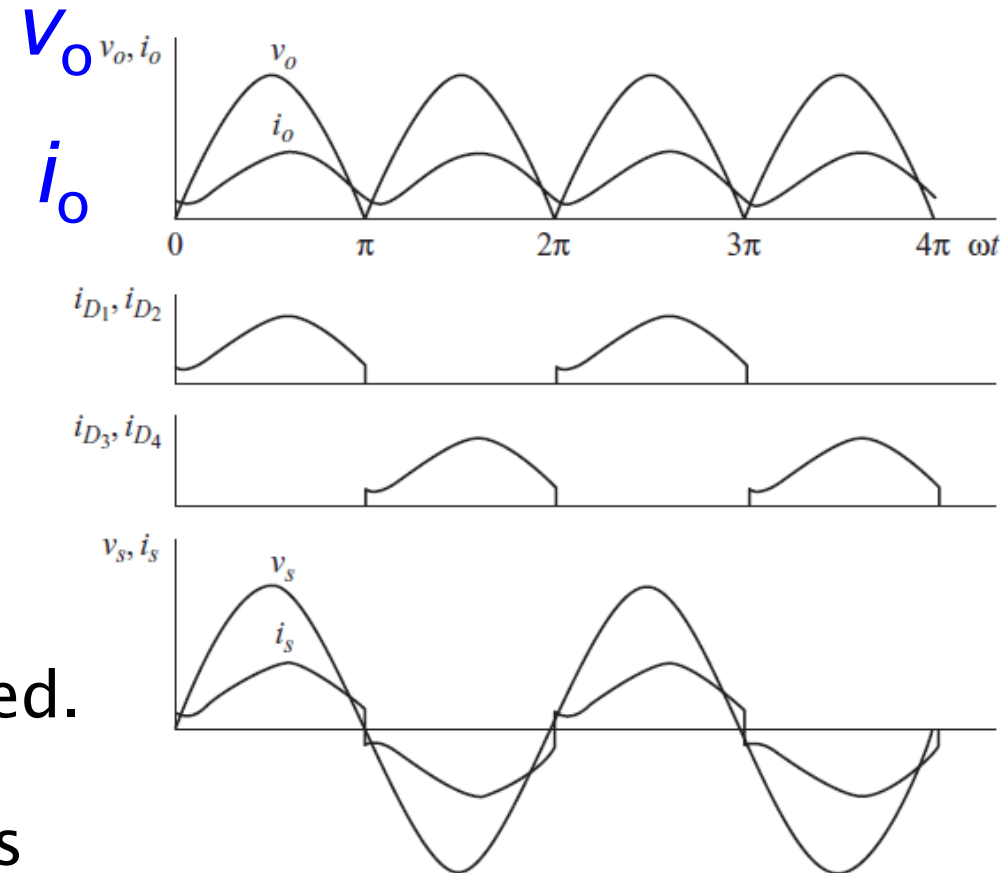

- Phase of the output current is shifted.
- Output current becomes continuous

Single phase full wave rectifier – RL load

Output voltage (Fourier series)



$$v_o(t) = V_o + \sum_{n=2,4,\dots}^{\infty} V_n \cos(n\omega t + \pi)$$

$$\text{where } V_o = \frac{2V_m}{\pi} \text{ and } V_n = \frac{2V_m}{\pi} \left(\frac{1}{n-1} - \frac{1}{n+1} \right)$$


- Voltage amplitude decreases as the harmonic number, n increases.
- The dc current and current amplitude at each frequency are given by

$$I_o = \frac{V_o}{R} \quad I_n = \frac{V_n}{Z_n} = \frac{V_n}{|R + jn\omega L|}$$

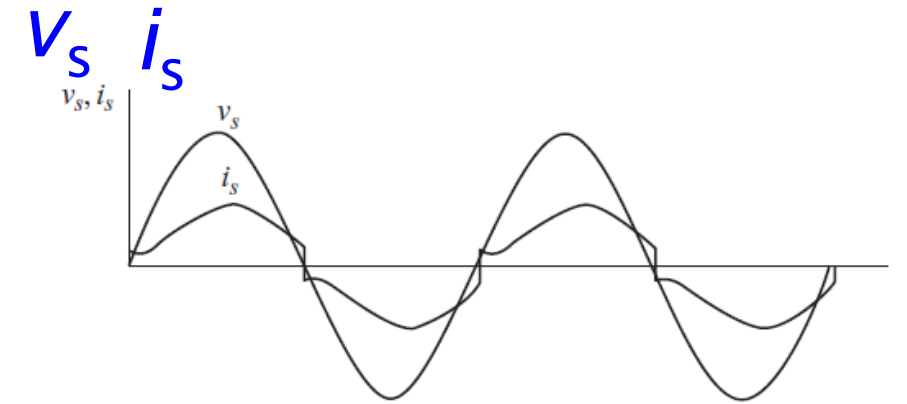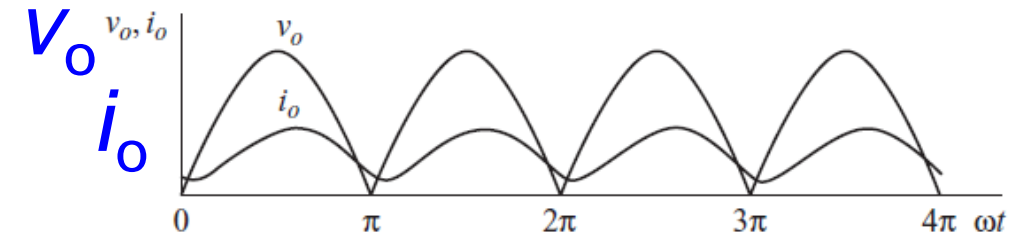- If $\omega L \gg R$, $I_o \gg I_n \longrightarrow i(t) \sim I_o$ (dc only)




Pure DC current
for larger L

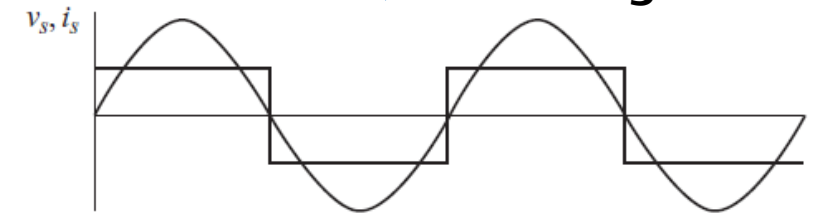


Single Phase Controlled Rectifier

Thyristors are used for rectification.

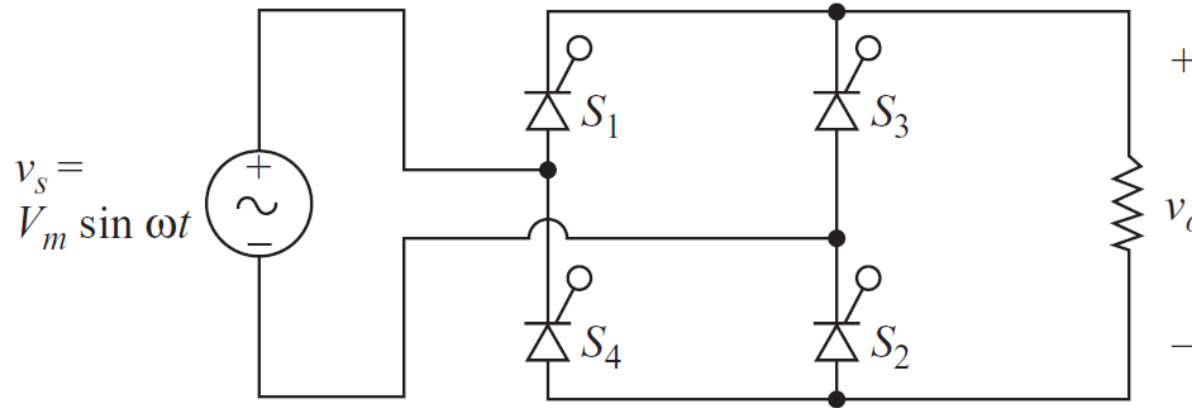

Output voltage

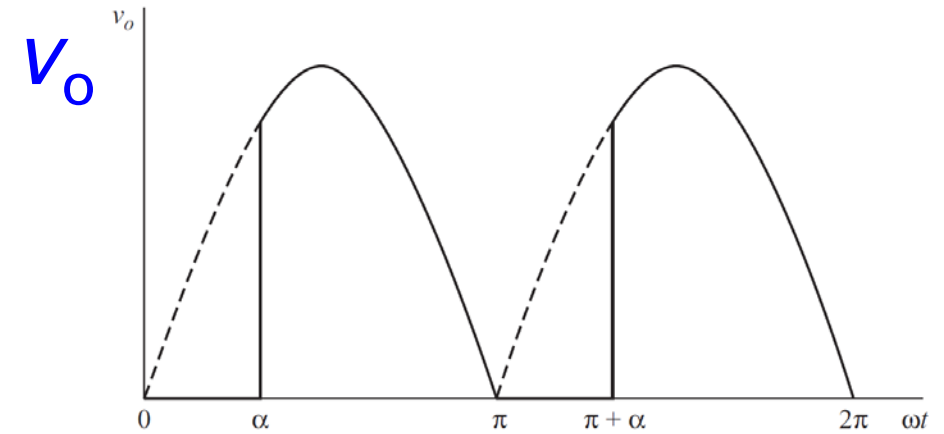

Replacing the diodes with thyristors allow for voltage and hence the power control by controlling the firing/delay angle.



Single Phase Controlled Rectifier

Resistive load

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d(\omega t) = \frac{V_m}{\pi} (1 + \cos \alpha)$$


$$I_o = \frac{V_o}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$
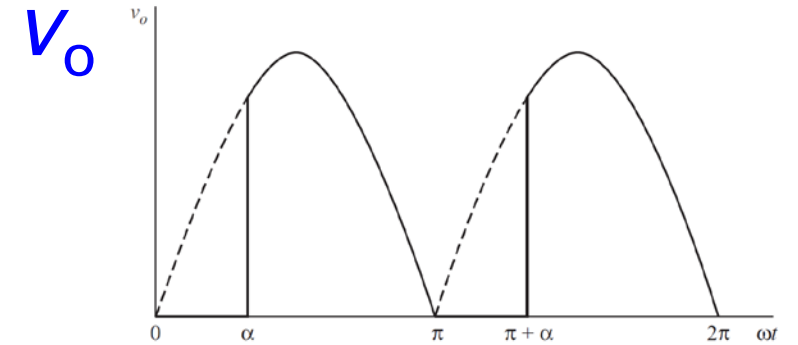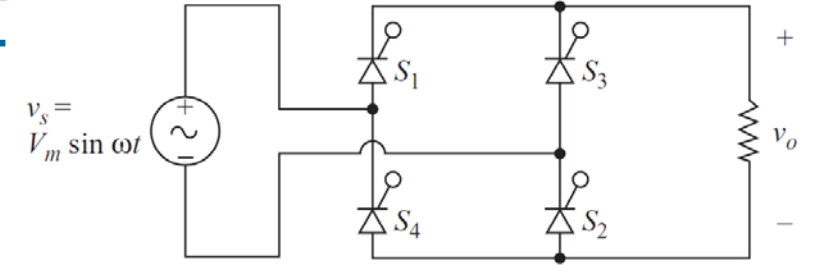
$$I_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} \left(\frac{V_m}{R} \sin \omega t \right)^2 d(\omega t)} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$




Single phase controlled rectifier

RL load

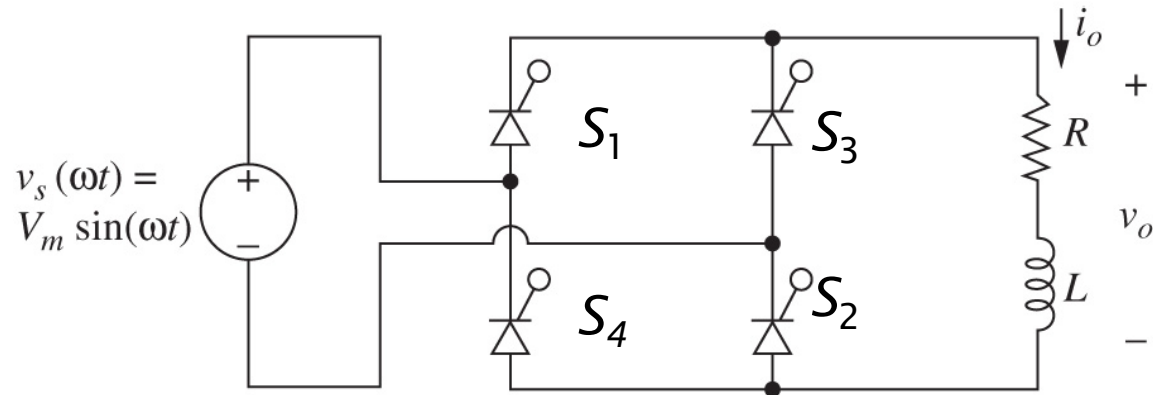


Load current can be continuous or discontinuous depending on the inductance.

Discontinuous current

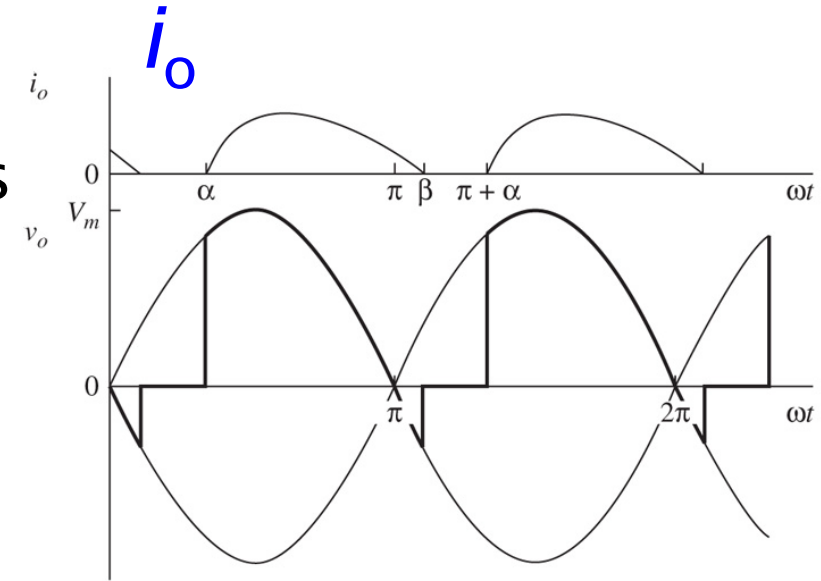

Continuous current (large L)

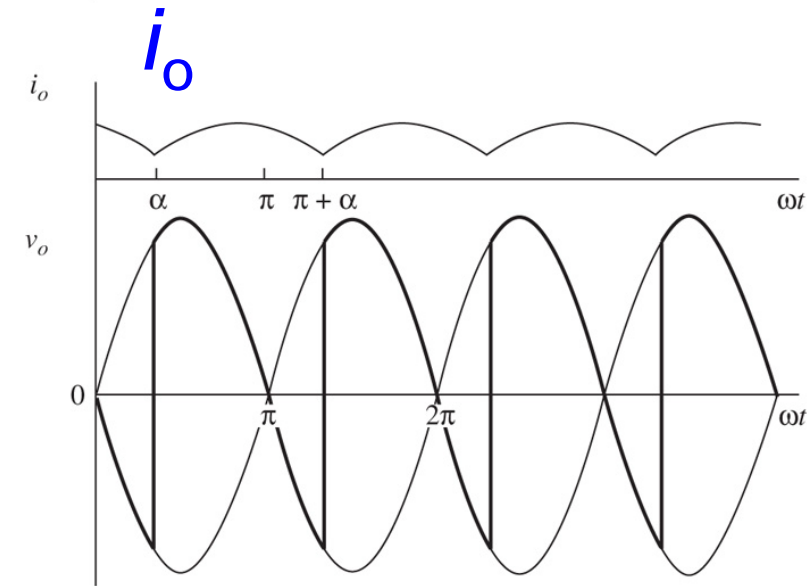

Single phase controlled rectifier

RL Load, Continuous Current

Condition $\alpha \leq \tan^{-1} \left(\frac{\omega L}{R} \right)$

Output voltage

$$v_o(t) = V_o + \sum_{n=1}^{\infty} V_n \cos(n\omega t + \theta_n)$$

DC average

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} V_m \sin(\omega t) d(\omega t) = \frac{2V_m}{\pi} \cos \alpha$$


AC components

$$V_n = \sqrt{a_n^2 + b_n^2}$$

$$a_n = \frac{2V_m}{\pi} \left[\frac{\cos(n+1)\alpha}{n+1} - \frac{\cos(n-1)\alpha}{n-1} \right]$$


$$b_n = \frac{2V_m}{\pi} \left[\frac{\sin(n+1)\alpha}{n+1} - \frac{\sin(n-1)\alpha}{n-1} \right]$$

$$n = 2, 4, 6 \dots$$

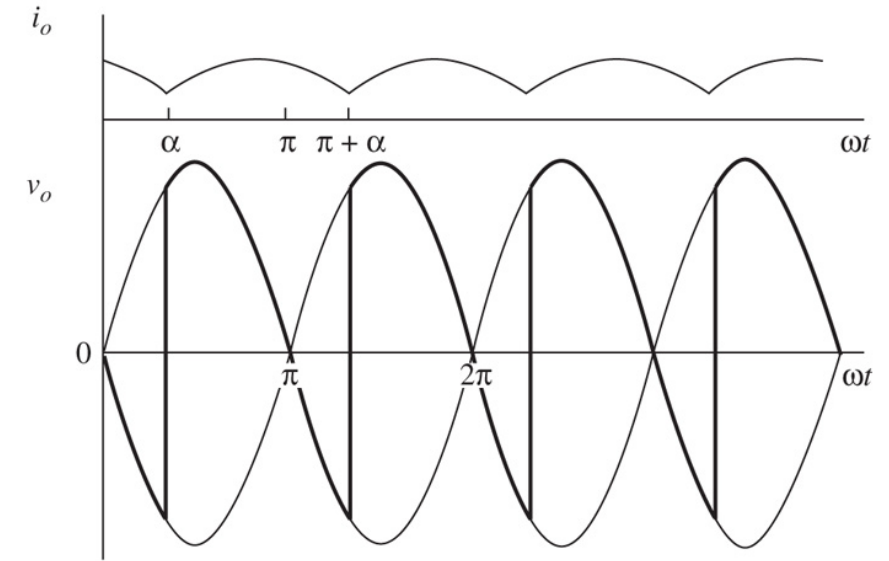

Single phase controlled rectifier

RL-Source load

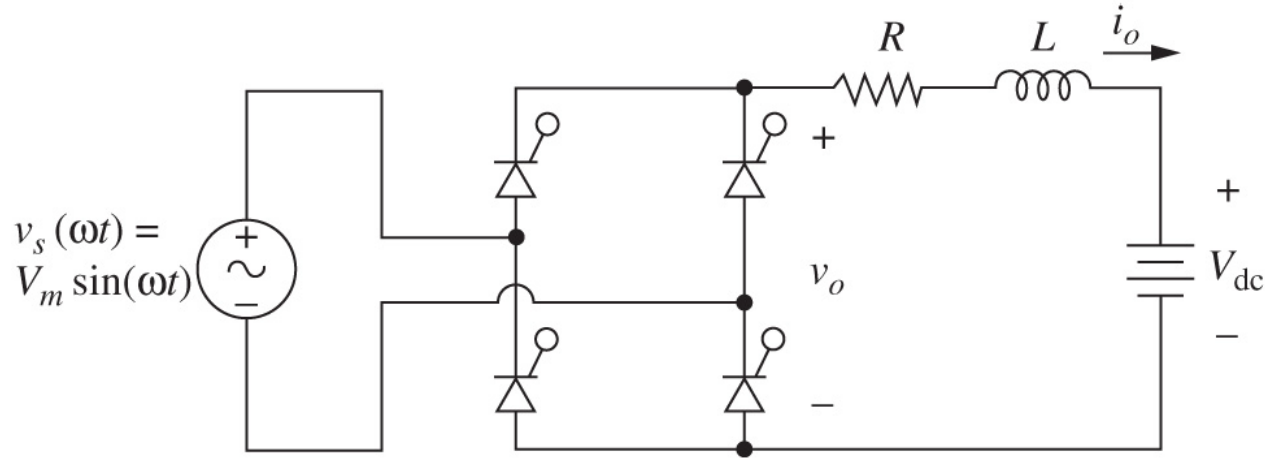

Common model in application
(DC motor, battery etc)

Minimum firing angle

$$\alpha \geq \sin^{-1} \left(\frac{V_{dc}}{V_m} \right)$$

For continuous current case

Average output voltage

$$V_o = \frac{2V_m}{\pi} \cos \alpha$$

Average load current

$$I_o = \frac{V_o - V_{dc}}{R}$$


Power adsorbed by dc voltage

$$P_{dc} = I_o V_{dc}$$

Rectifier operating as Inverter

- It is also possible for power to flow from the load to the ac source, which classifies the circuit as an inverter.
- By referring to the equation, $V_o = (2 V_m / \pi) \cos \alpha$, the output voltage reduces with firing angle.
- At 0.5π , the average output voltage is zero.
- The output voltage becomes negative (while the load current is remain positive) when α is greater than 0.5π .
- The average power is negative (positive current x negative voltage) indicates that the direction of power flow is reversed; from output (dc power source at load terminal) to input alternating supply.
- V_{dc} must be negative.

Rectifier operating as Inverter

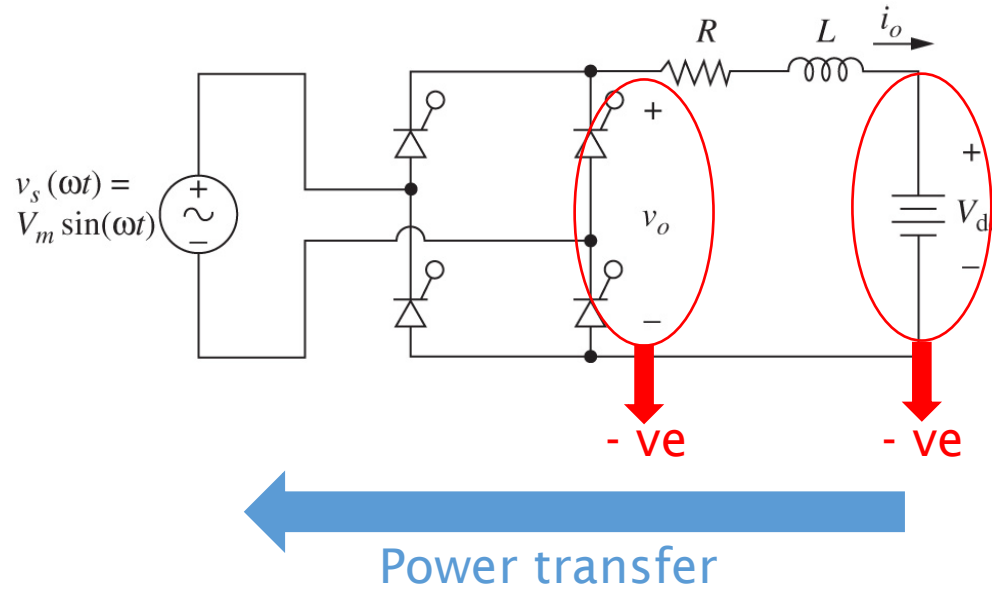

$0 < \alpha < 90^\circ \rightarrow V_o > 0$,
rectifier operation

$90^\circ < \alpha < 180^\circ \rightarrow V_o < 0$,
inverter operation

- Output current flows in +ve direction in both rectification and inversion mode.
- The load (battery) now supplies power (during inversion mode) hence the polarity must be reversed.
- Power is transferred from dc load terminal (battery) to ac supply terminal: DC to AC.

Summary - Single phase rectifier

- 4 diodes/thyristors are used for full-wave rectification.
- The thyristors allow for voltage and hence the power control by controlling the firing/delay angle.
- If the power flows from the load to the ac source, the circuit is classified as an inverter, suggesting a rectifier can be operated as an inverter.

