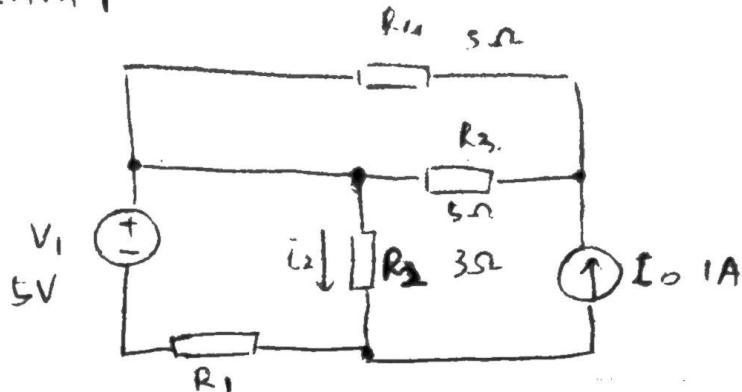



2021-2022 Transmission

Question 1


(a)



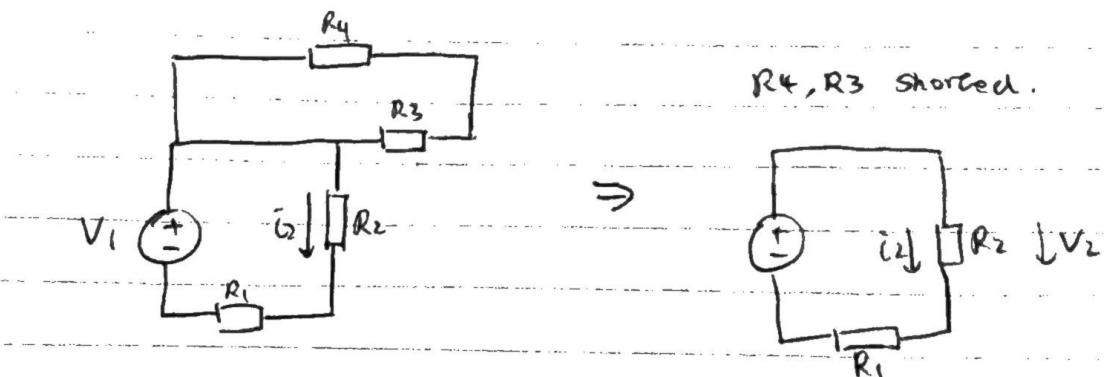(i) only voltage source, current source shorted. \Rightarrow open.



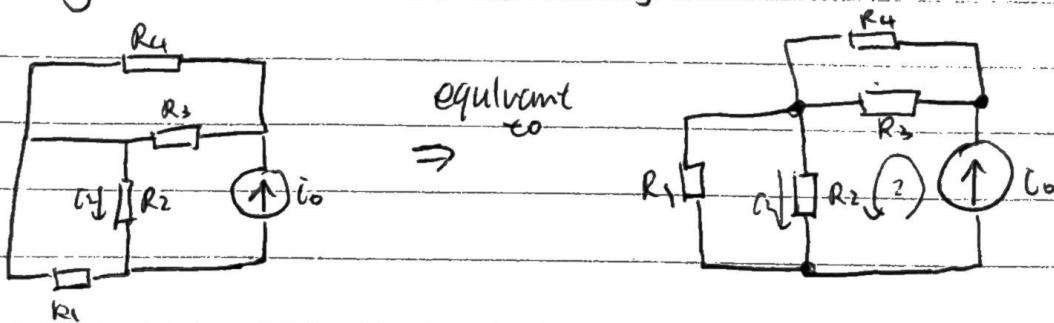(ii) only current source, or voltage source shorted



(iii) from (i)

$$V_{2,1} \approx V_1 \frac{R_2}{R_2 + R_1} \quad (\text{voltage divider})$$

$$V_{2,1} = \frac{3}{5} \times 5 = 3 \text{ V}$$


$$I_{2,1} = \frac{3 \text{ V}}{3 \Omega} = 1 \text{ A}$$

from (ii) I_{R2} . current across $= 1 \text{ A}$

$$\text{current } I_{2,2} = \frac{R_1}{R_2 + R_1} I_0 = \frac{2}{5} \times 1 = 0.4 \text{ A}$$

$$I_{\text{total}} = I_{2,1} + I_{2,2} = 1.4 \text{ A}_{\parallel}$$

(b)

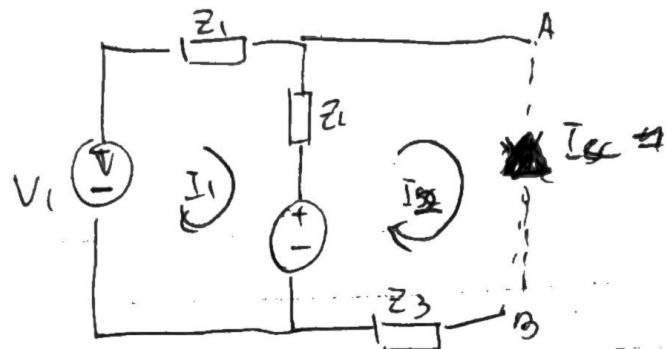

Note: terminal
→ AB shorted.

$$I_{SC} = -I_2$$

Mesh 1

$$V_1 + I_1 Z_1 + Z_2 (I_1 - I_2) - V_2 = 0$$

$$10I_1 - 5I_2 = 0$$

$$2I_1 = I_2$$


Mesh 2 $I_2 Z_3 + 3 + (I_2 - I_1) Z_2 = 0$

$$5I_2 + 5I_2 - 2.5I_2 = -3$$

$$I_2 = -0.4 \text{ A}$$


$$I_{SC} = 0.4 \text{ A.}$$

$$I_{SC} \Rightarrow I_{IN}$$

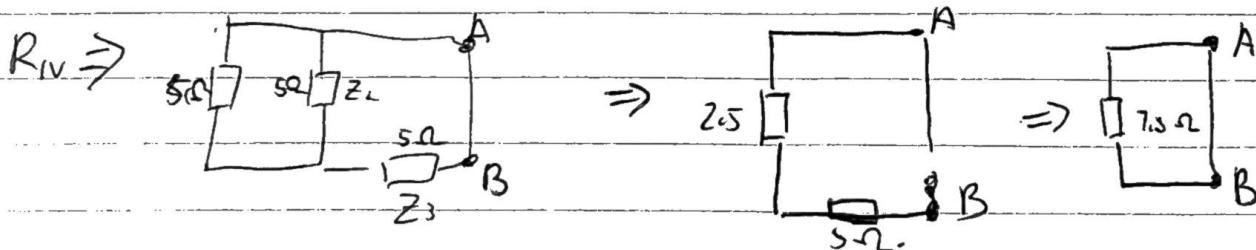

$$R_N = 7.5 \Omega$$

→ Equivalent circuit

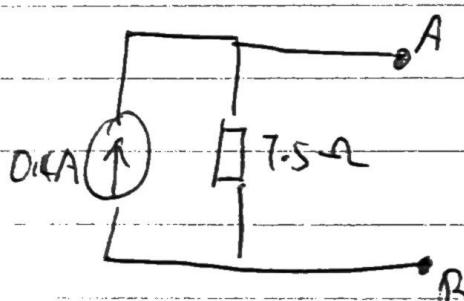

$$(C) \begin{bmatrix} AB \\ CD \end{bmatrix} \quad V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DJ_2$$

~~$V_1 = IA$~~
 ~~$I_1 = DC$~~

$$(D) \begin{vmatrix} 1 & 0 & | & 1 & Z & | & 1 & 0 \\ X & 1 & | & 0 & 1 & | & Y & 1 \end{vmatrix}$$

$$= \begin{vmatrix} 1 & Z & | & 1 & 0 \\ Y_1 & Y_1Z+1 & | & Y_2 & 1 \end{vmatrix}$$

$$= \begin{vmatrix} 1+ZY_2 & Z \\ Y_1+Y_1Y_2Z & Y_1Z+1 \end{vmatrix} = \begin{vmatrix} A & B \\ C & D \end{vmatrix} = \begin{bmatrix} 2.5 & 3 \\ 1 & 1.6 \end{bmatrix}$$

$$1+ZY_2 = 2.5 \quad Z = 3 \quad //$$

$$1+3Y_2 = 2.5$$

$$Y_2 = 0.5 \quad //$$

$$Y_1Z+1 = 1.6 \quad Y_1 = 0.2 \quad //$$

~~Y₁ =~~

(ii) To be symmetrical, ~~As~~ A has $C = D$


here $A \neq D \Rightarrow$ not symmetrical.

(iii) $AD - BC = 2.5 \times 1.6 - 3 = 1 \Rightarrow$ reciprocal

$$(IV) Z_H = \sqrt{\frac{AB}{CD}} \quad Z_L = \sqrt{\frac{DB}{CA}}$$

$$= 2.16 \quad = 3.19$$
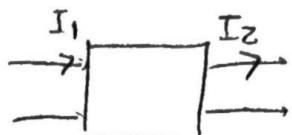
$$(d) \quad Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$



$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (2)}$$

$[Z]$ to $[ABCD]$

$$\text{--- (1)} \Rightarrow V_1 - Z_{12}I_2 = Z_{11}I_1$$

$$I_1 = \frac{V_1}{Z_{11}} - \frac{Z_{12}}{Z_{11}} I_2 \quad \text{--- (3)}$$

$$\text{--- (2)} \quad V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11}I_1 = V_2 - Z_{22}I_2$$

$$I_1 = \frac{V_2}{Z_{21}} - \frac{Z_{22}}{Z_{21}} I_2 \quad \text{--- (4)}$$

$$\text{--- (3)} = \text{--- (4)}$$

$$\frac{V_1}{Z_{11}} - \frac{Z_{12}}{Z_{11}} I_2 = \frac{V_2}{Z_{21}} - \frac{Z_{22}}{Z_{21}} I_2.$$

$$\frac{V_1}{Z_{11}} = \frac{V_2}{Z_{21}} + \left(\frac{Z_{12}}{Z_{11}} - \frac{Z_{22}}{Z_{21}} \right) I_2 \quad (1)$$

$$V_{AB} = \frac{Z_{11}}{Z_{21}} V_2 + \frac{(Z_{11})(Z_{21} - Z_{22} \cdot Z_{11})}{Z_{11}Z_{21}} I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 + \frac{Z_{12}Z_{21} - Z_{22}Z_{11}}{Z_{21}} I_2.$$

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} \xrightarrow{Z} \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{Z_{12}Z_{21} - Z_{22}Z_{11}}{Z_{21}} \\ \frac{1}{Z_{21}} & -\frac{Z_{22}}{Z_{21}} \end{bmatrix}$$

Question 2.

$$(a) (i) Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{4 \times 10^{-6}}{10^{-8}}} = 20 \Omega$$

$$T_{4, \text{BnM}} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{3+4j-20}{3+4j+20} = -0.688 + 0.294j \\ = 0.748 \angle 2.74^\circ$$

$$T_{2, \text{BnZ}} = \frac{Z_L - Z_0}{Z_L + Z_0} = -0.366 + 0.293j \\ = 0.469 \angle 2.47^\circ$$

$$(ii) Z_{m,L_1} = \frac{Z_0}{Z_0} \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{6 \times 10^6} \\ = \frac{3+4j + j(20) \tan (5.23 \times 10^5)}{20 + j(3+4j) \tan (5.23 \times 10^5)} = 1.047 \times 10^{-7} \quad l_1 = 50^\circ \\ \tan(\beta l) = 5.23 \times 10^5 \\ = 20 \times (0.150003 + 0.20005j) \quad \tan(\beta l) = 5.23 \times 10^5 \\ = 3+4j = 5 \angle 0.927^\circ$$

$$Z_{m,L_2} = \frac{Z_0}{Z_0} \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \quad \beta l = \frac{2\pi}{6 \times 10^6} \times 100 \\ = 1.047 \times 10^{-7} \quad \tan \beta l = 1.047 \times 10^{-4} \\ = 20 \times \frac{8+6j + j20 (1.047 \times 10^{-4})}{20 + j(8+6j) (1.047 \times 10^{-4})} \\ = 20 \times 0.4 + 0.3j = 8(6j) = 10 \angle 0.64^\circ$$

$$Z_{AB} = \cancel{Z_L} - \cancel{\frac{1}{Z_{m,L_1}}} - \frac{1}{Z_{m,L_1} + \frac{1}{Z_{m,L_2}}} \quad (\text{parallel})$$

$$= 2.26 + 2.49j = 3.36 \angle 0.83^\circ //$$

$$T = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{3.36 \angle 0.83 - 20}{3.36 \angle 0.83 + 20} = -0.775 + 0.198 \\ = 0.799 \angle 2.89^\circ //$$

$$(b)_{(i)} \quad V_{02} \quad V_0^+ \quad V^- \\ V(l) = V_0^+ e^{-j\beta l} + V_0^- e^{j\beta l}$$

$$I(l) = \frac{V_0^+ e^{-j\beta l}}{Z_0^+} - \frac{V_0^- e^{-j\beta l}}{Z_0^-}$$

$$Z_L = \frac{V(l)}{I(l)} = \frac{V_0^+ e^{-j\beta l} + V_0^- e^{j\beta l}}{\frac{V_0^+ e^{-j\beta l}}{Z_0^+} - \frac{V_0^- e^{-j\beta l}}{Z_0^-}}$$

at (and)

$$= T(l) = \frac{V(l)}{I(l)}$$

~~$$T(l) = \frac{V(l)}{I(l)}$$~~

$$Z_L = \frac{V_0^+ e^{-j\beta l} + V_0^- e^{j\beta l}}{\frac{V_0^+ e^{-j\beta l}}{Z_0^+} - \frac{V_0^- e^{j\beta l}}{Z_0^-}}$$

$$Z_L = \frac{V_0^+ e^{-j\beta l} + V_0^- e^{j\beta l}}{\frac{Z_0^- V_0^+ e^{-j\beta l}}{Z_0^+ Z_0^-} - \frac{V_0^- e^{j\beta l}}{(Z_0^+)}}$$

$$(l=0) \quad Z_L = \frac{V_0^+ + V_0^-}{Z_0^- V_0^+ - V_0^- Z_0^+}$$

$$(RMM) \quad Z_L (Z_0^- V_0^+ - V_0^- Z_0^+) = (V_0^+ + V_0^-) (Z_0^+ Z_0^-)$$

$$Z_L Z_0^- V_0^+ - Z_L Z_0^+ V_0^- = Z_0^+ Z_0^- V_0^+ + Z_0^+ Z_0^- V_0^-$$

$$Z_L Z_0^- V_0^+ - Z_0^+ Z_0^- V_0^+ = V_0^- (Z_L Z_0^+ + Z_0^+ Z_0^-)$$

$$\frac{V_0^-}{V_0^+} = \frac{Z_L Z_0^- - Z_0^+ Z_0^-}{Z_L Z_0^+ + Z_0^+ Z_0^-}$$

(b) find phase voltage (V_{AN} , V_{BN} , V_{CN})

$$\omega_1 = 127 \text{ rad/s} \quad \omega_2 = 460 \text{ rad/s} \quad Z = 30 + 40j$$

$$W_{\text{total}} = \omega_1 + \omega_2 = 127 + 460 = 587$$

$$\text{Power per phase} = \frac{587}{3} = 195.7$$

$$(I_{\text{rms}})^2 \times |R| = P \quad Z = 30 + 40j$$
$$I_{\text{rms}} = 2.55 \quad = 50 \angle -53.1^\circ$$

$$I_a = 2.55 \angle -53.1^\circ \quad (\text{line current})$$

$$P = |I_{\text{rms}}| |V_{\text{rms}}| \cos(\phi_{V_{ab}, I_a}) \quad V_{an} \rightarrow V_{ab} \quad +30^\circ$$

we measure ab

$$127 = (2.55) (V_{ab}) \cos(30 - 53.1)$$

$$V_{ab, \text{rms}} = 54.1 \text{ V}$$

$$\text{phase voltage peak} = \sqrt{2} \times \frac{54.1}{\sqrt{3}} = \sqrt{2} \times 31.26 \\ = 44.2$$

$$V_{AN} = 44.2 \angle 0^\circ$$

$$V_{BN} = 44.2 \angle -120^\circ$$

$$V_{CN} = 44.2 \angle 120^\circ$$

//