

ELEC2208 Power Electronics and Drives

Inverter

Yoshi Tsuchiya

Smart Electronic Materials and Systems (SEMS) Group

yt2@ecs.soton.ac.uk

59/4219

Classification

- Phase-Controlled Thyristor Converter


AC-AC, Voltage

- Rectifier **AC-DC**

- Cycloconverter **AC-AC, Frequency**

- Inverter **DC-AC**


- DC-to-DC Converter **DC-DC**

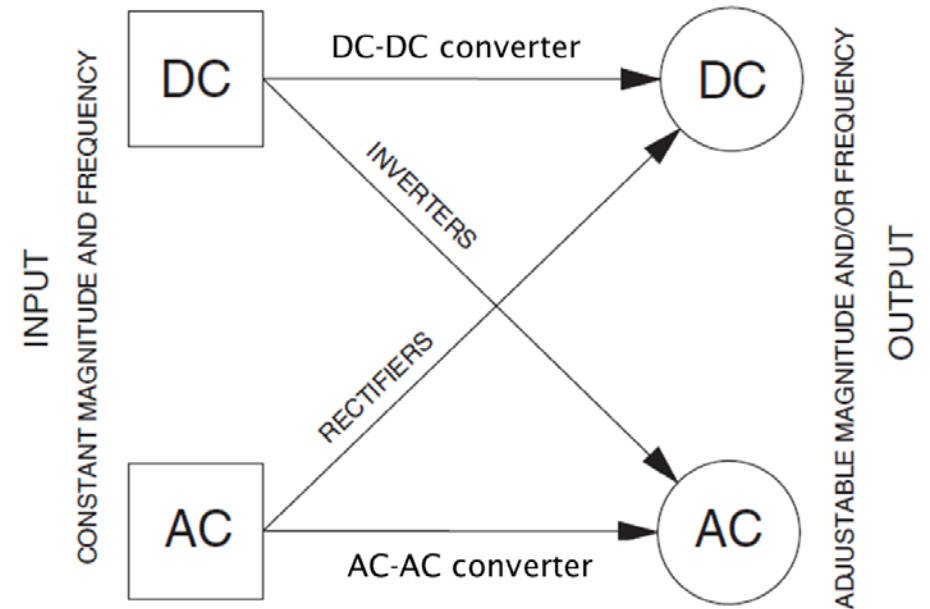

What is Inverter?

- Converts DC to AC.
- Inverters transfer power from a DC source to an AC load.
- Synthesize a sinusoidal voltage waveform (fundamental component) that has a controlled frequency and magnitude from a dc supply.
- Applications: adjustable-speed ac motor drives, uninterruptable power supplies (UPS), running ac appliances from dc power source such as automobile battery.

Single-Phase Full-Bridge Inverter


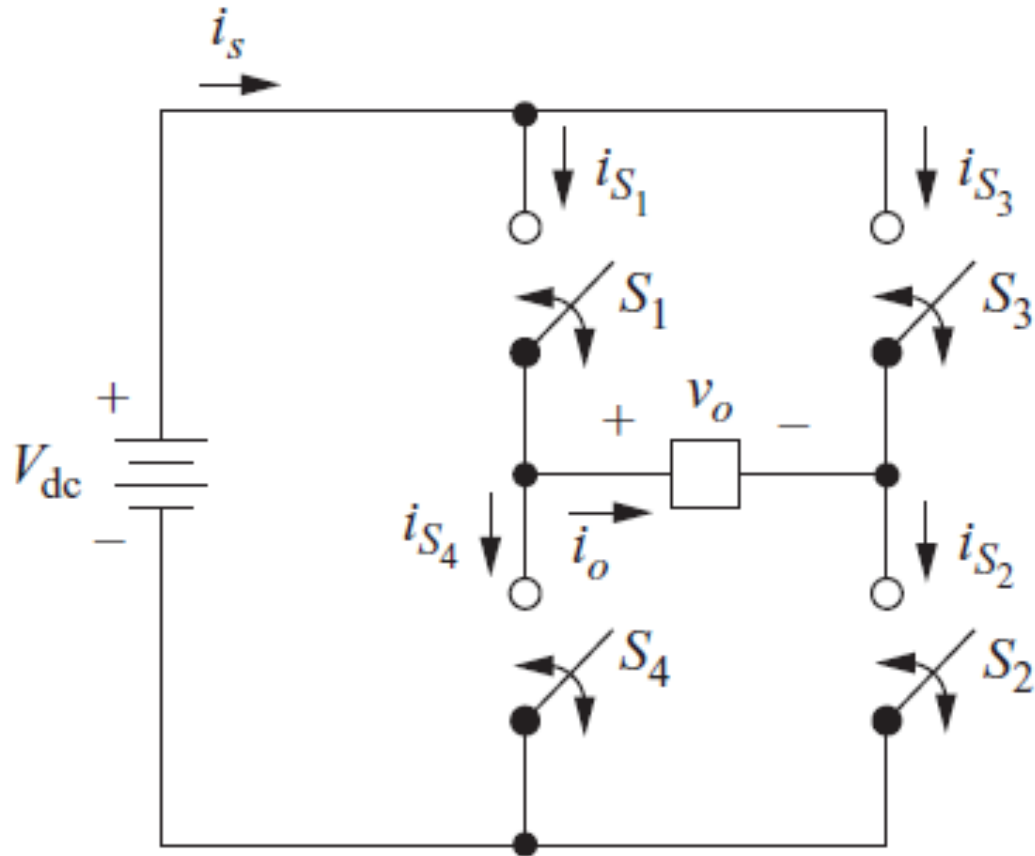


Power switches: MOSFET or IGBT


Only one switch in each leg closed at a time.

Neither S_1 & S_4 nor S_2 & S_3 should be closed at the same to avoid the source short-circuited.

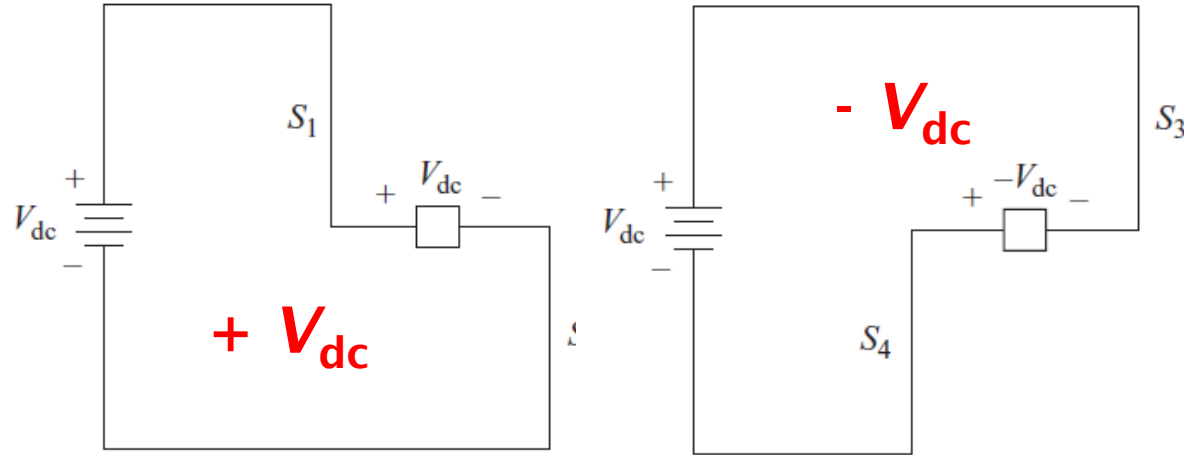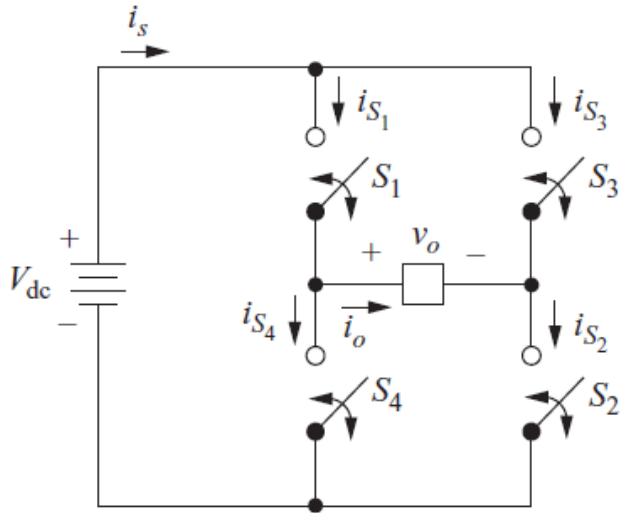Single-Phase Full-Bridge Inverter - Operation





Switches Closed	Output voltage v_o
S_1 & S_2	$+ V_{dc}$
S_3 & S_4	$- V_{dc}$
S_1 & S_3	0
S_2 & S_4	0

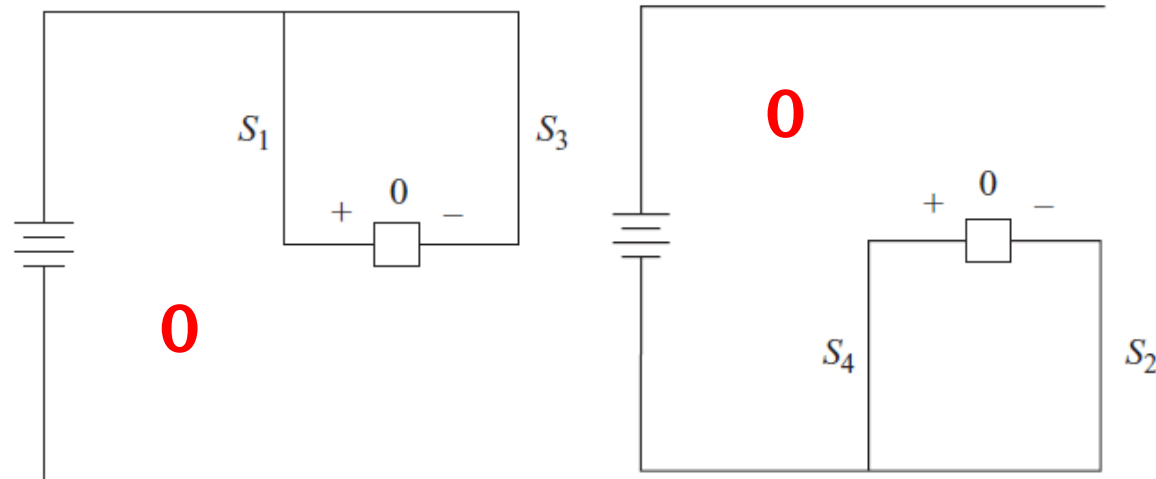

Square Wave Inverter

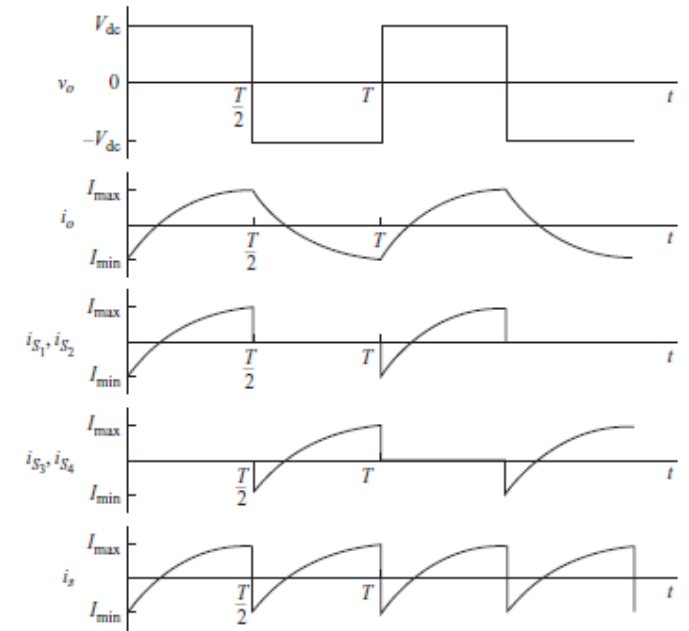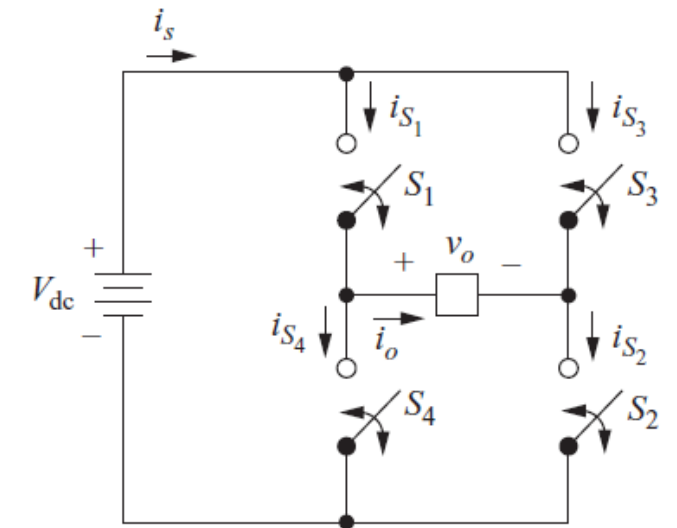- Simplest switching scheme that produces square wave output voltage.
- The current waveform in the load depends on the load components.
- Resistive load - the current waveform matches the shape of the output voltage.
- Inductive load - current that has more of a sinusoidal quality than the voltage because of the filtering property of the inductance. The switch current is bidirectional.




RL load




Square Wave Inverter – Dead time

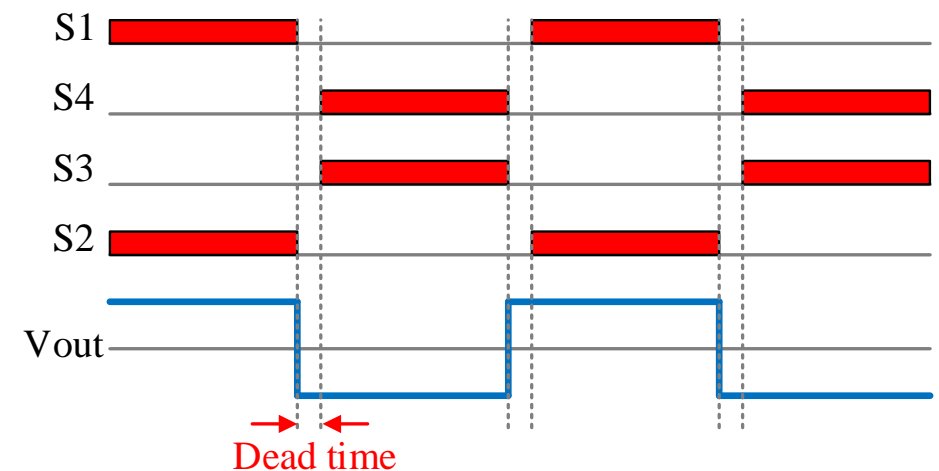- Real switches do not turn on or off instantaneously.
- Therefore, switching transition times must be accommodated in the control of the switches.
- Overlap of switch “on” times will result in a short circuit, sometimes called a **shoot-through fault**, across the dc voltage source.
- The time allowed for switching is called **blanking time** or **dead time**.




Square Wave Inverter – feedback diodes

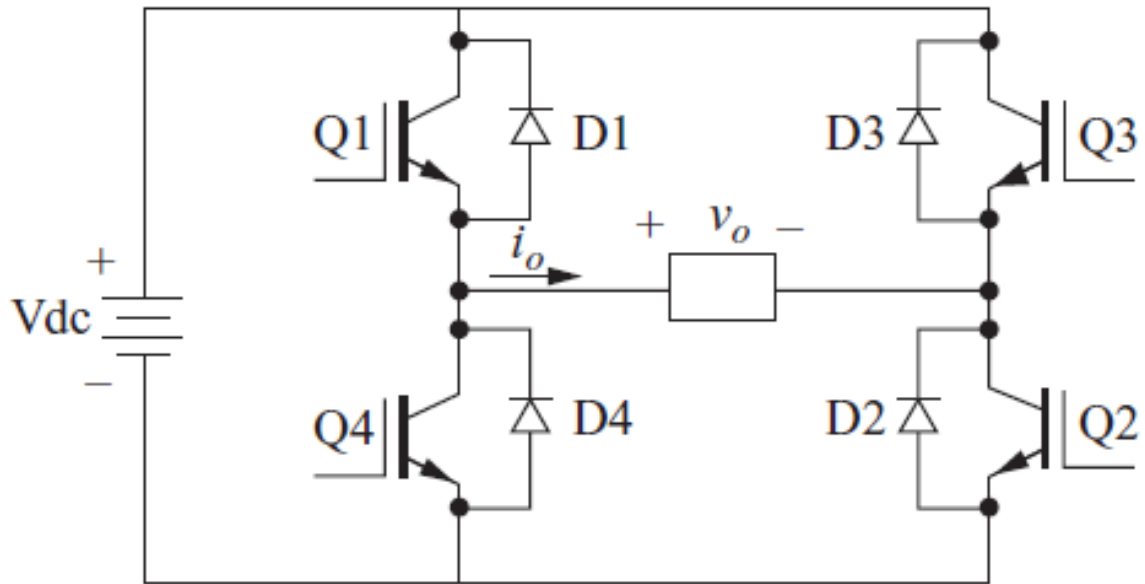For Inductive loads, the switches must be capable of both positive and negative currents.



Inductive RL load

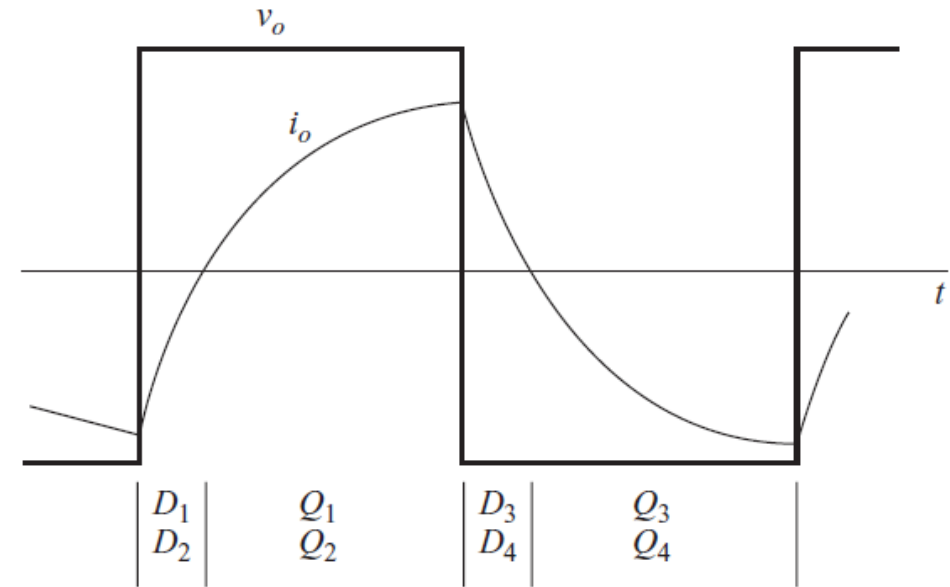

Inductive load current freewheels through antiparallel diode of switches.

Total Harmonic Distortion (THD)

THD expresses the quality of nonsinusoidal wave

Voltage

$$v_o(t) = \sum_{n=1}^{\infty} V_n \sin(n\omega_o t + \theta_n)$$

$$\text{THD} = \frac{\sqrt{\sum_{n=2}^{\infty} (V_{n,rms})^2}}{V_{1,rms}} = \frac{\sqrt{V_{rms}^2 - V_{1,rms}^2}}{V_{1,rms}}$$

Current

$$i_o(t) = \sum_{n=1}^{\infty} I_n \sin(n\omega_o t + \phi_n)$$

$$\text{THD} = \frac{\sqrt{\sum_{n=2}^{\infty} (I_{n,rms})^2}}{I_{1,rms}} = \frac{\sqrt{I_{rms}^2 - I_{1,rms}^2}}{I_{1,rms}}$$

Pure sinusoidal: THD = 0 %

High THD: More higher-order components

Square Wave Inverter - THD

The output voltage of square wave inverter consists of odd harmonics.


$$v_o(t) = \sum_{n \text{ odd}} \frac{4V_{dc}}{n\pi} \sin n\omega_0 t$$

$$V_{rms} = V_{dc} \quad V_{1,rms} = \frac{4V_{dc}}{\sqrt{2}\pi}$$

Total Harmonic Distortion


$$THD = \frac{\sqrt{V_{rms}^2 - V_{1,rms}^2}}{V_{1,rms}} = 48.3\%$$

Square wave

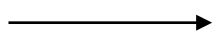

High THD

Square wave

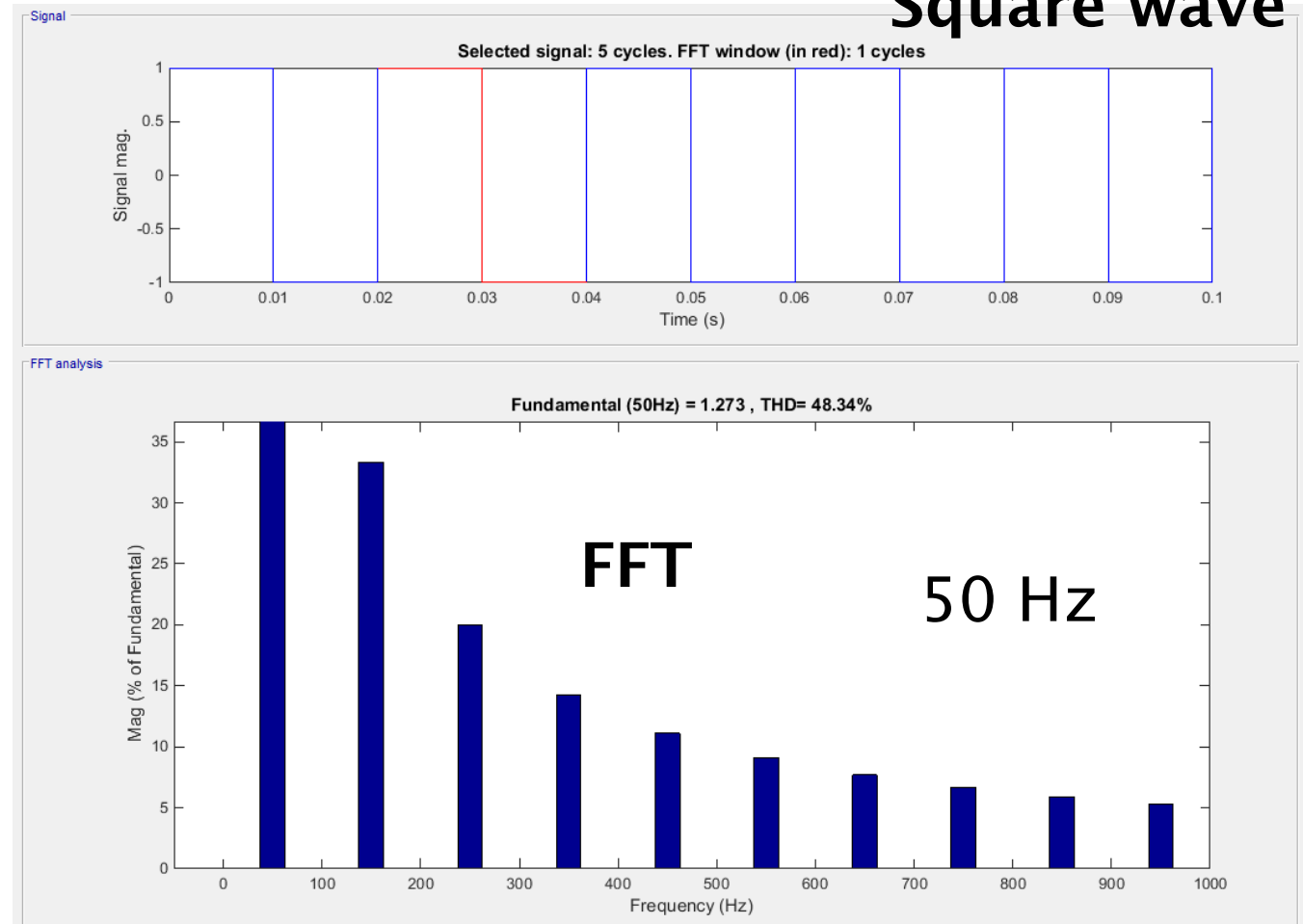

Pulse-Width Modulation (PWM)

- PWM provides a way to decrease the total harmonic distortion (THD) of load current.
- A PWM inverter output, with some filtering, can generally meet THD requirements more easily than the square wave switching scheme.
- The amplitude of the output voltage can be controlled with the modulating waveforms.
- Advantages of PWM: (1) decrease harmonics to reduce filter requirements. (2) control of the output voltage amplitude.

Sinusoidal Pulse-Width Modulation (SPWM)

Control of the switches for sinusoidal PWM (SPWM) output requires:




- (1) Reference signal, sometimes called a modulating or control signal, which is a sinusoid in this case
- (2) Carrier signal, which is a triangular wave that controls the switching frequency.

Two types of SPWM switching schemes

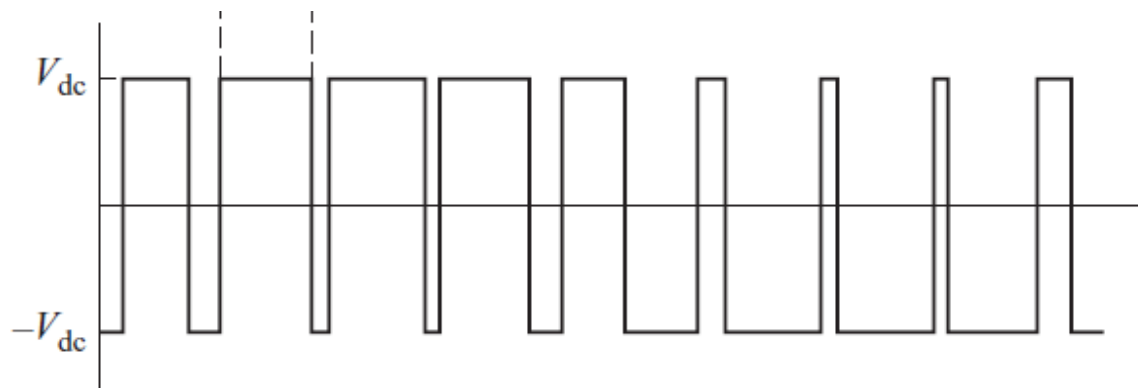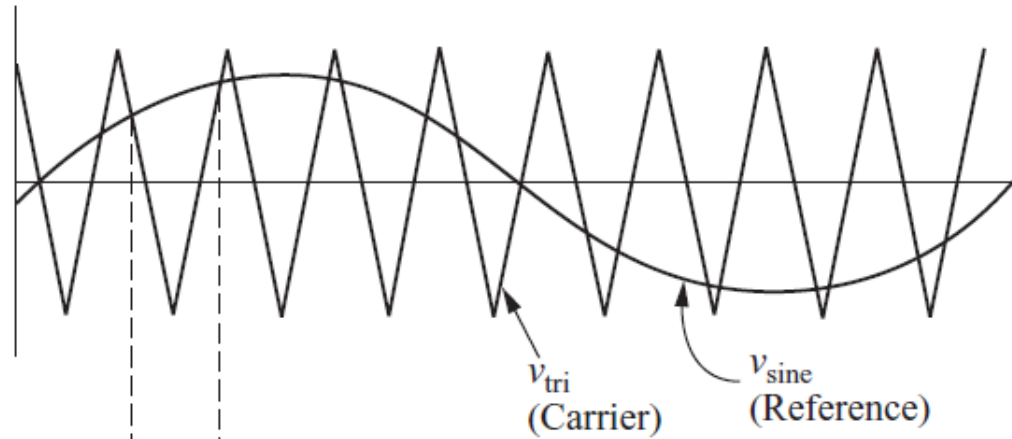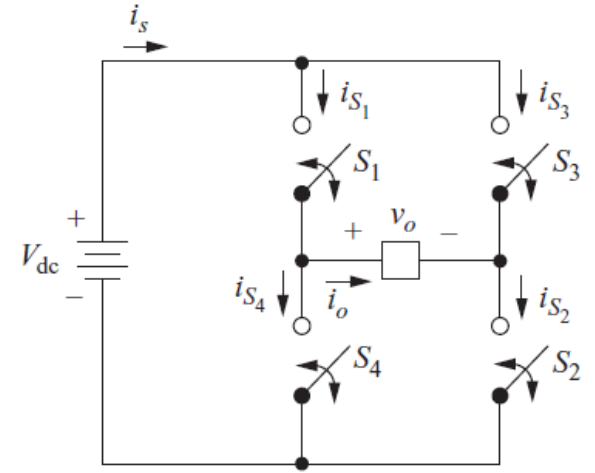- a. Bipolar switching
- b. Unipolar switching

SPWM - Bipolar switching

One reference signal and one carrier signal for full-bridge.



S_1 and S_2 are on when $v_{\text{sine}} > v_{\text{tri}}$

$$(v_o = +V_{dc})$$


S_3 and S_4 are on when $v_{\text{sine}} < v_{\text{tri}}$.

$$(v_o = -V_{dc})$$

SPWM - Bipolar switching



The inductive load current rises and falls linearly with time at a constant rate as the applied voltage is either $+V_{dc}$ or $-V_{dc}$.

$$di/dt = v_o/L$$

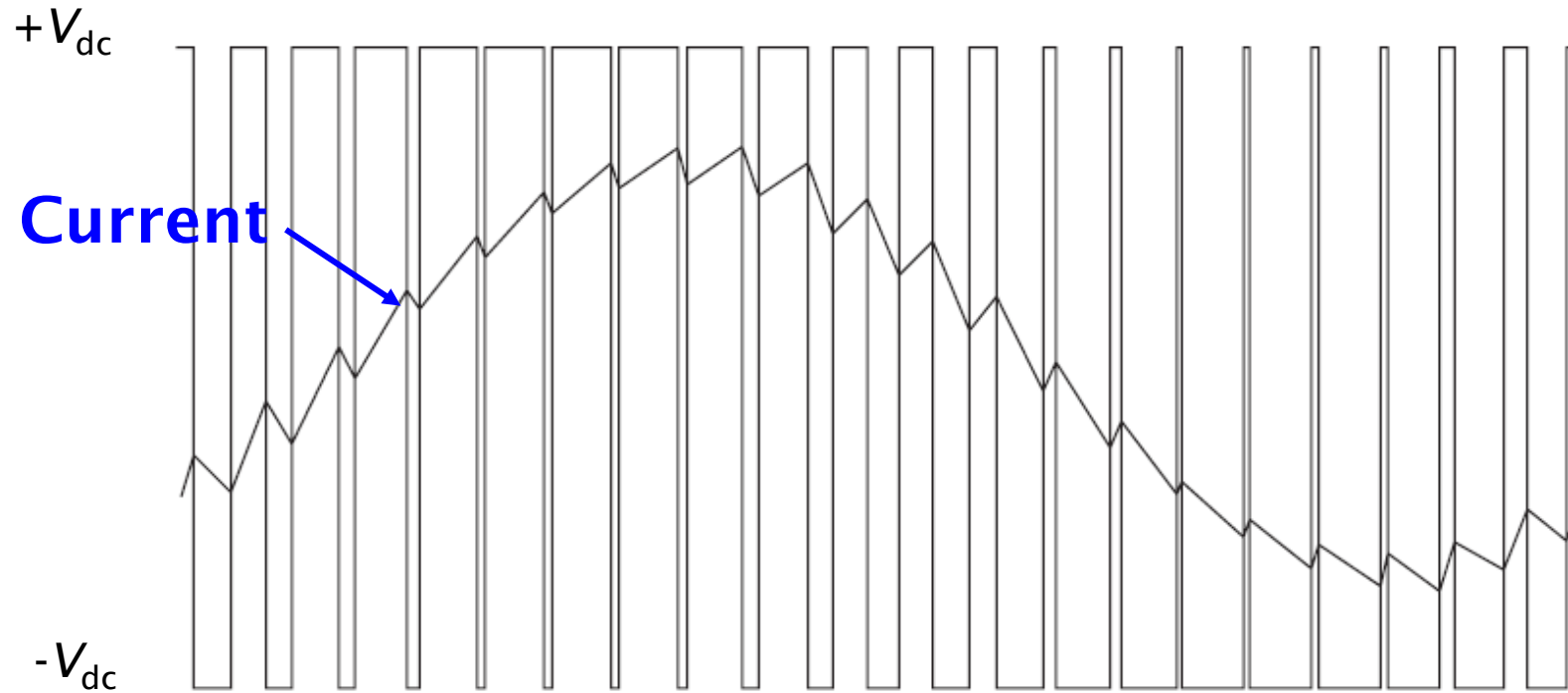

SPWM - Unipolar switching

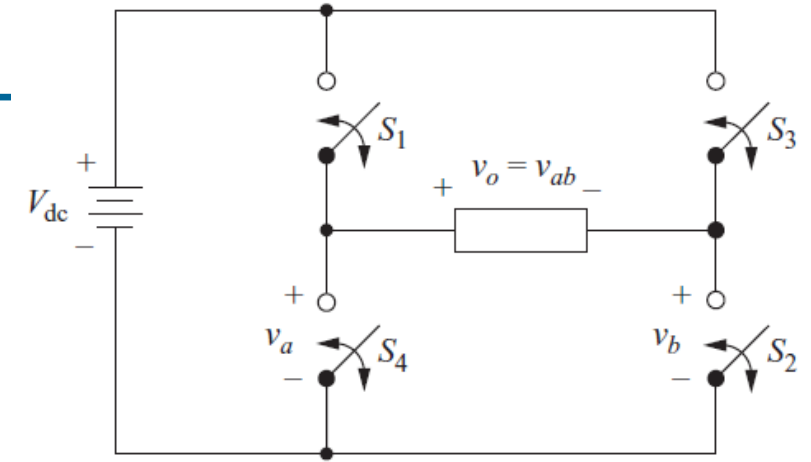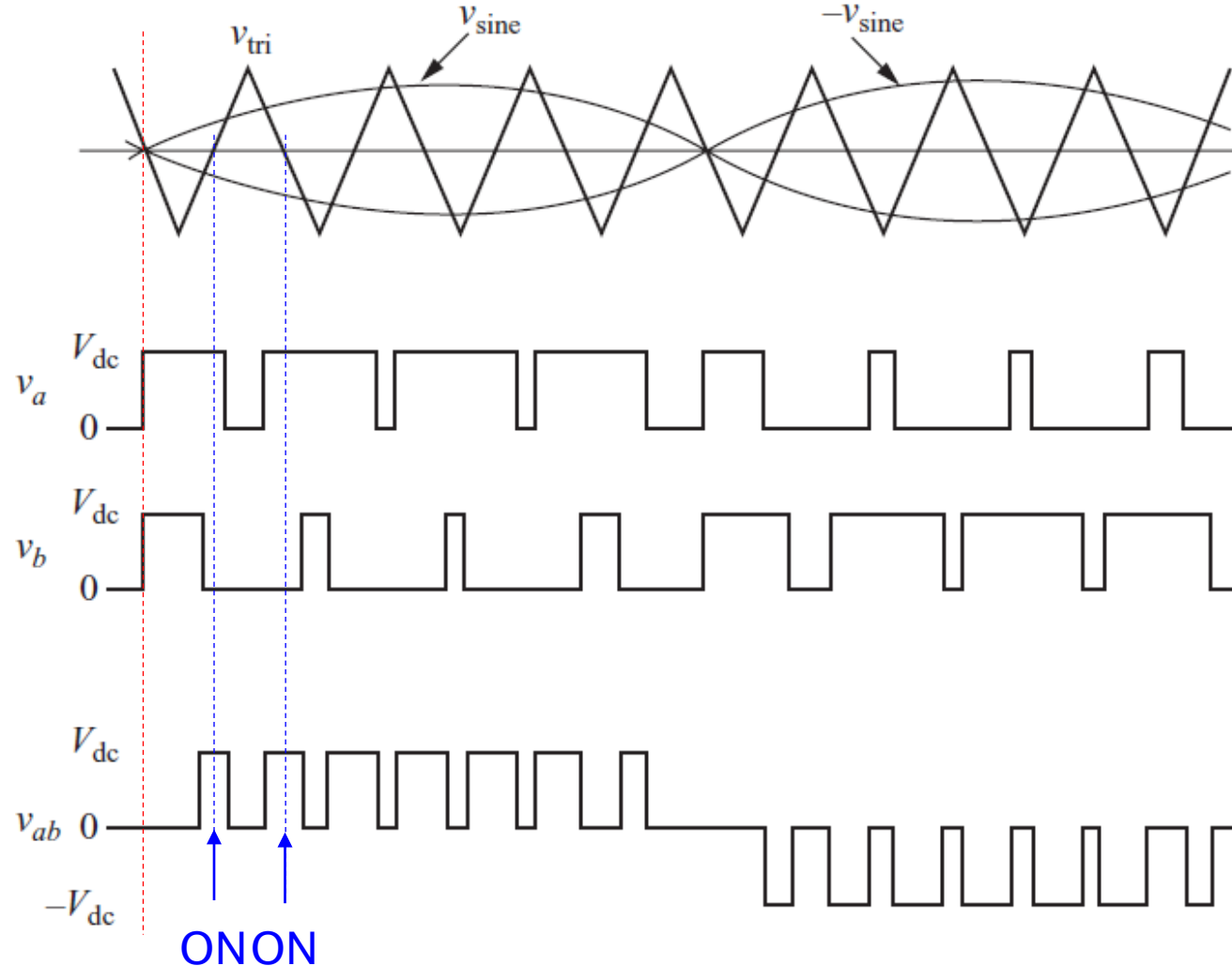Two reference signal and one carrier signal.



- v_{sine} for controlling S_1 & S_4 , and $-v_{sine}$ for controlling S_2 & S_3 .

S_1 is on when $v_{sine} > v_{tri}$
 S_4 is on when $v_{sine} < v_{tri}$
 S_3 is on when $-v_{sine} > v_{tri}$
 S_2 is on when $-v_{sine} < v_{tri}$

PWM – Modulation ratio


Frequency modulation ratio m_f

$$m_f = \frac{f_{\text{carrier}}}{f_{\text{reference}}} = \frac{f_{\text{tri}}}{f_{\text{sine}}}$$

Increasing m_f increases the frequencies at which the harmonics occur.



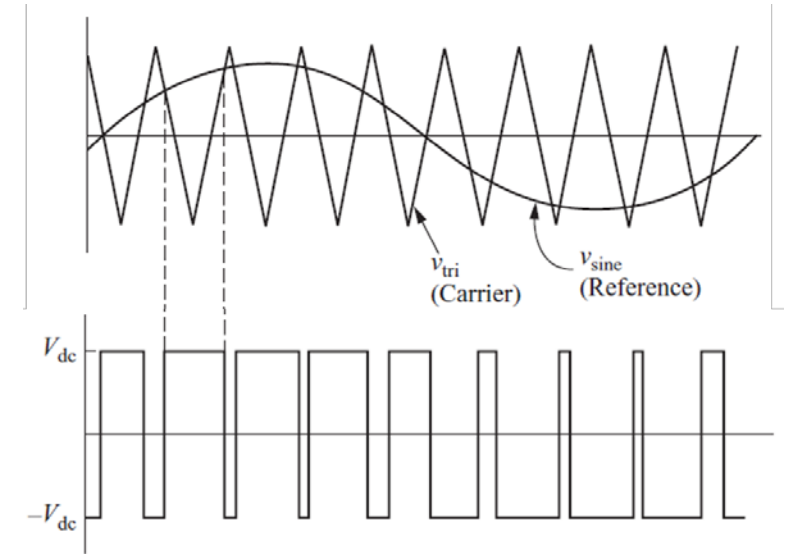A simple low-pass filter is enough to remove, but switching losses are high.



Amplitude modulation ratio m_a

$$m_a = \frac{V_{m, \text{reference}}}{V_{m, \text{carrier}}} = \frac{V_{m, \text{sine}}}{V_{m, \text{tri}}}$$

If $m_a \leq 1$


$$V_1 = m_a V_{\text{dc}}$$

The amplitude of the fundamental component is thus controlled by m_a .





- Good to compensate unregulated dc supply voltage.
- m_a can be varied to change the amplitude of the output.

Three-phase Inverter

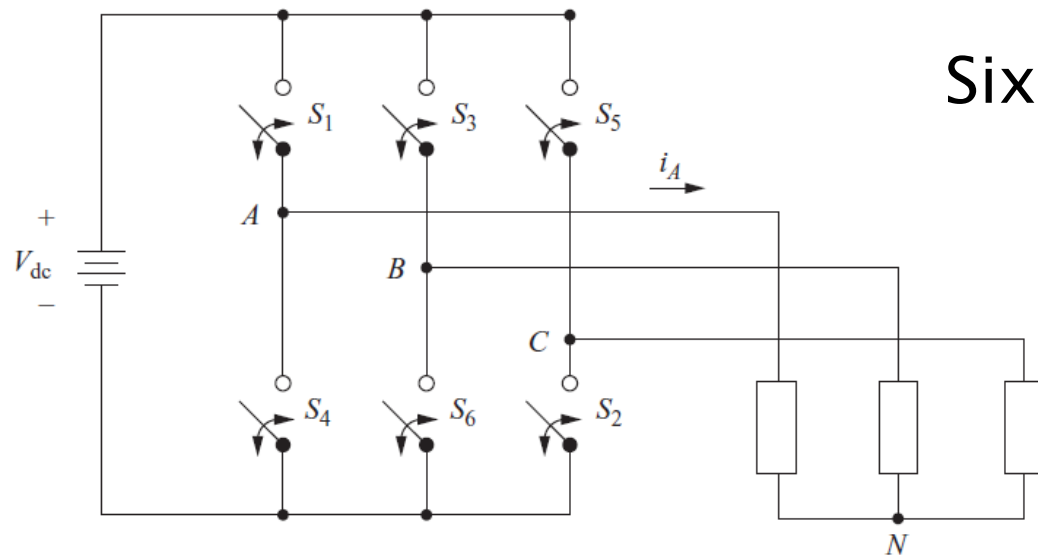


Six step operation


Each switch has a duty ratio of 50%.

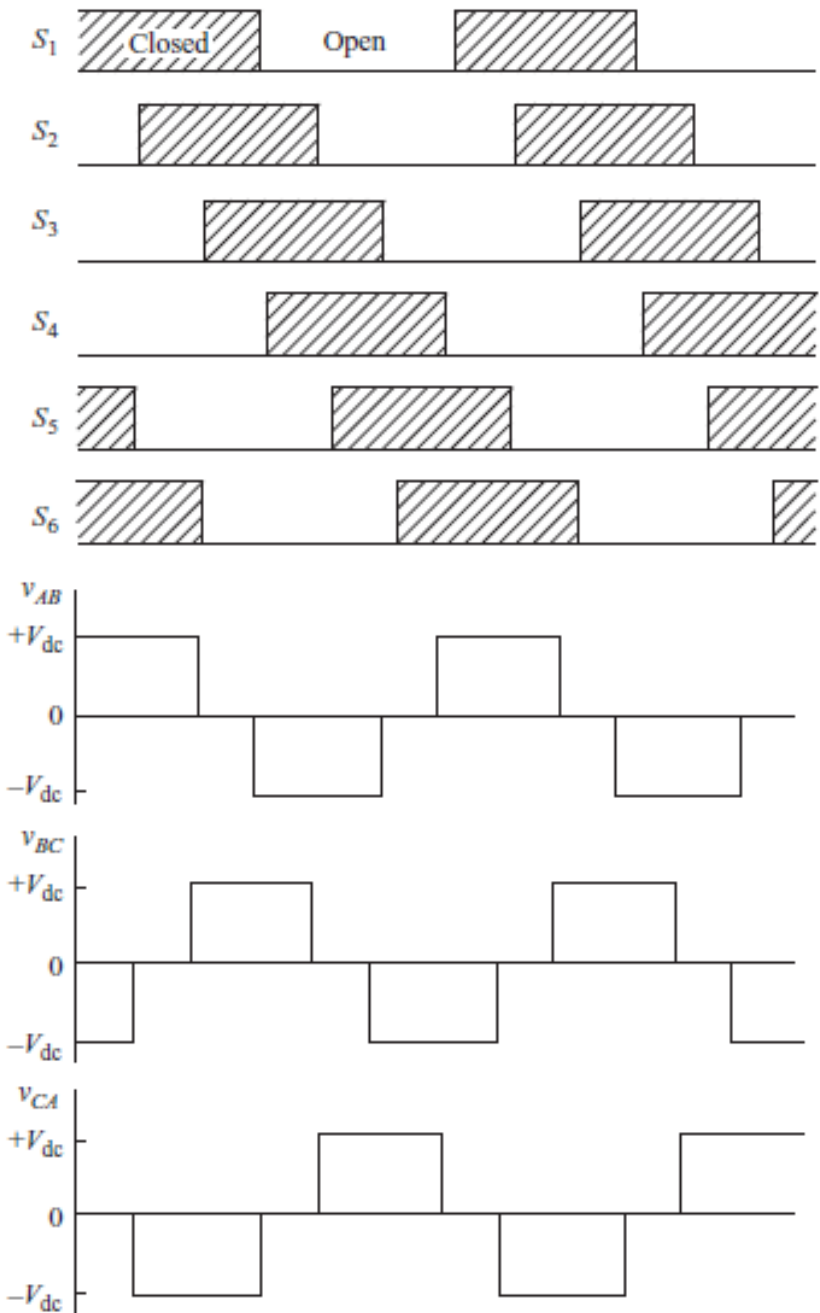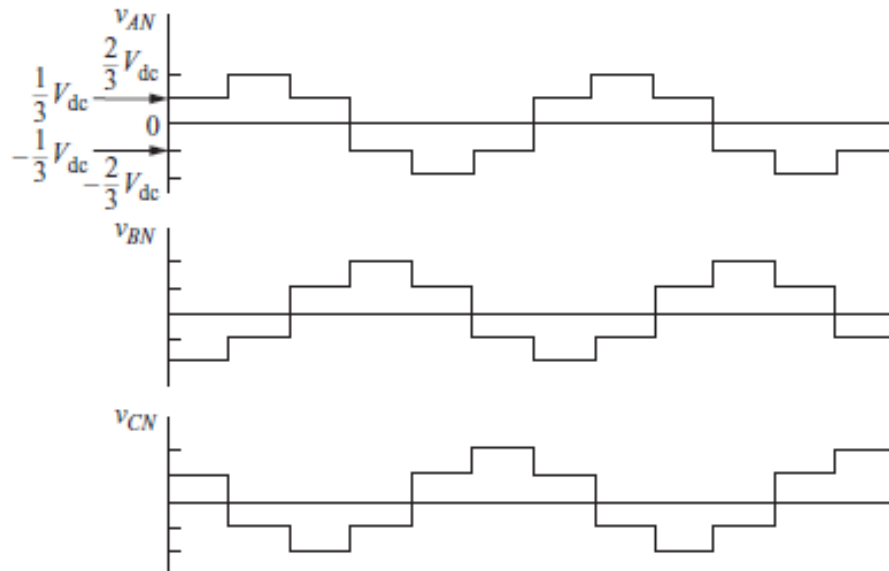

Three-phase SPWM

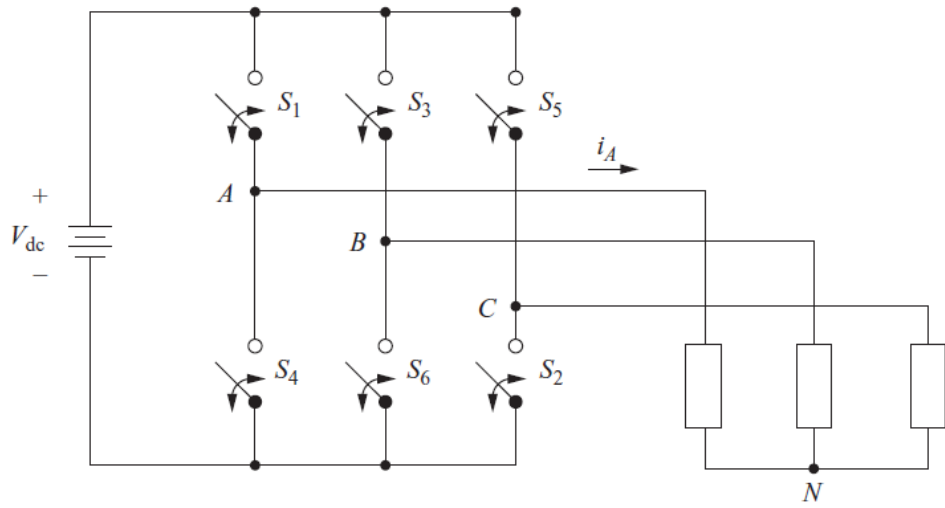


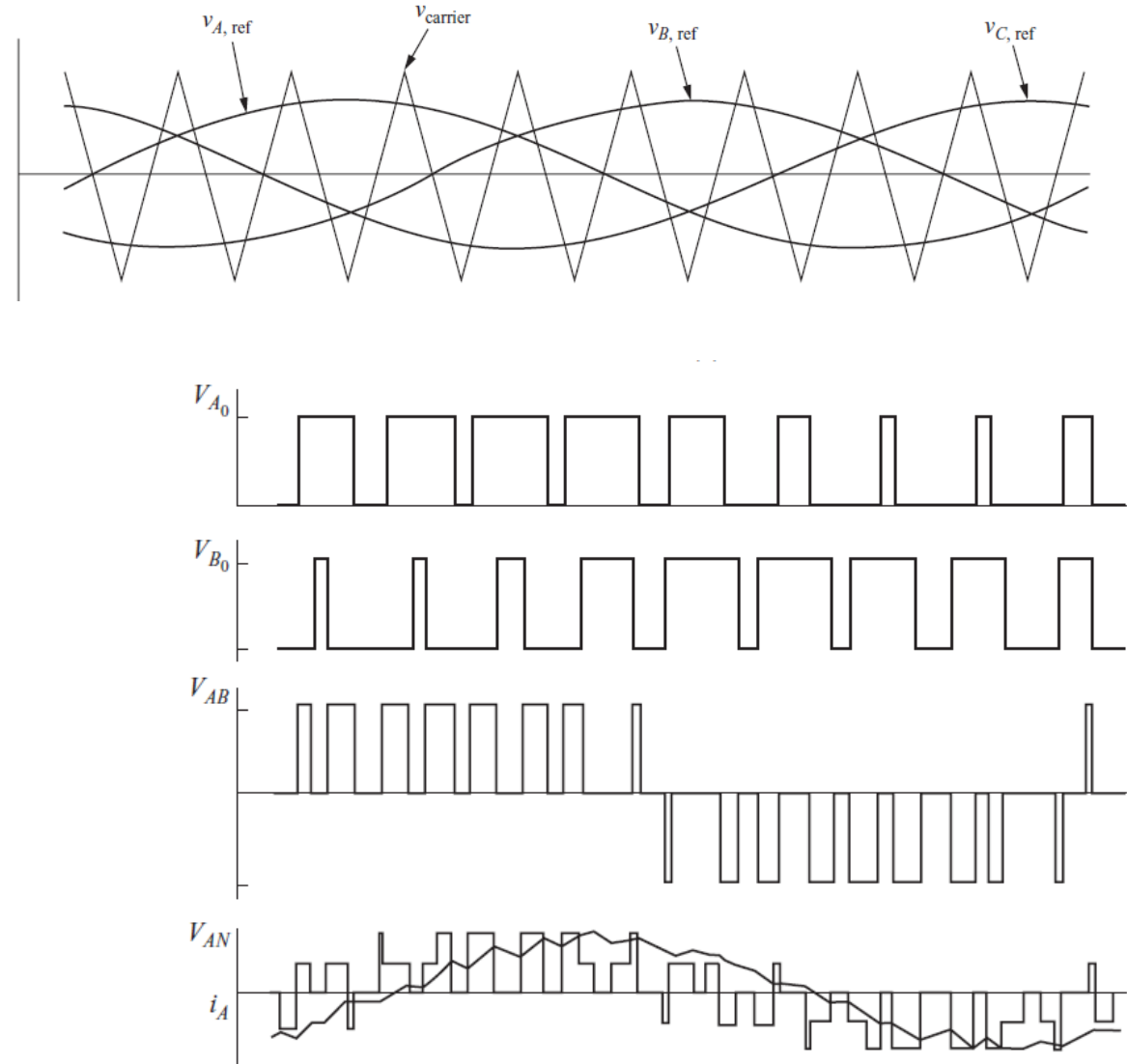S_1 is on when $v_a > v_{tri}$
 S_4 is on when $v_a < v_{tri}$
 S_3 is on when $v_b > v_{tri}$
 S_6 is on when $v_b < v_{tri}$
 S_5 is on when $v_c > v_{tri}$
 S_2 is on when $v_c < v_{tri}$



Three-phase SPWM

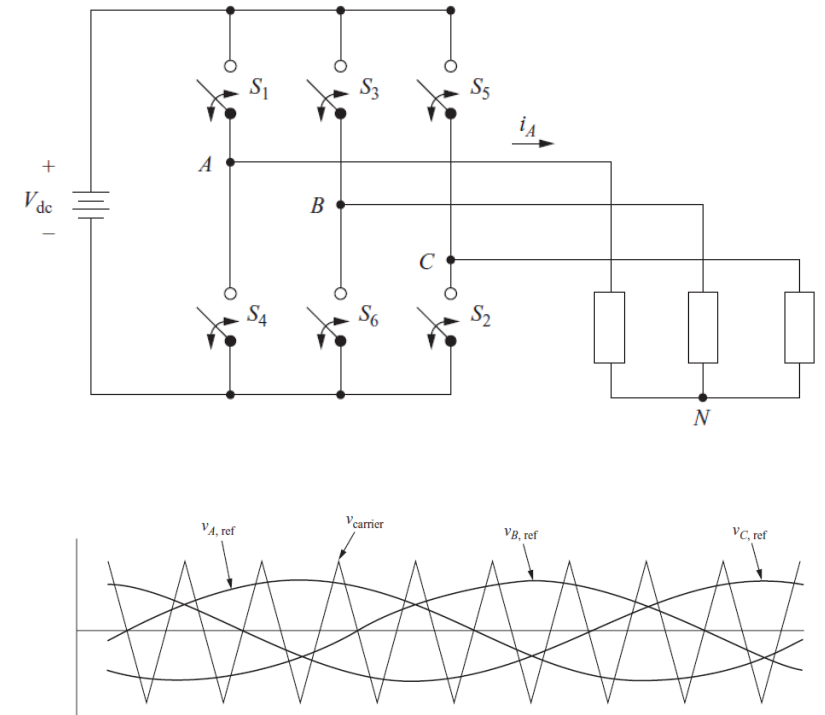- Each switch is controlled by comparing a sinusoidal reference wave with a triangular carrier wave.
- The three reference sinusoids are 120° apart to produce a balanced three-phase output.
- The fundamental frequency of the output is the same as that of the reference wave, and the amplitude of the output is determined by the modulation index, m_a .



Summary - Inverter

- Inverters convert a DC voltage supply to an AC voltage.
- Single-Phase Full-Bridge Inverter consists of 4 power switches to generate square waveform.
- Pulse-width modulation (PWM) can decrease the total harmonic distortion (THD) of load current.
- Three phase Inverter consists of 6 power switches to convert DC to three phase AC power.