

SEMESTER TWO EXAMINATIONS 2019/20

POWER CIRCUITS AND TRANSMISSION

Duration 120 mins (2 hours)

This paper contains 3 questions

Answer all questions.

Section A carries 33% of the total marks for the exam paper.

Section B carries 33% of the total marks for the exam paper.

Section C carries 33% of the total marks for the exam paper.

Only University approved calculators may be used.

A foreign language dictionary is permitted ONLY IF it is a paper version of a direct 'Word to Word' translation dictionary AND it contains no notes, additions or annotations.

7 page examination paper (+ 1 page formula sheet)

SECTION A

Answer all questions in this section

Question 1:

- (a) Consider the circuit shown in Figure 1. Using mesh analysis, find the values of i_1 , i_2 , and i_3 when $V_1 = 10 \text{ V}$, $I_0 = 1 \text{ A}$, $R_1 = R_2 = 5 \Omega$, $R_3 = 7 \Omega$, and $R_4 = 3 \Omega$. [7 marks]

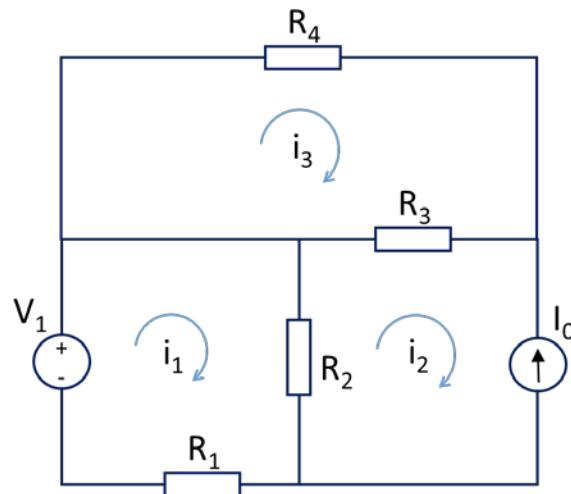


Fig. 1. The circuit for question (a)

- (b) Using the Millman's (parallel generator) theorem, find the voltage V_{AB} across the node A and B, in the circuit shown in Figure 2. $V_1 = 5 \text{ V}$, $V_2 = 10 \text{ V}$, $R_1 = R_2 = 5 \Omega$, $R_3 = 20 \Omega$. [5 marks]

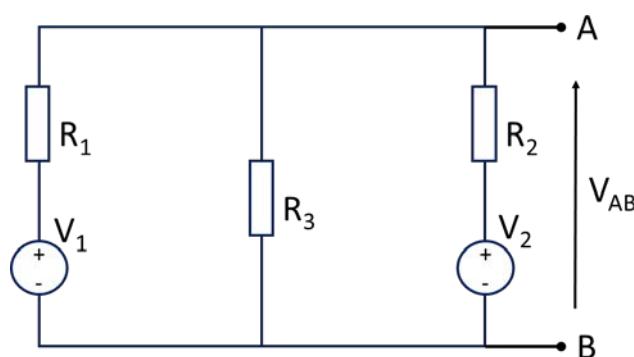


Fig. 2. The circuit for question (b)

- (a) Consider the circuit shown in Figure 1. Using mesh analysis, find the values of i_1 , i_2 , and i_3 when $V_1 = 10 \text{ V}$, $I_0 = 1 \text{ A}$, $R_1 = R_2 = 5 \Omega$, $R_3 = 7 \Omega$, and $R_4 = 3 \Omega$. [7 marks]


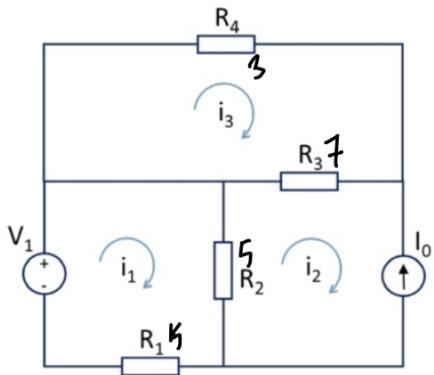


Fig. 1. The circuit for question (a)

Show circuit

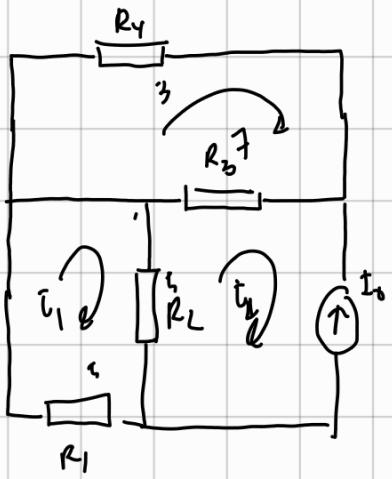

$$i_2 = -I_0$$


$$= -1$$

$$i_1 R_1 + (i_1 - i_2) R_2 = 0$$

$$5i_1 + 5i_1 + 5 = 0$$

$$10i_1 = -5$$

$$i_1 = -0.5$$

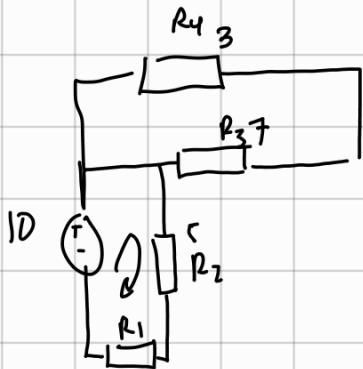

$$i_3 R_4 + (i_3 - i_2) R_3 = 0$$

$$3i_3 + (i_3 + 1) 7 = 0$$

$$3i_3 + 7i_3 + 7 = 0$$

$$10i_3 = -7$$

$$i_3 = \frac{-7}{10} A$$

$$i_1 R_2 + i_1 R_1 = V$$

$$i_1 (5) + i_1 (5) = 10$$

$$10i_1 = 10$$

$$i_1 = 1$$

$$i_1 = 1 + -0.5 A$$

$$= 0.5 A$$

- (b) Using the Millman's (parallel generator) theorem, find the voltage V_{AB} across the node A and B, in the circuit shown in Figure 2. $V_1 = 5 \text{ V}$, $V_2 = 10 \text{ V}$, $R_1 = R_2 = 5 \Omega$, $R_3 = 20 \Omega$.
[5 marks]

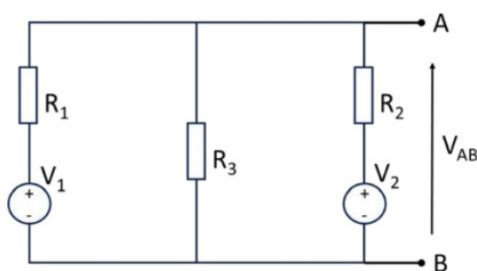


Fig. 2. The circuit for question (b)

$$\begin{aligned} Y_1 &= \frac{1}{R_1} & Y_2 &= \frac{1}{R_2} & Y_3 &= \frac{1}{R_3} \\ &= \frac{1}{5} & &= \frac{1}{5} & &= \frac{1}{20} \\ &= 0.2 \text{ A}^{-1} & &= 0.2 \text{ A}^{-1} & &= 0.05 \text{ A}^{-1} \end{aligned}$$

$$\begin{aligned} V_{AB} &= \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3} \\ &= \frac{5(0.2) + 10(0.2) + 0(0.05)}{0.2 + 0.2 + 0.05} \\ &= \frac{20}{3} \\ &= 6.667 \text{ V} \end{aligned}$$

- (c) Consider the two-port network in Figure 3. There are two impedances Z , and two admittances Y connected as shown in the network. Derive the (A,B,C,D) representation of this two-port network. Please also write the image impedances Z_{l1} and Z_{l2} in terms of A,B,C,D .

[8 marks]

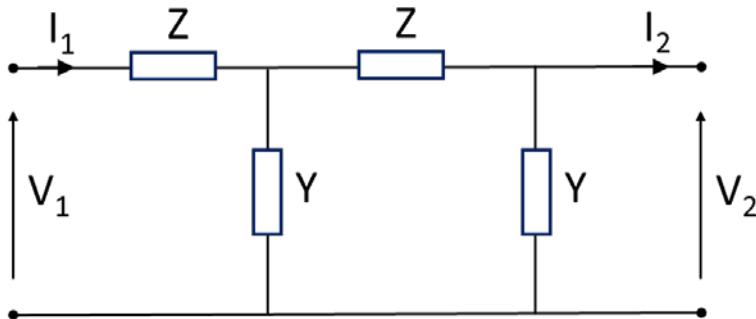


Fig. 3. The circuit for question (c)

- (d) Starting from the (A,B,C,D) representation of a two-port network, derive its equivalent Y-representation. Show clearly how you arrived at your conclusions.

[6 marks]

- (e) Describe what is symmetry of a two-port network? Write down the equation, in terms of the (A,B,C,D) representation, derived from a reciprocal and symmetrical two-port network. Write down the iterative impedance Z_{it} of a symmetrical two-port network.

[7 marks].

TURN OVER

SECTION B

- (c) Consider the two-port network in Figure 3. There are two impedances Z , and two admittances Y connected as shown in the network. Derive the (A, B, C, D) representation of this two-port network. Please also write the image impedances Z_{11} and Z_{22} in terms of A, B, C, D .

[8 marks]


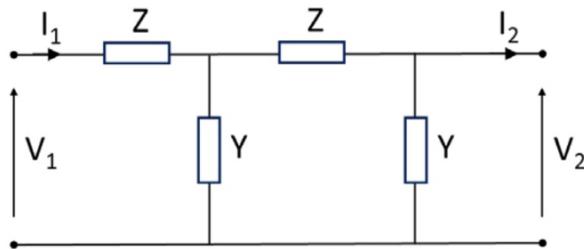


Fig. 3. The circuit for question (c)

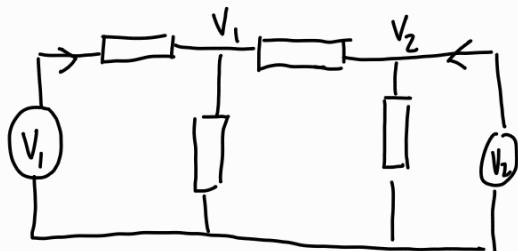

$$I_1 = \frac{V_1}{Z} + V_1 Y + \frac{V_1 - V_2}{Z}$$

$$I_2 = V_2 Y + \frac{V_2 - V_1}{Z}$$

$$I_2 Z = V_2 Y Z + V_2 - V_1$$

$$\begin{aligned} V_1 &= V_2 Y Z + V_2 - I_2 Z \\ &= V_2 (Y Z + 1) - I_2 Z \end{aligned}$$

$$\begin{aligned} I_1 &= V_1 \left(\frac{2}{Z} + Y \right) - \frac{V_2}{Z} \\ &= (V_2 (Y Z + 1) - I_2 Z) \left(\frac{2}{Z} + Y \right) - \frac{V_2}{Z} \\ &= \frac{2V_2}{Z} (Y Z + 1) - 2I_2 + V_2 Y (Y Z + 1) - I_2 Y Z - \frac{V_2}{Z} \\ &= \underline{\underline{2V_2 Y}} + \underline{\underline{\frac{2V_2}{Z}}} - 2I_2 + \underline{\underline{V_2 Y^2 Z}} + \underline{\underline{V_2 Y}} - \underline{\underline{I_2 Y Z}} - \underline{\underline{\frac{V_2}{Z}}} \\ &= 3V_2 Y + \frac{V_2}{Z} + V_2 Y^2 Z - 2I_2 - I_2 Y Z \\ &= V_1 \left(3Y + \frac{1}{Z} + Y^2 Z \right) + I_2 (-2 - Y Z) \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} Y_{21} + 1 & -z \\ 3Y + \frac{1}{Z} + Y^2 Z & -2 - Y_Z \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

ABCD parameter

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} Y_{21} + 1 & z \\ 3Y + \frac{1}{Z} + Y^2 Z & 2 + Y_Z \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$V_2 = \frac{I_1 - DI_2}{C}$$

$$V_1 = A \left(\frac{I_1 - DI_2}{C} \right) + BI_2$$

$$= \frac{A}{C} I_1 - \frac{AD}{C} I_2 + BI_2$$

$$= \frac{A}{C} I_1 + \frac{BC - AD}{C} I_2$$

$$Z_{11} = \frac{A}{C} \quad Z_{12} = \frac{BC - AD}{C}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = \frac{V_2 - Z_{22} I_2}{Z_{21}}$$

- (d) Starting from the (A, B, C, D) representation of a two-port network, derive its equivalent Y-representation. Show clearly how you arrived at your conclusions.

[6 marks]

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$I_2 = \frac{AV_2 - V_1}{B}$$

$$I_1 = CV_2 - D\left(\frac{AV_2 - V_1}{B}\right)$$

$$= CV_2 - \frac{AD}{B}V_2 + \frac{D}{B}V_1$$

$$= \frac{D}{B} + \frac{CB - AD}{B}V_2$$

Y-parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$I_2 = \frac{V_1}{B} - \frac{A}{B}V_2$$

$$Y_{11} = \frac{D}{B} \quad Y_{12} = -\frac{(AD - CB)}{D} \quad Y_{21} = -\frac{1}{B} \quad Y_{22} = \frac{A}{B}$$

$$Y = \begin{bmatrix} \frac{D}{B} & \frac{CB - AD}{D} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$$

- (e) Describe what is symmetry of a two-port network? Write down the equation, in terms of the (A, B, C, D) representation, derived from a reciprocal and symmetrical two-port network. Write down the iterative impedance Z_{it} of a symmetrical two-port network.

[7 marks].

A symmetry of a two-port network is when $A=D$.

Reciprocal is when $AD - BC = 1$ - (1)

Symmetrical is when $A=D$ - (2)

$$\text{So } D^2 - BC = 1$$

Iterative Impedance

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} D & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = DV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

Z -parameter

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = \frac{I_1 - DI_2}{C} = \frac{I_1}{C} - \frac{D}{C} I_2$$

$$V_1 = D\left(\frac{I_1 - DI_2}{C}\right) + BI_2$$

$$= \frac{D}{C} I_1 - \frac{D^2}{C} I_2 + BI_2$$

$$= \frac{D}{C} I_1 + \frac{BC - D^2}{C} I_2$$

$$Z_{11} = \frac{D}{C} \quad Z_{12} = \frac{BC - D^2}{C} = \frac{-D^2 - BC}{C} = -\frac{1}{C}$$

$$Z_{21} = \frac{1}{C} \quad Z_{22} = -\frac{D}{C}$$


$$Z_{1t} = \frac{A + D - 2B}{A + D + 2B})$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{A Z_{12} + B}{C Z_{12} + D}$$

$$\frac{V_2}{I_2} = D Z_{11} + B$$

Iterative impedance Z_{1t} of a symmetrical TPN:

$$Z_{11} = Z_{12} = \sqrt{\frac{B}{C}}$$

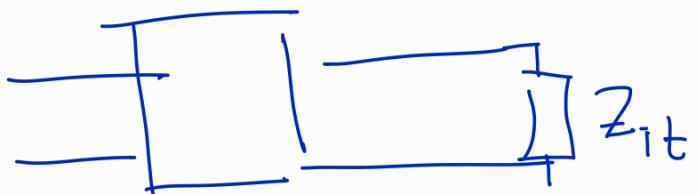

$$Z_{1t} = Z_{1n} = \frac{V_1}{I_1}$$

Answer all questions in this section

Question 2:

- a) **Explain** why there are *distortions* in signal transmission in lossy transmission lines. **Explain** what relation among the line parameters should hold to correct such distortions and why such a relation corrects the distortions.
[6 marks]
- b) A lossless transmission line has the following per-unit-length parameters: $L = 0.5 \mu H/m$, $C = 200 pF/m$. **Calculate** the *propagation constant* and *characteristic impedance*, *wavelength* and the *phase velocity* for this lossless line at 800 MHz.
[5 marks]
- c) **Calculate** the *propagation constant* and *characteristic impedance* of the line in section (b) at frequency 800 MHz for the case when the line is lossy with, $R = 4.0 \Omega/m$ and $G = 0.02 S/m$. If the line is 30 cm long, **Calculate** the *attenuation* in dB.
[6 marks]
- d) A coaxial transmission line with the characteristic impedance of 75Ω has a length of 2.0 cm and is terminated with a load impedance of $37.5 + j75\Omega$. If the line has permeability of free space and the relative permittivity of 2.56 and the frequency is 3.0 GHz, **find** the *input impedance* of the line, the *reflection coefficient* at the load, the *reflection coefficient* at the input and the *SWR* on the line.
[9 marks]
- e) Let Z_{sc} be the input impedance of a length of coaxial line when one end is short-circuited, and let Z_{oc} be the input impedance

of the line when one end is open-circuited. **Derive** an expression for the *characteristic impedance* of the cable in terms of Z_{sc} and Z_{oc} .

[7 marks]

TURN OVER

SECTION C

Answer all questions in this section

Question 3:

A balanced, star-connected three-phase voltage source is connected to an unbalanced star-connected three-phase load as shown in the Figure 4 below:

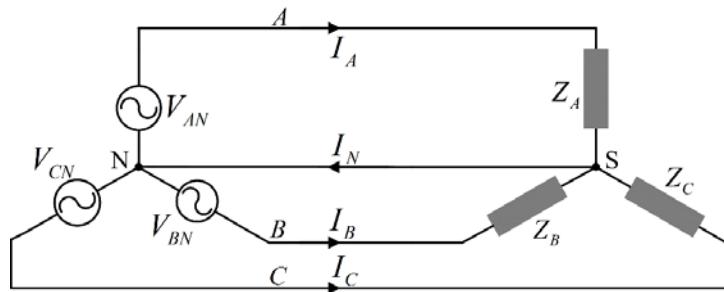


Fig. 4. The circuit for question 3

The phase voltage phasors and the loads are:

$$\begin{array}{ll} V_{AN} = 230 \angle 0^\circ \text{ V (rms)} & Z_A = 10 \angle 0^\circ \Omega \\ V_{BN} = 230 \angle -120^\circ \text{ V (rms)} & Z_B = 15 \angle 45^\circ \Omega \\ V_{CN} = 230 \angle 120^\circ \text{ V (rms)} & Z_C = 20.02 \angle 29.81^\circ \Omega \end{array}$$

- (a) Given that **total complex power** (S_{tot}) consumed by the three-phase load is $10772 \angle 20.7^\circ \text{ VA}$, **calculate** phase currents I_A , I_B , I_C and neutral return current I_N . **Calculate** complex powers S_A , S_B , S_C for each load. **Prove** that the phase impedance $Z_C = 17.37 + 9.95i \text{ (} 20.02 \angle 29.81^\circ \text{)} \Omega$. Show full workings.

Hint: complex conjugate is required for power calculations.

[16 marks]

- (b) Neutral current, I_N can be reduced by connecting an impedance, Z_N between the two neutral terminals N and S. **determine** Z_N such that neutral current reduces to $1 \angle 0^\circ \text{ A}$. **Calculate** the neutral line voltage V_{SN} . Show full workings

[6 marks]

- (c) Use Millmans theorem to **calculate** the voltage between the two neutral terminals N and S for the case where the neutral

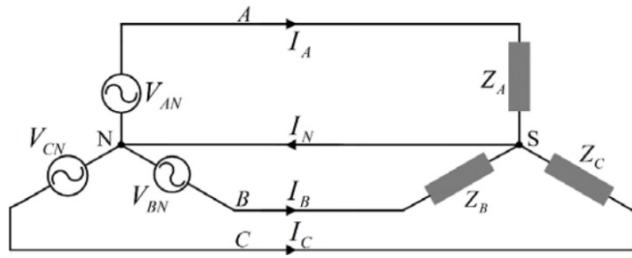


Fig. 4. The circuit for question 3

The phase voltage phasors and the loads are:

$$\begin{aligned}V_{AN} &= 230 \angle 0^\circ \text{ V (rms)} & Z_A &= 10 \angle 0^\circ \Omega \\V_{BN} &= 230 \angle -120^\circ \text{ V (rms)} & Z_B &= 15 \angle 45^\circ \Omega \\V_{CN} &= 230 \angle 120^\circ \text{ V (rms)} & Z_C &= 20.02 \angle 29.81^\circ \Omega\end{aligned}$$

- (a) Given that **total complex power** (S_{tot}) consumed by the three-phase load is $10772 \angle 20.7^\circ$ VA, **calculate** phase currents I_A , I_B , I_C and neutral return current I_N . **Calculate** complex powers S_A , S_B , S_C for each load. **Prove** that the phase impedance $Z_C = 17.37 + 9.95i (20.02 \angle 29.81^\circ)$ Ω. Show full workings.

Hint: complex conjugate is required for power calculations.

[16 marks]

$$I_A = \frac{V_{AN}}{Z_A} = \frac{\sqrt{2} (230 \angle 0^\circ)}{10} = 32.527 \text{ A}$$

$$I_B = \frac{V_{BN}}{Z_B} = \frac{\sqrt{2} (230 \angle -120^\circ)}{15 \angle 45^\circ} = 21.6846 \angle -165^\circ \text{ A} \\ = -20.946 - j 5.6124$$

$$I_C = \frac{V_{CN}}{Z_C} = \frac{\sqrt{2} (230 \angle 120^\circ)}{20.02 \angle 29.81} = 16.247 \angle 90.19^\circ \text{ A} \\ = -0.0539 + j 16.247 \text{ A}$$

$$I_N = I_A + I_B + I_C \\ = 32.527 + 21.684 \angle -165^\circ + 16.247 \angle 90.19^\circ \\ = 15.68 \angle 42.7^\circ$$

$$S = \sqrt{I^*}$$

$$S_A = \sqrt{2} (230 \angle 0^\circ) (32.527) \\ = 10580.02864$$

$$S_A = \frac{(230 \angle 0^\circ) (32.527)}{\sqrt{2}} \\ = 5290.014$$

$$S_B = \sqrt{2} (230 \angle 120) (-20.946 + j5.6124)$$

$$= 7053.421 \angle 45^\circ \div 2$$

$$= 3526.7105 \angle 45^\circ$$

$$S_C = \sqrt{2} (230 \angle 120) (-0.0539 - j16.247)$$

$$= 5284.676 \angle 29.81^\circ \div 2$$

$$= 2642.338 \angle 29.81^\circ$$

$$\text{Total } S_A + S_B + S_C$$

$$= 5290.014 + 3526.7105 \angle 45^\circ + 2642.338 \angle 29.81^\circ$$

$$= 10771.8 \angle 20.7$$

$\sqrt{S_N}$:


$$54.463 \angle 63.39^\circ$$

$$Z_C = 20.02 \angle 29.81^\circ$$

$$S_N = 853.98 \angle 20.69^\circ$$

$$\cos(29.81) = \frac{x}{20.02}$$

$$x = 17.371$$

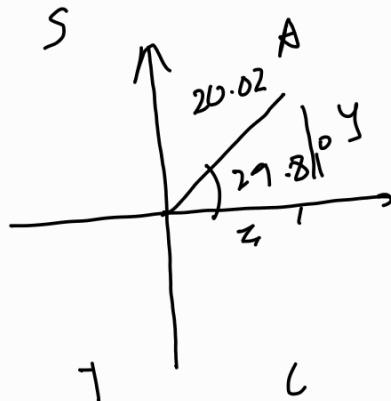

$$\sin(29.81) = \frac{y}{20.02}$$

$$y = 9.9525$$

$$Z = 17.371 + j9.9525 \angle$$

$$= 17.37 + j9.95 \angle$$

XX

- (c) Use Millmans theorem to **calculate** the voltage between the two neutral terminals N and S for the case where the neutral

wire is disconnected (open circuit). **Calculate** voltages V_{AS} , V_{BS} , V_{CS} and currents I_A, I_B, I_C across each load. Calculate **total complex power** consumed by the three-phase load. Show full workings.

Hint: complex conjugate is required for power calculations.

[11 marks]

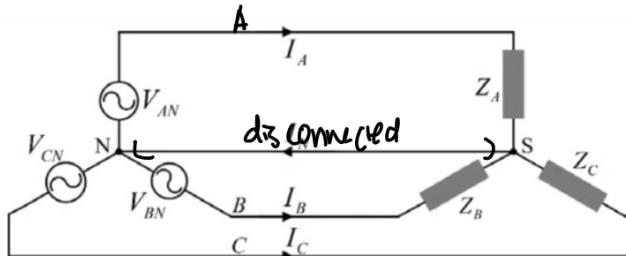


Fig. 4. The circuit for question 3

END OF PAPER

$$V_{SN} = \frac{\frac{230\angle 0}{10\angle 0} + \frac{230\angle -120}{15\angle 45} + \frac{230\angle 120}{20.02\angle 29.81}}{\frac{1}{10\angle 0} + \frac{1}{15\angle 45} + \frac{1}{20.02\angle 29.81}}$$

$$= \frac{11.09\angle 42.694}{0.20362\angle -20.699}$$

$$= 54.463\angle 63.39$$

$$V_{AS} = V_{AN} - V_{SN}$$

$$= 230 - 54.463\angle 63.39$$

$$= 211.293\angle -13.324$$

Peak voltage V_{AS}

$$= \sqrt{2} \times 211.293\angle -13.324$$

$$= 298.81\angle -13.324^\circ$$

$$V_{BS} = V_{BN} - V_{SN}$$

$$= 230\angle -120 - 54.463\angle 63.39$$

$$= 284.386\angle -119.35$$

Peak voltage V_{BS}

$$= \sqrt{2} \times 284.386\angle -119.35^\circ$$

$$= 402.1824\angle -119.35^\circ$$

$$V_{CS} = V_{CN} - V_{SN}$$

$$= 230\angle 120 - 54.463\angle 63.39$$

$$= 205.13\angle 132.808$$

Peak voltage V_{CS}

$$= \sqrt{2} \times 205.13\angle 132.808$$

$$= 290.099\angle 132.81^\circ$$

$$I_A = \frac{V_{AS}}{Z_A}$$

$$= \frac{298.81 \angle -13.324}{10}$$

$$= 29.881 \angle -13.324 \text{ A}$$

$$= 29.08 - j6.886 \text{ A}$$

$$I_B = \frac{V_{BS}}{Z_B}$$

$$= \frac{402.1824 \angle -119.35^\circ}{15 \angle 45}$$

$$= 26.81 \angle 164.35^\circ \text{ A}$$

$$= -25.816 + j7.232 \text{ A}$$

$$I_C = \frac{V_{CS}}{Z_C}$$

$$= \frac{205.13 \angle 132.808}{20.02 \angle 29.81}$$

$$= 10.246 \angle 102.998^\circ \text{ A}$$

$$= -2.3045 + j9.983 \text{ A}$$

Complex power

$$S = \frac{1}{2} V I^*$$

$$S_A = (298.81 \angle -13.324)(29.08 + j6.886)$$

$$= \frac{8928.74}{2}$$

$$= 4464.37 \text{ VA}$$

$$S_B = (402.1824 \angle -119.35^\circ)(-25.816 - j7.232) \div 2$$

$$= (2553.71 + j10475.74) \div 2$$

$$= (10782.51 \angle 76.3) \div 2$$

$$= 5391.255 \angle 76.3$$

$$S = \sqrt{RMS} I_{RMS}^*$$

$$\begin{aligned}
 S_c &= \frac{(290.099 \angle 132.81)(-2.3045 - j9.783)}{2} \\
 &= (2578.997 + j1477.72) \div 2 \\
 &= (2972.35 \angle 29.812) \div 2 \\
 &= 1486.175
 \end{aligned}$$

$$S_A + S_B + S_c = \underline{18455.60 \angle 40.37^\circ}$$

$$\begin{aligned}
 S_N &= \sqrt{2}(54.463 \angle 63.39)(0.956 - j10.329) \\
 &= 7989.64 \angle -21.322
 \end{aligned}$$

$$S_A + S_B + S_c + S_N = 18847.61 \angle 38.23 \quad (?)$$

- (b) Neutral current, I_N can be reduced by connecting an impedance, Z_N between the two neutral terminals N and S. **determine** Z_N such that neutral current reduces to $1 \angle 0^\circ$ A. **Calculate** the neutral line voltage V_{SN} . Show full workings.

[6 marks]

$$V_{SN} = \frac{\frac{230 \angle 0}{10 \angle 0} + \frac{230 \angle -120}{15 \angle 45} + \frac{230 \angle 120}{20.02 \angle 29.81}}{\frac{1}{10 \angle 0} + \frac{1}{15 \angle 45} + \frac{1}{20.02 \angle 29.81}}$$

$$= \frac{11.09 \angle 42.694}{0.20362 \angle -20.699}$$

$$= 54.463 \angle 63.39$$

$$I_N = 15.68 \angle 42.7^\circ \quad \text{we want}$$

$$V_{SN} = I_N Z_N \quad I_N = 1 \angle 0^\circ$$

$$Z_N = \frac{V_{SN}}{I_N}$$

$$= \frac{54.463 \angle 63.39}{1 \angle 0}$$

$$= 54.463 \angle 63.39$$

?

$$\frac{15.68 \angle 42.7}{1 \angle 0} \quad V = IR$$

$$= 15.68 \angle 42.7$$

