

- 1 (a) In the network shown in Figure 1, two voltage sources act on the load impedance connected between A, B. If the load Z_L is variable in both resistance and reactance, what load Z_L will receive the maximum power and what is the value of the maximum power? Use Millman's theorem.


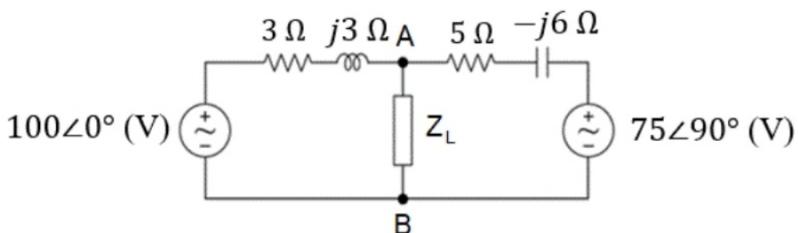


Fig. 1. The circuit for question 1(a)

[7 marks]

Equivalent circuit

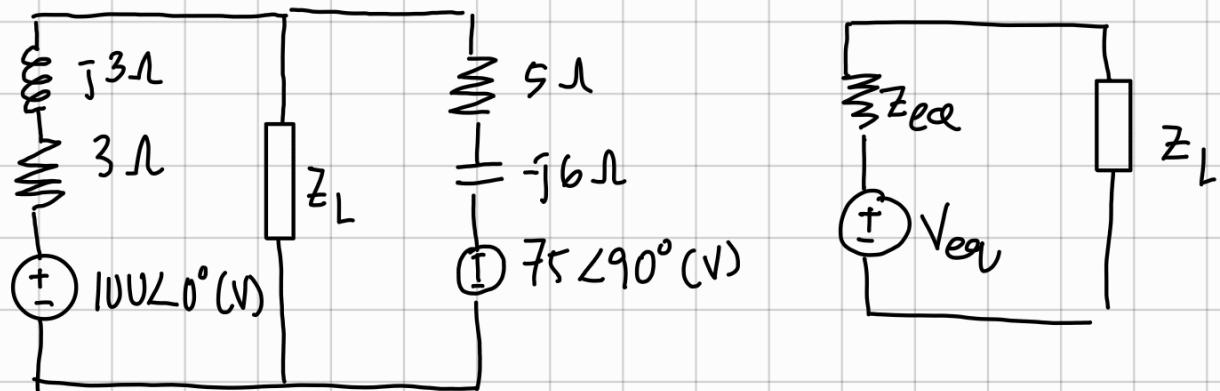

$$\frac{1}{Z_{eq}} = \frac{1}{3+j3} + \frac{1}{5-j6}$$

$$V_1 = 100\angle 0^\circ$$

$$= 100$$

$$V_2 = 75\angle 90^\circ$$

$$= 75j$$

$$= \frac{91}{366} + \frac{25}{366} j \Lambda^{-1}$$

$$Z_{eq} = \frac{273}{73} - \frac{75}{73} j \Lambda$$

$$V_{eq} = \frac{100}{3+j3} + \frac{75j}{5-j6}$$

$$= \frac{91+25j}{366} \Lambda^{-1}$$

$$= 23.9333 - j 48.883 \text{ V}$$

$$= 54.429 \angle -63.913^\circ$$

$$P = VI$$

$$= \frac{V^2}{R}$$

$$= \frac{V^2}{R}$$

$$I_L = \frac{V}{Z_{eq} + Z_L}$$


$$\frac{(54.427 \angle -63.913)^2}{\frac{273-j75}{73} + Z_L} > 0$$

$$\frac{273-j75}{73} + Z_L > 0$$

$$Z_L < -\frac{(273-j75)}{73}$$

$$Z_L < -\frac{273}{73} + j\frac{75}{73}$$

$$Z_L < -3.73972 + j1.0274$$

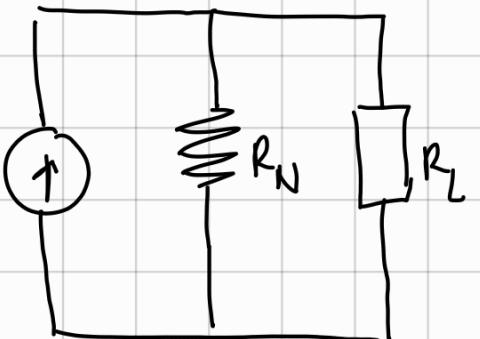

$$Z_L = 0$$

$$P = \frac{V^2}{R}$$

$$= \frac{(54.427 \angle -63.913)^2}{\frac{273-j75}{73}}$$

$$= -291.861 - j705.86$$

$$= 763.82 \angle -112.5^\circ$$

$$E = I_N \times R_N$$

- (b) Consider the circuit in Figure 2, operating in steady state at a particular frequency. The values of the parameters are $X_1 = 40 \Omega$, $X_2 = 40 \Omega$, $B_I = 1/80 \text{ mho}$. Find the impedances Z_i and Z_L so that the circuit is matched.

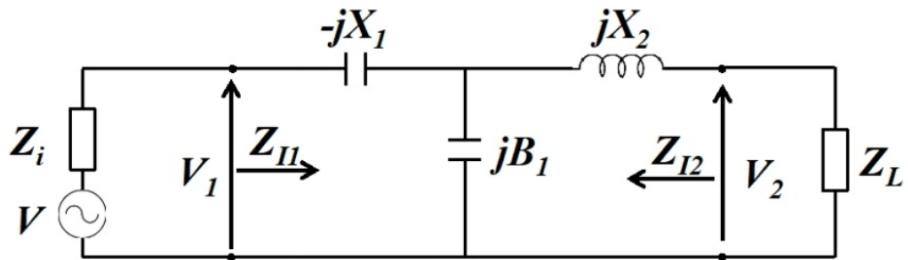


Fig. 2. The circuit for question 1(b)

[10 marks]

Question 2

- (a) Find and draw the Norton equivalent to the circuit shown in Figure 4 (with respect to the terminals A and B). The values of the components are $V_0 = 8 \text{ V}$, $R_1 = 4 \Omega$, $R_2 = 1 \Omega$, and $R_L = 5 \Omega$.

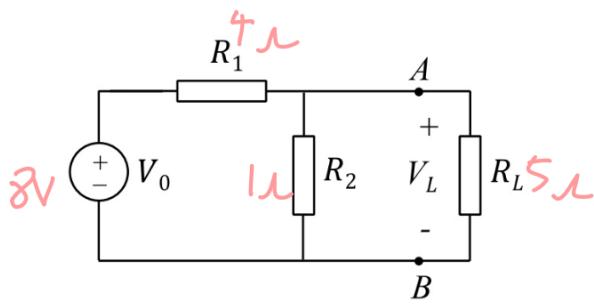


Fig. 4. The circuit for question 2(a)

[5 marks]

Total resistance (except R_1)

$$= R_1 + R_2 = 4 + 1 = 5 \Omega$$

$$I_{\text{total}} = \frac{8}{5} = 1.6 \text{ A}$$

$$= \left(\frac{1}{4} + \frac{1}{1} \right)^{-1} = 0.8 \Omega$$

Voltage drop across R_1 ,

$$\begin{aligned} V &= IR \\ &= 1.6(4) \\ &= 6.4 \text{ V} \quad \text{--- logical} \end{aligned}$$

$$\begin{aligned} V_2 &= 8 - 6.4 \\ &= 1.6 \text{ V} \end{aligned}$$

$$V = IR$$


$$I = \frac{V}{R}$$

$$= \frac{1.6}{5} = 0.32 \text{ A}$$

$$I_{\text{Norton}} = 0.32 \text{ A}$$

Norton's equivalent circuit

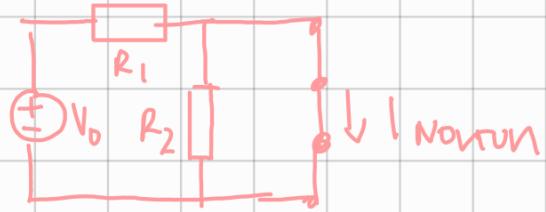1. Remove the $Z_L/R_L \rightarrow$ replace with short circuit




2. Find I_{Norton} by calculating the current through the short circuit where the load was.

3. Find R_{Norton} by creating open circuit where the load resistor is shorted all voltage sources $\not\equiv$ by open circuiting all the current sources.



$$\begin{aligned} R_{\text{Norton}} &= R_1 + R_2 \\ &= 5 \Omega \end{aligned}$$

Equivalent circuit

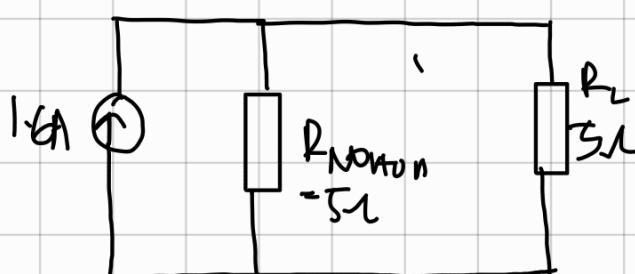

Check Validity

salah

- (b) Consider the circuit in Figure 5. Using mesh analysis, find the values of i_1 , i_2 , and i_3 when $V_0 = 4 \text{ V}$, $I_0 = 1 \text{ A}$, $R_1 = R_2 = 2 \Omega$, $R_3 = 3 \Omega$, and $R_4 = 4 \Omega$.

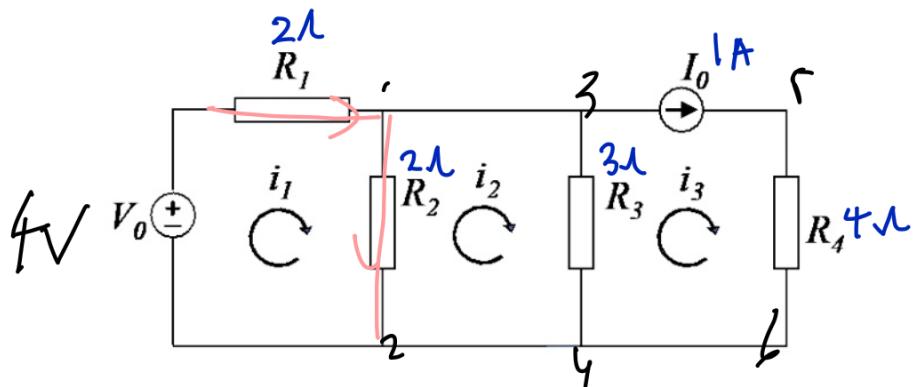


Fig. 5. The circuit for question 2(b)

[8 marks]

Mesh analysis

$$V_0 = i_1 R_1 + (i_1 - i_2) R_2$$

$$4 = 2i_1 + 2(i_1 - i_2)$$

$$0 = (i_2 - i_1) R_2 + (i_2 - i_3) R_3$$

$$4 = 4i_2 - 2i_1$$

$$(i_3 - i_2) R_3 + (i_3 + i_0) R_4 = 0$$

$$2 = 2i_3 - i_2 - ①$$

$$3(i_3 - i_2) + 4(i_3 + 1) = 0$$

$$2(i_2 - i_1) + 3(i_2 - i_3) = 0$$

$$7i_3 - 3i_2 + 4 = 0$$

$$5i_2 - 2i_1 - 3i_3 = 0 - ②$$

$$7i_3 - 3i_2 = -4 - ③$$

$$i_1 = \frac{2 + i_2}{2}$$

into ②

$$5i_2 - 2\left(\frac{2+i_2}{2}\right) - 3\left(\frac{-4+3i_2}{7}\right) = 0$$

$$i_3 = \frac{-4+3i_2}{7}$$

$$5i_2 - 2 - i_2 + \frac{12}{7} - \frac{9}{7}i_2 = 0$$

$$i_1 = \frac{2 + \left(\frac{2}{19}\right)}{2}$$

$$4i_2 - \frac{1}{7}i_2 = \frac{2}{7}$$

$$= \frac{40}{38} A$$

$$\frac{19}{7}i_2 = \frac{2}{7}$$

$$i_2 = \frac{2}{19} A$$

$$i_3 = -4 + 3\left(\frac{2}{19}\right)$$

$$= \frac{7}{19} A$$

$$= -\frac{10}{19} A$$

$$I_1 = \frac{40}{38} A \quad I_2 = \frac{2}{19} A \quad I_3 = -\frac{10}{19} A$$

check

- (a) Describe what are meant by characteristic impedance and phase velocity. Explain when propagation constant becomes purely an imaginary number.

[6 marks]

Question 3

- (b) A 75Ω coaxial transmission line has a length of 2.0 cm and is terminated with a load impedance of $37.5+j75 \Omega$. Find the input impedance to the line, the reflection coefficient at the load and the reflection coefficient at the input and the SWR on the line for a wave traveling along the line with the wavelength of 16.0 cm.

$$\lambda = 16.0 \text{ cm}$$

[8 marks]

$$Z_L = 37.5 + j75 \quad l = 0.02$$

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tan(\beta l)}{Z_0 + Z_L \tan(\beta l)}$$

$$B = \frac{2\pi}{\lambda}$$

$$= 75 \frac{(37.5+j75) + 75 \tan(39.2699(0.02))}{(75 + (37.5+j75)\tan(39.2699(0.02)))}$$

$$= 39.2699$$

$$= 39.2728 + 73.9547j \Omega$$

$$\Gamma_{load} = \frac{(Z_L - Z_0)}{(Z_L + Z_0)}$$

$$= \frac{37.5 + j75 - 75}{37.5 + j75 + 75}$$

$$= \frac{-37.5 + j75}{112.5 + j75}$$

$$= \frac{1}{13} + \frac{8}{13}j$$

$$= 0.07692$$

$$\Gamma_{input} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$= \frac{39.2728 + 73.9547j - 75}{39.2728 + 73.9547j + 75}$$

$$= \frac{-35.7272 + 73.9547j}{114.2728 + 73.9547j}$$

$$= 0.07484 + 0.59874j$$

$$= 0.6034$$

$$SWR = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|} = \frac{1 + 0.6034}{1 - 0.6034}$$
$$= 4.043$$

c