

ELEC2208 Power Electronics and Drives

Power Electronics **- Introduction -**

Yoshi Tsuchiya
Smart Electronic Materials and Systems (SEMS) Group
yt2@ecs.soton.ac.uk
59/4219

Part 1: Power Electronics

Dr Yoshi Tsuchiya

1. Introduction

2. Diode

3. Thyristor

4. Transistor

Individual devices

5. Heating and Cooling

Thermal management

6. Phase-Controlled Thyristor
Converter and Diode Rectifier

7. Cycloconverter

8. Inverter

9. DC-to-DC Converter

Convertors

Part 1: Timetable 2022/23

W/C	Tuesday 3pm	Wednesday 11am	Thursday 3pm
30 th Jan	Introduction	Diode	Diode/Thyristor
6 th Feb	Thyristor	Tutorial 1	Transistor
13 th Feb	Cooling	Tutorial 2	Phase-Controlled Converter
20 th Feb	Rectifier	Cycloconverter	Tutorial3
27 th Feb	Inverter	DC-DC converter	DC-DC converter
6 th Mar	Tutorial 4	Drive Systems (Fred & Zehor)	...
Room	46/2003	02A/2065	58/1007

12 lectures and 4 tutorials

Part 1: Power Electronics

Tutorials

Tutors will work out the questions in a tutorial sheet to be delivered in advance to tutorials

Revision sessions

Example questions to be worked out: 10 & 11 May 2023

Lecture recording

All the sessions will be recorded.

Further textbook

Daniel W. Hart, “[Power Electronics](#)” 201, McGraw-Hill Companies, Inc

What is Power Electronics?

Definition

Branch of **electrical engineering** devoted to **conversion and control of electric power** using electronic converters based on **semiconductor power switches**.



The input and output may be **alternating current (AC)** or **direct current (DC)** and may differ in magnitude and frequency.

Elements of Power Converters


Passive components

- Capacitors
- Inductors
- Transformers


Power switches

- Diodes
- Thyristors
- Transistors

Application – Electric Vehicle

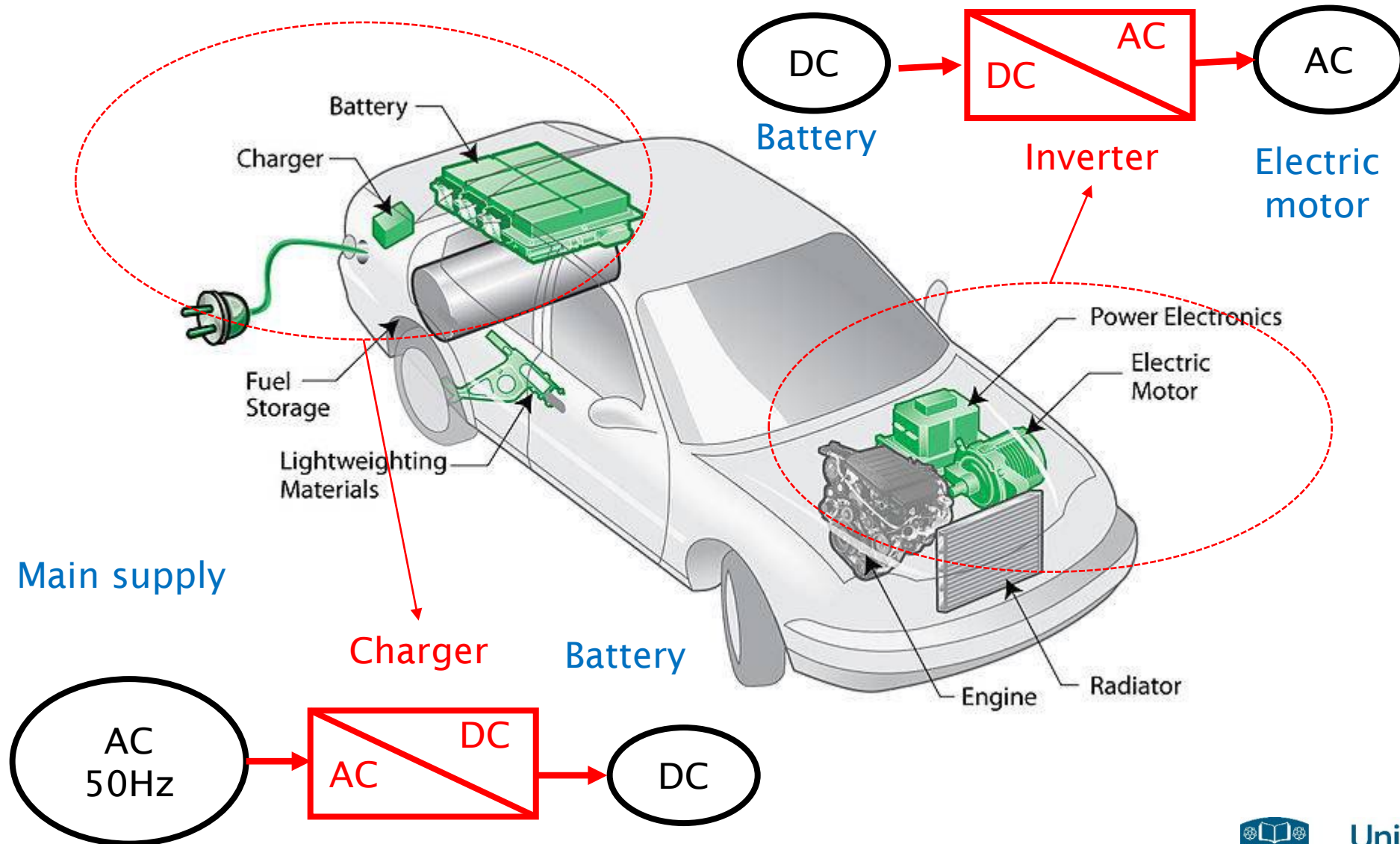

Further applications

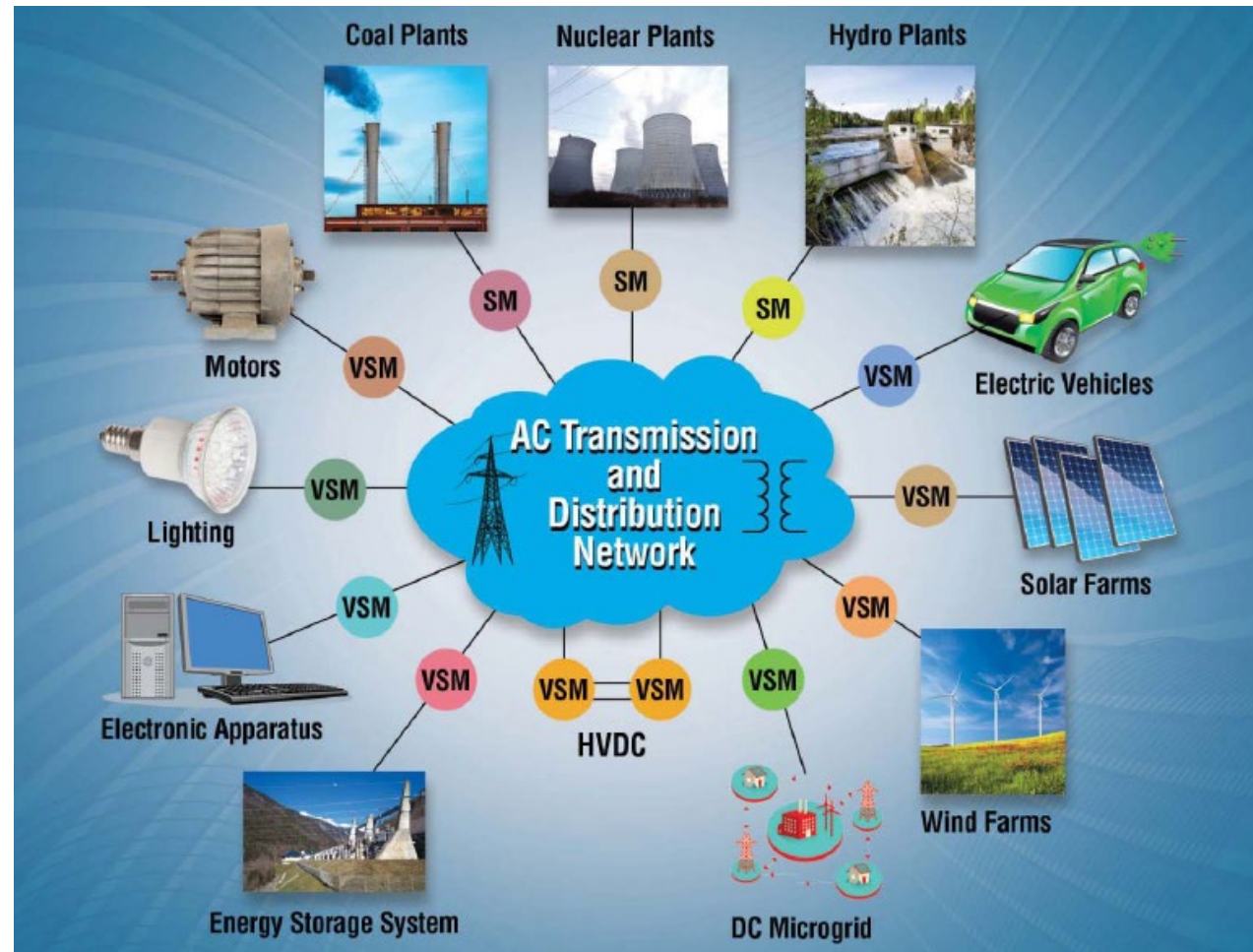

Power electronics is a key enabling technology for a sustainable world.

Classification of Power Converters

Electrical supplies: **AC** or **DC**

—————→ **4 input output combinations**

AC input/DC output – Rectifier

Half-wave, full-wave rectifier, etc.

DC input/AC output – Inverter

Half-bridge, full-bridge, multilevel inverter, etc.


DC input/DC output – DC-DC converter

Buck, boost, buck-boost, etc.

AC input/AC output – AC-AC converter

Matrix converter, cycloconverter, etc.

Classification of Power Converters

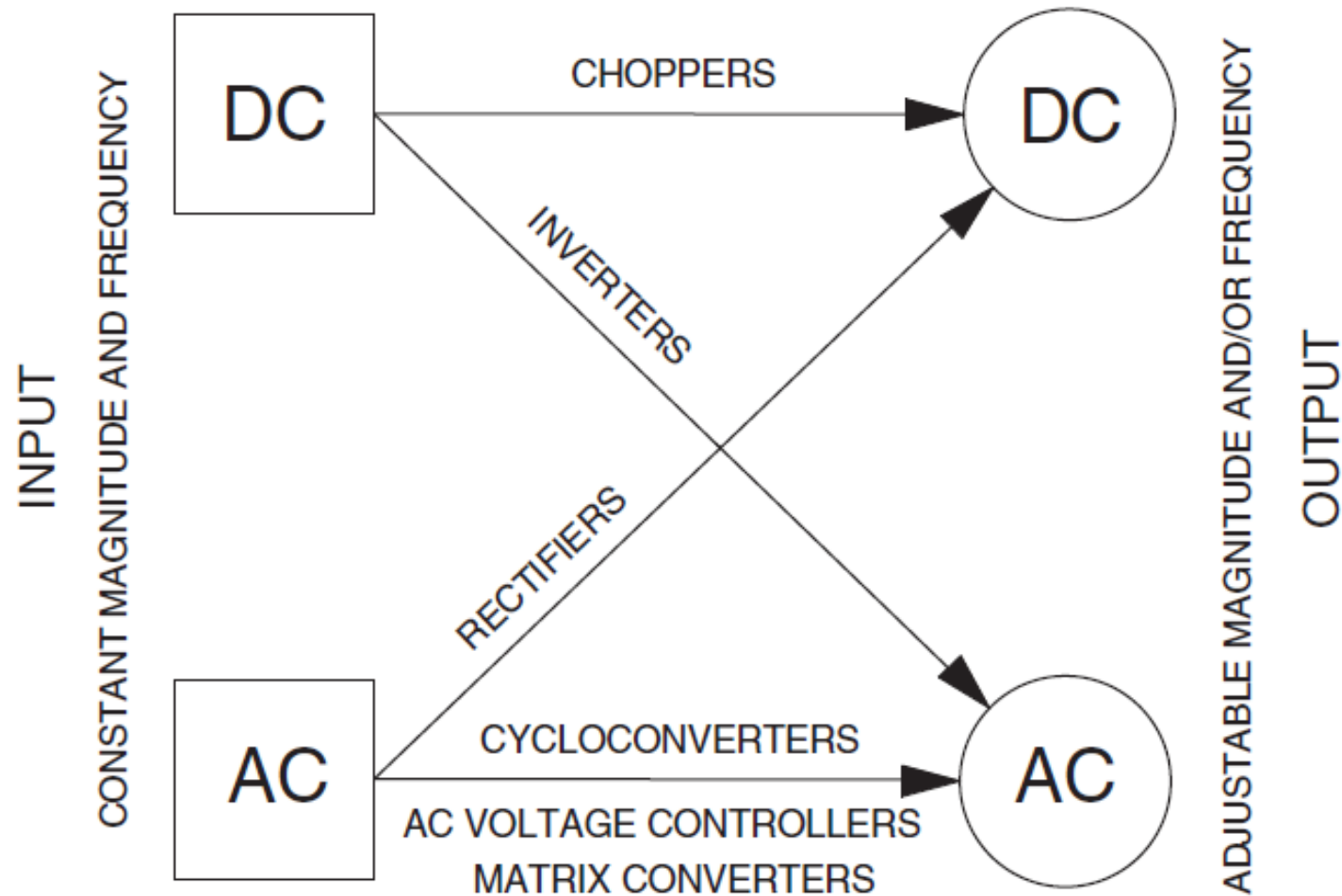


Power Converters - Features

- The voltages on either side of a power converter do not have to be equal.
- For AC supplies, the frequency and phase angle on either side of a power converter can be the same or different.
- Power conversion can be a multistep process (combination of multiple power converters) involving more than one type of converter.

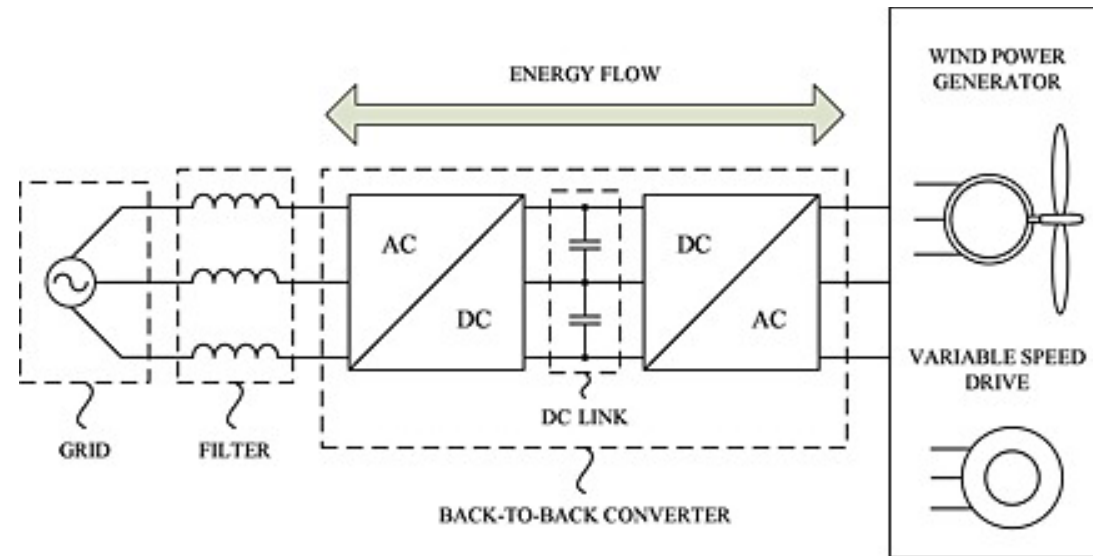
Example:

AC to DC then DC to AC
for motor drive system.



Power Converter Systems

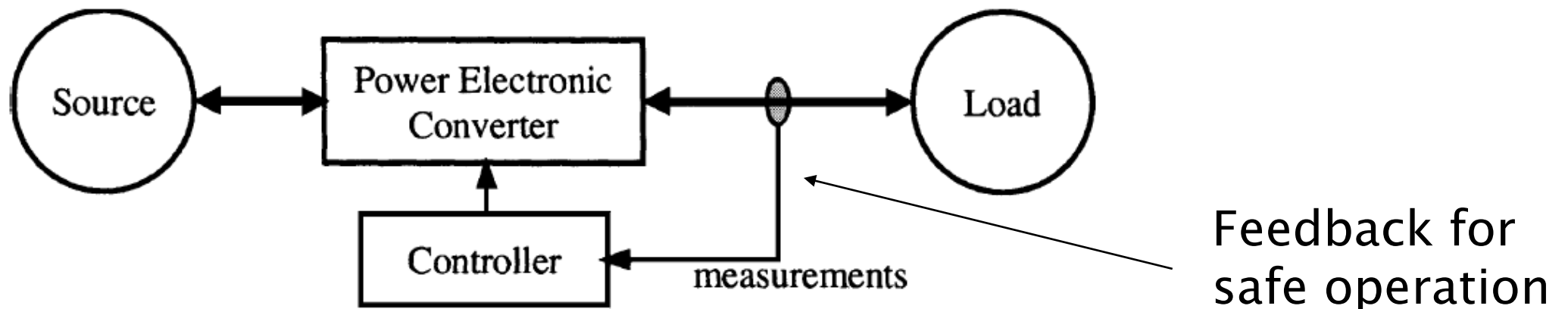- Power converter system consists of semiconductor devices as **power switches** and **passive components** as filter or energy storage elements to synthesize voltage and current waveforms according to the demand.
- Power supply with constant (in most cases) magnitude and frequency.
- Demand with specific magnitude and frequency which is different from the source.



Circuit analysis revision

1. **Passive components**
 - Capacitors
 - Inductors
2. **Wave form analysis**
 - Fourier series
3. **Circuit analysis**
 - KVL, KCL, RMS
4. **Average power**
5. **Ideal vs Practical switches**

Capacitors

Capacitors can store energy in electric field.

Amount of charge stored is proportional to the voltage:


$$Q(t) = C v_C(t) \quad \Delta Q = C \Delta V$$

Energy stored


$$w(t) = \frac{1}{2} C v_C^2$$

Current and voltage
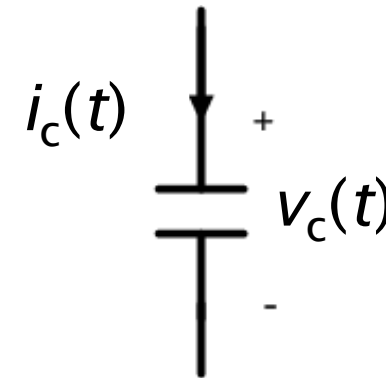
$$i_C(t) = C \frac{dv_C(t)}{dt} \quad v_C(t) = \frac{1}{C} \int_{t_0}^t i_C(t) dt + v_C(t_0)$$



Capacitors

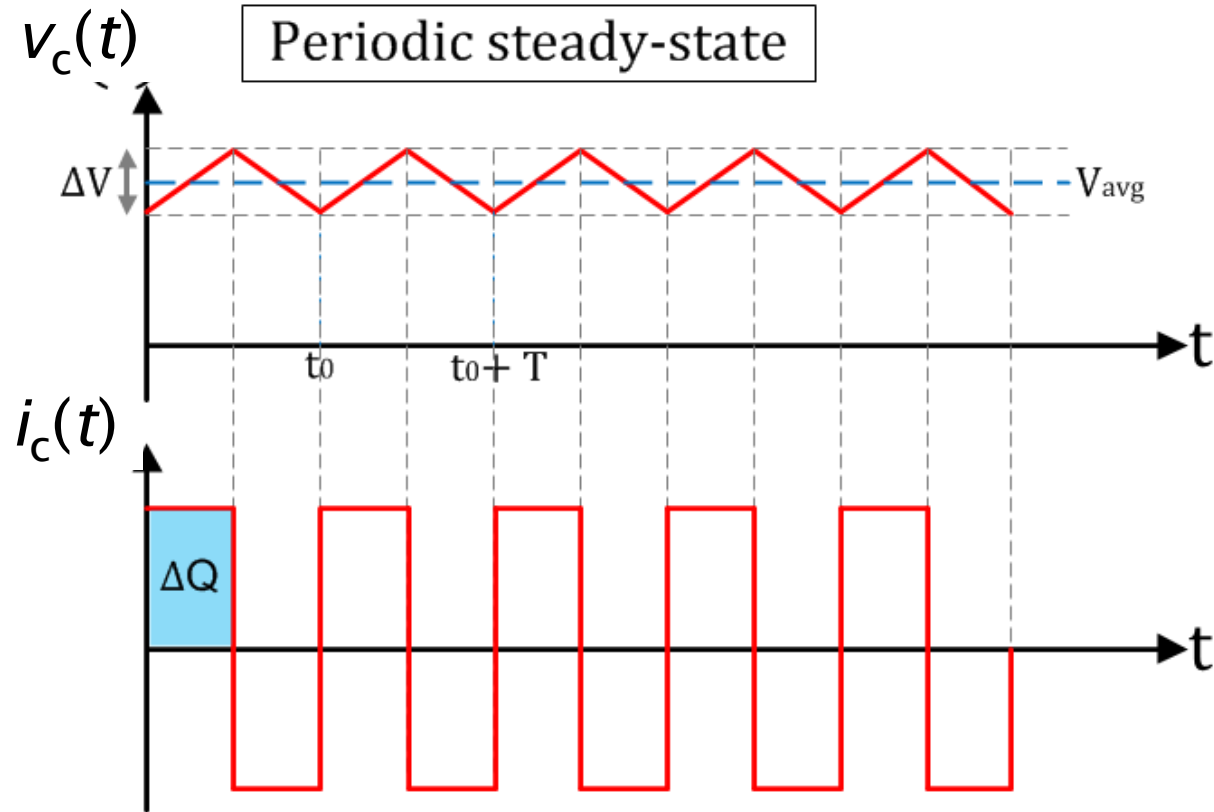

Response to periodic voltage waveform at steady state

$$v_C(t + T) = v_C(t)$$

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$\begin{aligned} \langle i_C(t) \rangle &= I_C \\ &= \frac{1}{T} \int_t^{t+T} i_C(t) dt = 0 \end{aligned}$$

Average current is zero.

Average power: $P_C = 0$

Inductors

Inductors can store energy in magnetic field.

Flux linkage is proportional to the current:


$$\lambda(t) = Li_L(t) \quad \Delta\lambda = L\Delta I$$

Energy stored


$$w(t) = \frac{1}{2} Li_L^2$$

Voltage and current
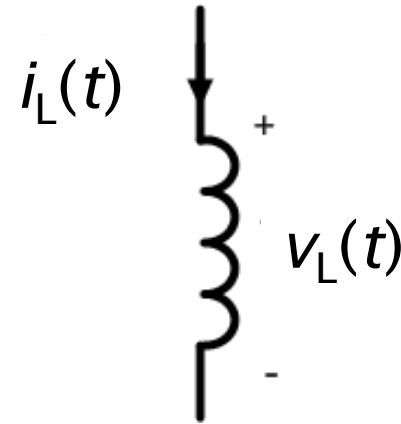
$$v_L(t) = L \frac{di_L(t)}{dt} \quad i_L(t) = \frac{1}{L} \int_{t_0}^t v_L(t) dt + i_L(t_0)$$



Inductors

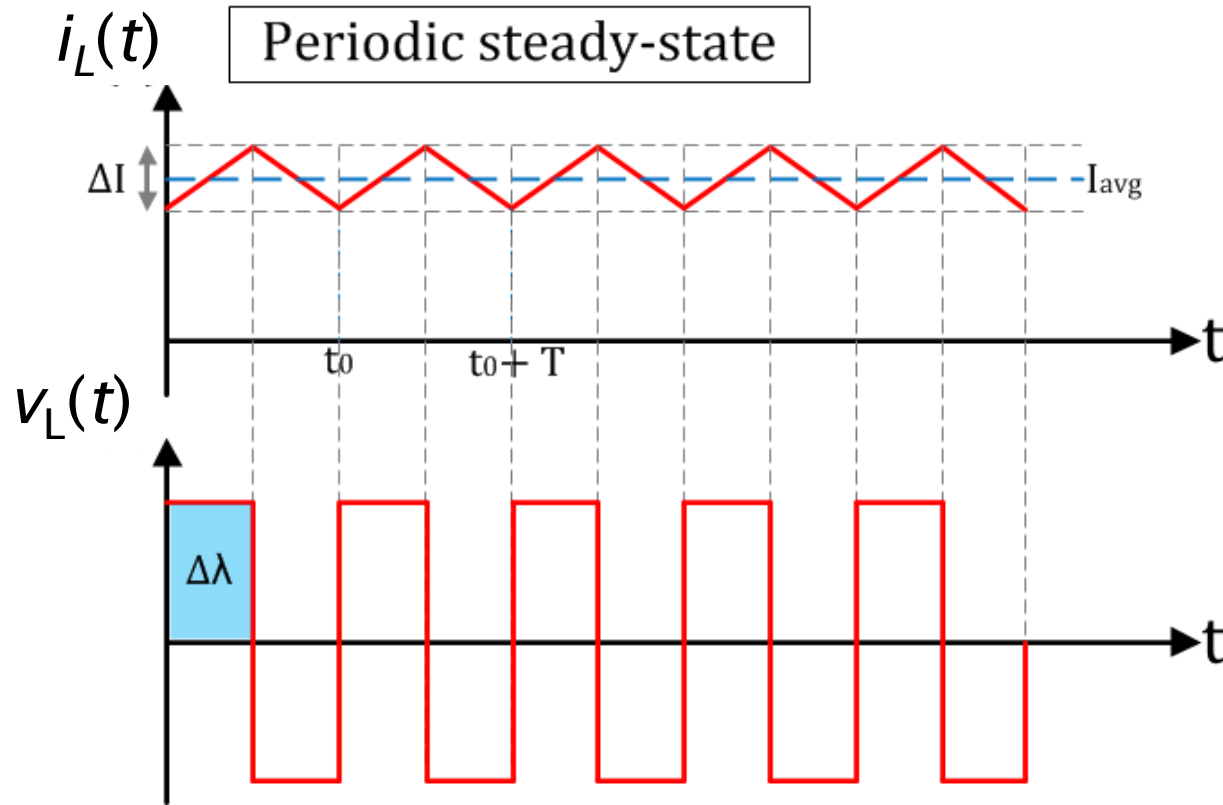

Response to periodic current waveform at steady state

$$i_L(t + T) = i_L(t)$$

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$\begin{aligned} \langle v_L(t) \rangle &= V_L \\ &= \frac{1}{T} \int_t^{t+T} v_L(t) dt = 0 \end{aligned}$$

Average voltage is zero.

Average power: $P_L = 0$


Analysis of Waveform

Periodic waveforms

The magnitude at the end of one period is the same as the beginning.



$$f(t + T) = f(t)$$

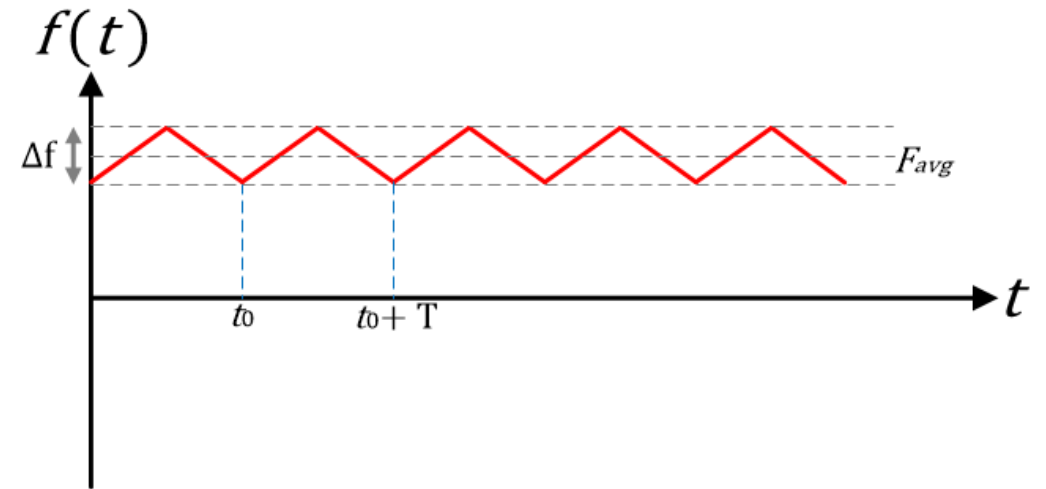The periodic waveform consists of DC and AC components and can be described by a **Fourier Series** of sinusoids.



Analysis of Waveform

Periodic waveforms

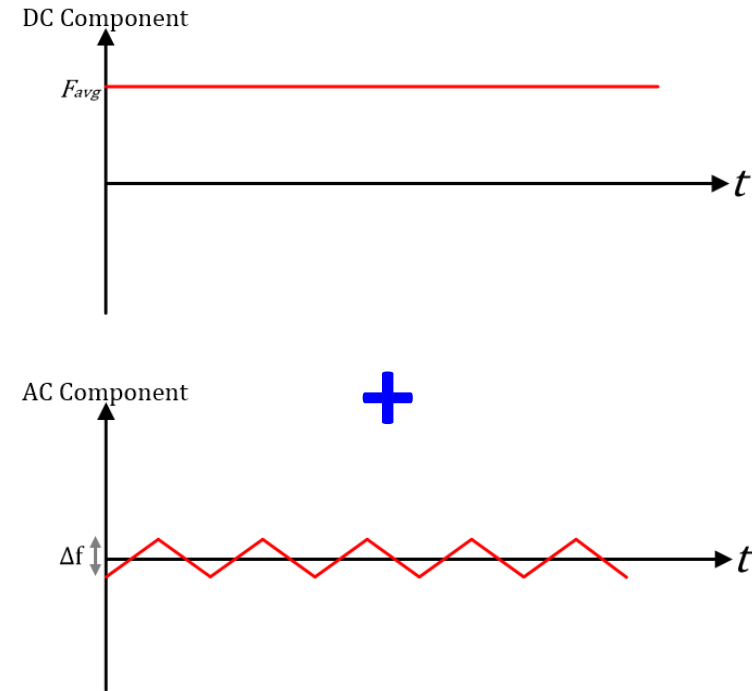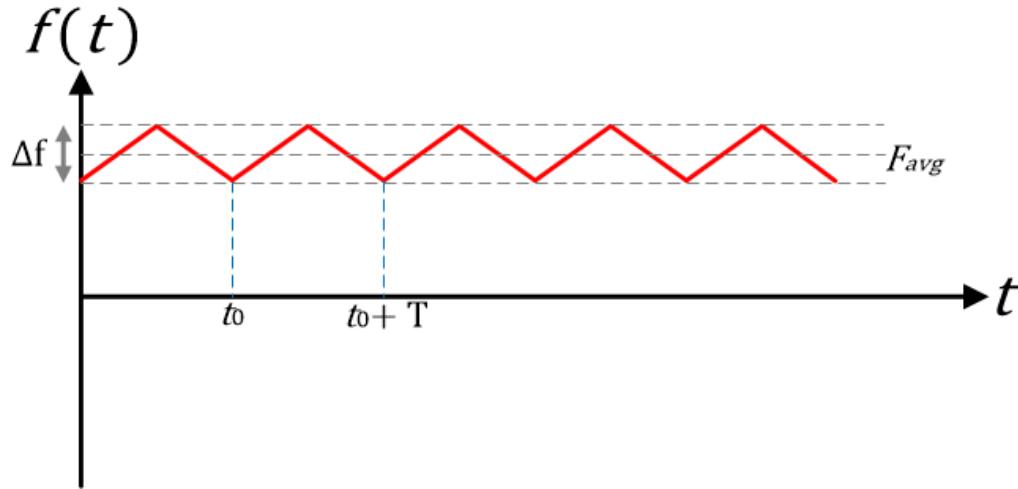

Fourier Series

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)]$$

$$= \frac{a_0}{2} + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \theta_n) \quad \leftarrow \text{AC components}$$

DC component



KVL and KCL

$$v(t) = V_{dc} + \sum_{n=1}^n V_n \cos(n\omega_0 t + \theta_n) \quad i(t) = I_{dc} + \sum_{n=1}^n I_n \cos(n\omega_0 t + \phi_n)$$

Circuit analysis methods, KVL and KCL apply individually to DC and AC components.

KVL

$$v(t) = V_{dc} + v_{ac}(t)$$

$$\sum_{loop} V_{dc} = 0$$


$$\sum_{loop} v_{ac}(t) = 0$$

KCL

$$i(t) = I_{dc} + i_{ac}(t)$$

$$\sum_{node} I_{dc} = 0$$

$$\sum_{node} i_{ac}(t) = 0$$

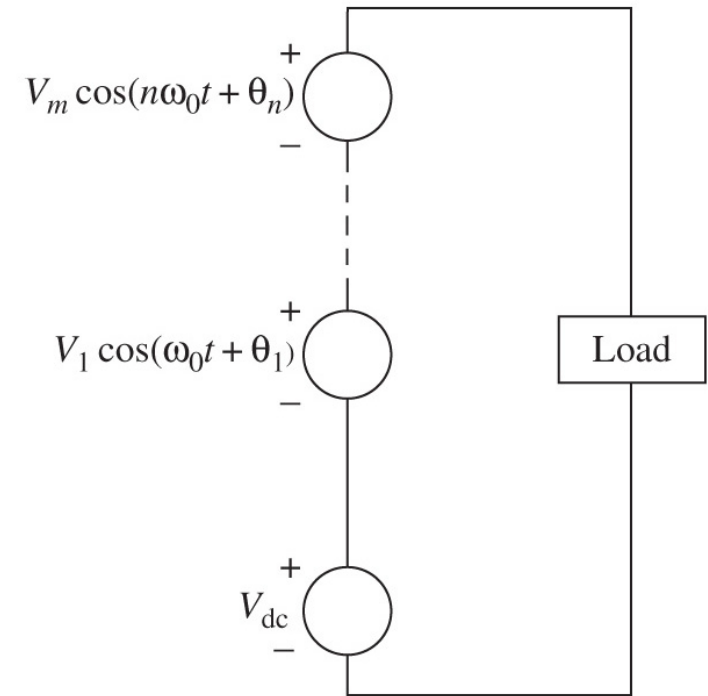

Root Mean Square (RMS)

RMS of a function $f(t)$

$$F_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} f^2(t) dt}$$

If $f(t)$ is sum of N periodic waveforms: $f(t) = f_1(t) + f_2(t) + \dots + f_N(t)$

$$F_{rms} = \sqrt{F_{1,rms}^2 + F_{2,rms}^2 + \dots + F_{N,rms}^2} = \sqrt{\sum_{n=1}^N F_{n,rms}^2}$$

If $f(t)$ is Fourier Series: $f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \theta_n)$

$$F_{rms} = \sqrt{\sum_{n=1}^{\infty} F_{n,rms}^2} = \sqrt{\left(\frac{a_0}{2}\right)^2 + \sum_{n=1}^{\infty} \left(\frac{C_n}{\sqrt{2}}\right)^2}$$

Power

Average of a function $f(t)$:

$$F_{mean} = \frac{1}{T} \int_{t_0}^{t_0+T} f(t) dt$$

Power

Instantaneous power

$$p(t) = v(t)i(t)$$

Average power/real power

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt = \frac{1}{T} \int_{t_0}^{t_0+T} v(t)i(t) dt$$

DC average power

$$P = V_{dc} I_{dc} \quad \text{if } v(t) = V_{dc} \text{ and } i(t) = I_{dc}.$$

If $v(t)$ and $i(t)$ are sinusoidal waveforms,

AC average power

$$P = V_{rms} I_{rms} \cos(\theta - \phi)$$

θ : Phase of voltage
 ϕ : Phase of current

Power factor

$$pf = \cos(\theta - \phi)$$

Power

If $v(t)$ and $i(t)$ are non-sinusoidal periodic waveforms,

$$v(t) = V_{dc} + \sum_{n=1}^n V_n \cos(n\omega_0 t + \theta_n) \quad i(t) = I_{dc} + \sum_{n=1}^n I_n \cos(n\omega_0 t + \phi_n)$$

Average power

$$P = V_{dc} I_{dc} + \sum_{n=1}^{\infty} V_{n,rms} I_{n,rms} \cos(\theta_n - \phi_n)$$

Power factor

$$pf = \frac{P}{S} = \frac{P}{V_{rms} I_{rms}}$$

$$S = V_{rms} I_{rms} \quad \text{Magnitude of apparent power}$$

Ideal power devices

Ideal characteristics of power switches

- Turn on and off instantaneously without delay
- High speed switching
- Zero power loss


Ideal ON-state

Zero voltage drop across the switch and it can conduct infinite current due to zero impedance.


Ideal OFF-state

Zero current flow due to infinite impedance and it can block infinite voltage.

Ideal switch
in on state

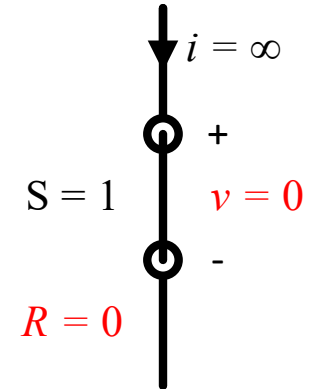

Ideal switch
in off state

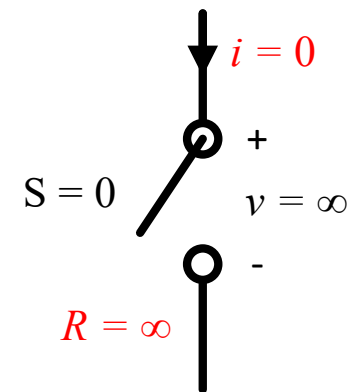

Practical power devices

- Real power switches are semiconductor devices.
- They consume some power during operation.
- **Leakage current flows during Off state.**
- **Voltage drop occurs during On state** due to on resistance.
- Semiconductor power devices does not switch instantly. Delay during switching instant causes **switching loss**.
- Switching loss limits the switching frequency.
- Voltage and current of semiconductor power devices should be kept within **the safe operating value** to prevent failure.
- Due to power losses, **cooling by attaching the devices to heat sink is usually required** to keep the temperature of the devices within limits.

We need to study Power Electronics!